

# Digital Logic Circuit (SE273 – Fall 2020)

## Lecture 6: Hardware Description Languages




*Some slides from ICL, Peter Chung*

Jaesok Yu, Ph.D. (jaesok.yu@dgist.ac.kr)

Assistant Professor  
*Department of Robotics Engineering, DGIST*
 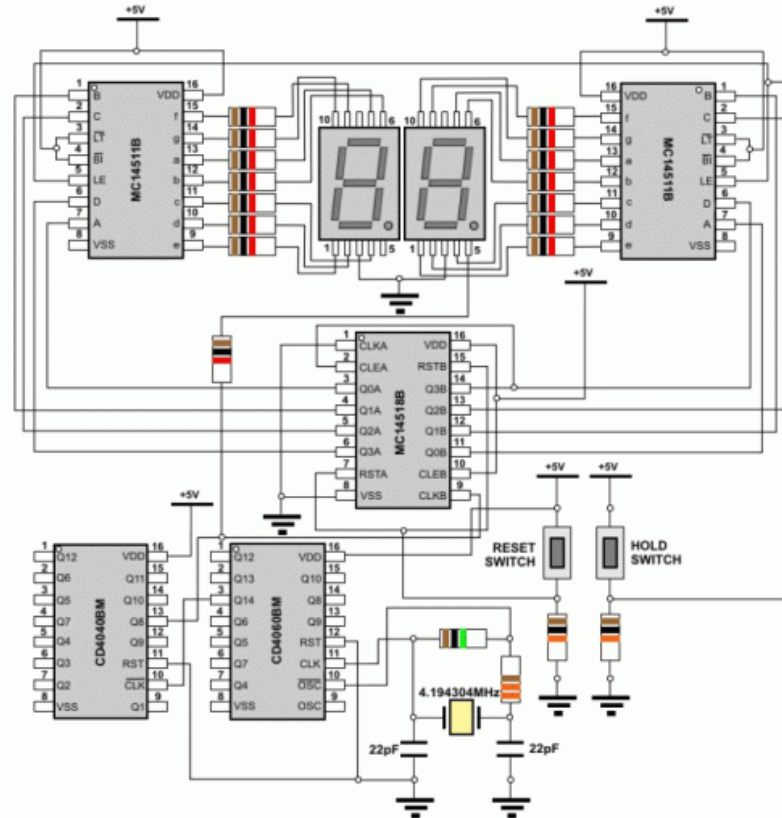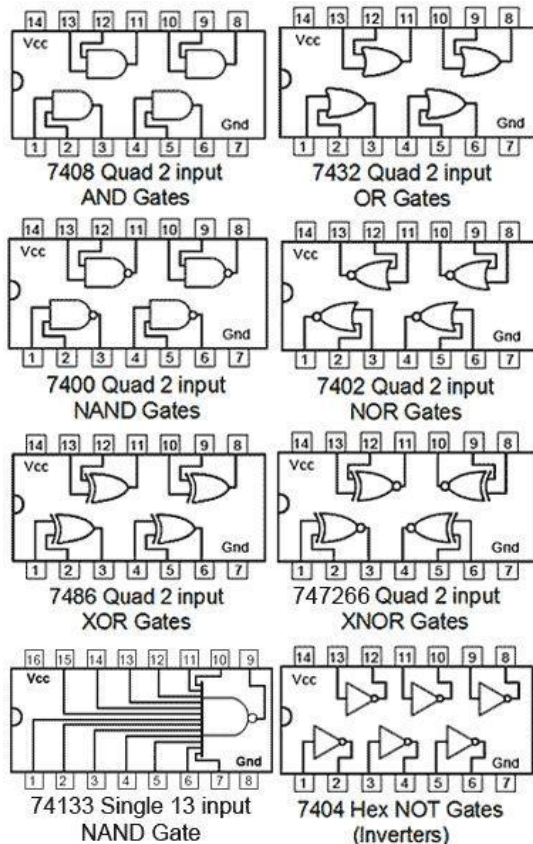
# ▶ Traditional ways of implementing digital circuit


- Discrete logic based on gates or small silicon
- Tedious, Slow, Expensive, Low Efficiency, Low Readability





 
## ▶ Early Integrated Circuits based on Gate Arrays

- Row of Standard gates – Connect or Disconnect between gates to form customer specific circuits



- Can be full-custom
  - Completely fabricated from scratch
- Can-be semi-custom
  - Customization on the metal layers only
- Once fabricated, the design is fixed.
 
# ► Modern Digital Design – Full custom Integrated Circuits



- Intel Core i9 Die Shot
  - >20 billion transistors
  - Expensive to design and manufacture
  - Highly risky
  - Hard to change the design
  - Not viable unless the market is huge
  - Most applications cannot afford to embark on such a design
- > **FPGA can be solution.**

# ▶ Field Programmable Gate Arrays (FPGAs)

- Combining idea from Programmable Logic Devices (PLDs) and gate arrays
- First introduced by Xilinx (1985)

- **Pros**

- Fast (Parallelism)
- Flexibility
- Power-efficient
- Low prototyping cost




- **Applications**

- ASIC/DSP prototyping (Simulation > FPGA Hardware > ASIC/DSP Hardware)
- A.I. accelerator: **FPGA** vs GPGPU
  - Pros: Performance / Power efficiency / Heat
  - Cons: Requiring hardware design knowledge.
  - (Recently, compiler from C language to HDL was released but you still need to know hardware design skill to achieve high performance.)




# ▶ Field Programmable Gate Array (FPGA)

- Architecture

 

Basic FPGA Architecture

 




Modern FPGA Architecture

# ► Field Programmable Gate Array (FPGA)

## • Architecture

Configurable Logic Block (CLB)


- LUT + Flip-flops

   

Switching Matrix

Routing Channels

I/O Pad

 

X12468-102417


# ▶ Field Programmable Gate Array (FPGA)

- Look-up table (LUT) - This element performs logic operations.
- Flip-Flop (FF) - This register element stores the result of the LUT.
- Wires - These elements connect elements to one another.
- Input/Output (I/O) pads - These physical ports get data in and out of the FPGA.


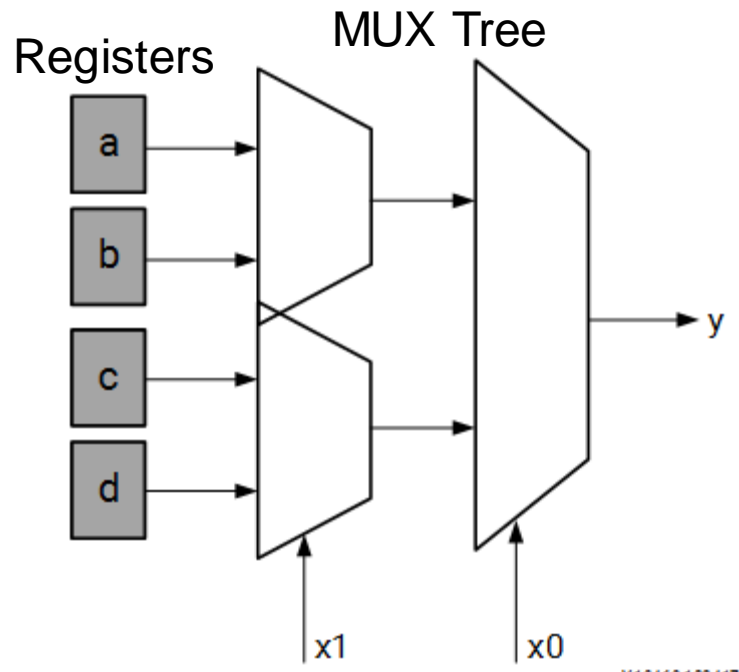
# ► Look-up Table (LUT)


- LUT: The basic building block of an FPGA and is capable of implementing any logic function of N Boolean variables. (In modern Xilinx FPGA, N = 6)
- Truth Table! (Download a BITSTREAM, which is not a PROGRAM)
- **NOTE: Discrete logic gates do not actually exist inside of an FPGA!**



2-input LUT Structure

x0	x1	y
0	0	1
0	1	0
1	0	0
1	1	1


*XNOR Truth Table*

 


ex) LUT implementation of XNOR gate
 
# ► Configurable Logic Block (CLB)

- Based around Look-up Tables
- Optional D-Flipflop at the output of the LUT
- Special Circuit for cascading logic blocks (ex, carry-chain)



CLB with 4-input LUT and D-flipflop

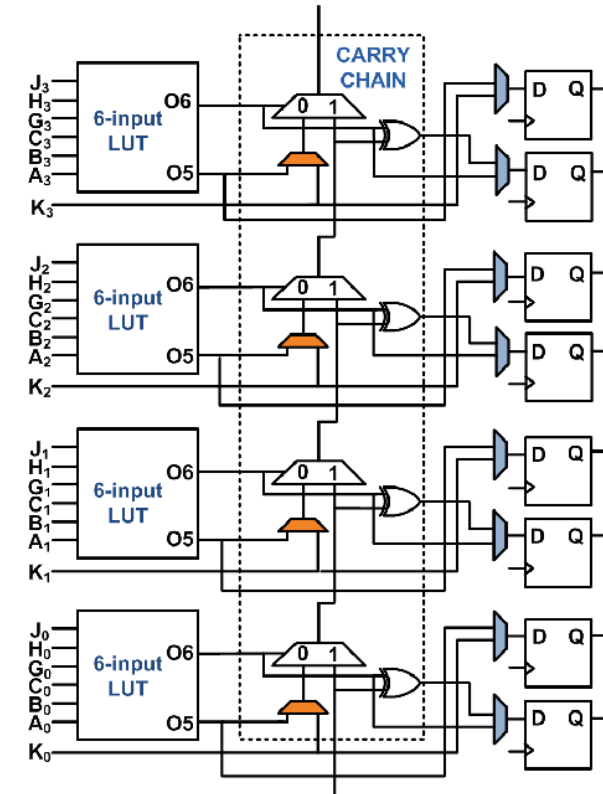

# ▶ Configurable Logic Block (CLB)

## ▶ Two side-by-side slices per CLB



- Slice\_M are memory-capable
- Slice\_L are logic and carry only

## ▶ Four 6-input LUTs per slice

- Consistent with previous architectures
- Single LUT in Slice\_M can be a 32-bit shift register or 64 x 1 RAM
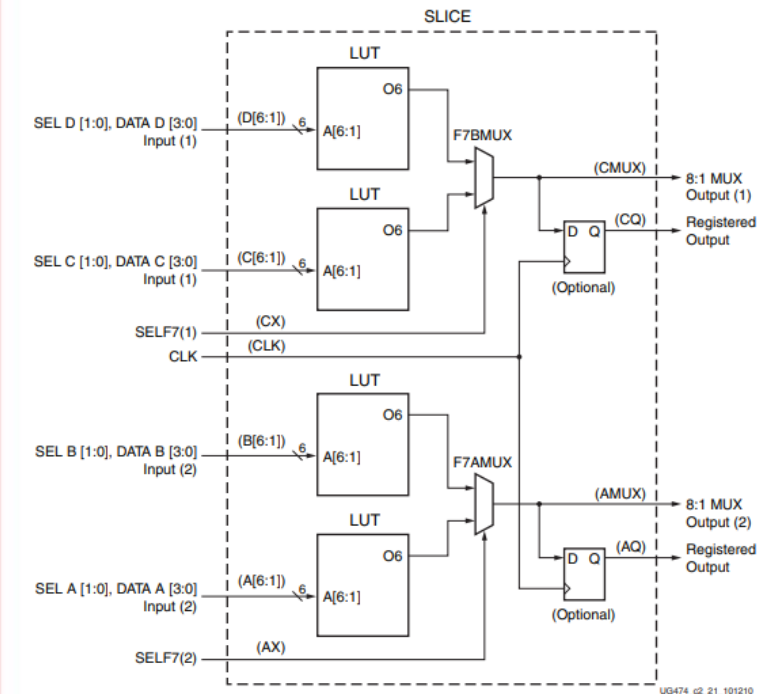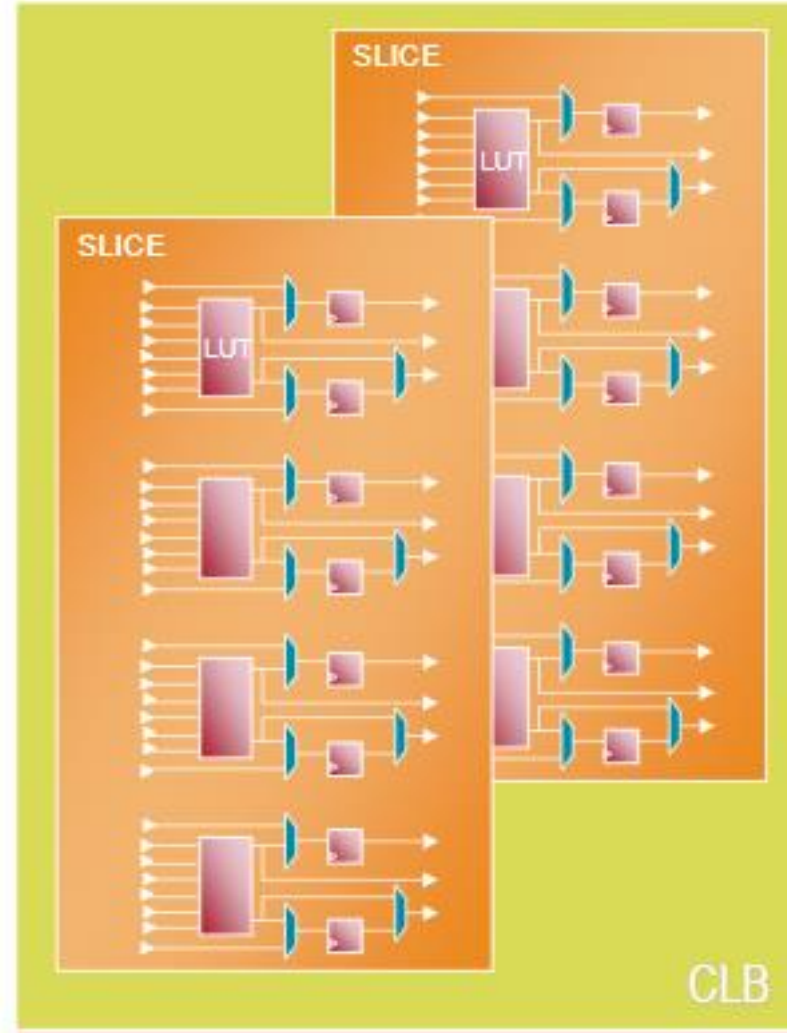
## ▶ Two flip-flops per LUT

- Excellent for heavily pipelined designs



# ► Configurable Logic Block (CLB)

Capacity + Routability

28 nm  
VIRTEX<sup>7</sup>



**7V2000T**

2M System Logic Cells  
1st Gen SSI technology

2011

20 nm  
VIRTEX<sup>U</sup>  
UltraSCALE



**VU440**

5.5M System Logic Cells  
2nd Gen SSI technology

2015

14/16 nm  
VIRTEX<sup>U</sup>  
UltraSCALE<sup>+</sup>



**VU19P**

9M System Logic Cells  
3rd Gen SSI technology

2019

>> 11



© Copyright 2019 Xilinx

XILINX



  
# ▶ Programmable Routing (Switching Matrix)

- Between rows and columns of logic blocks are wiring channels
- **Programmable** – a logic block pin can be connected to one of many wiring tracks through programmable switch
- Each wire segment can be connected in one of many ways


 
# ▶ Programmable Routing (Switching Matrix)

- At each interconnect site, there is a transistor switch which is default OFF (not conducting)
- Each switch is controlled by the output of a 1-bit configuration register
- Configuring the routing is simply to put a '1' or '0' in this register to control the routing switches
- Configuration is volatile
- “Bitstream” is either stored on local flash memory or download via computer
- Configuration happens on Power-up



# Modern FPGA

## Kintex-7 FPGA Feature Summary

Table 6: Kintex-7 FPGA Feature Summary by Device

Device	Logic Cells	Configurable Logic Blocks (CLBs)		DSP Slices <sup>(2)</sup>	Block RAM Blocks <sup>(3)</sup>			CMTs <sup>(4)</sup>	PCIe <sup>(5)</sup>	GTXs	XADC Blocks	Total I/O Banks <sup>(6)</sup>	Max User I/O <sup>(7)</sup>
		Slices <sup>(1)</sup>	Max Distributed RAM (Kb)		18 Kb	36 Kb	Max (Kb)						
XC7K70T	65,600	10,250	838	240	270	135	4,860	6	1	8	1	6	300
XC7K160T	162,240	25,350	2,188	600	650	325	11,700	8	1	8	1	8	400
XC7K325T	326,080	50,950	4,000	840	890	445	16,020	10	1	16	1	10	500
XC7K355T	356,160	55,650	5,088	1,440	1,430	715	25,740	6	1	24	1	6	300
XC7K410T	406,720	63,550	5,663	1,540	1,590	795	28,620	10	1	16	1	10	500
XC7K420T	416,960	65,150	5,938	1,680	1,670	835	30,060	8	1	32	1	8	400
XC7K480T	477,760	74,650	6,788	1,920	1,910	955	34,380	8	1	32	1	8	400

**Notes:**

- Each 7 series FPGA slice contains four LUTs and eight flip-flops; only some slices can use their LUTs as distributed RAM or SRLs.
- Each DSP slice contains a pre-adder, a 25 x 18 multiplier, an adder, and an accumulator.
- Block RAMs are fundamentally 36 Kb in size; each block can also be used as two independent 18 Kb blocks.
- Each CMT contains one MMCM and one PLL.
- Kintex-7 FPGA Interface Blocks for PCI Express support up to x8 Gen 2.
- Does not include configuration Bank 0.
- This number does not include GTX transceivers.

Table 7: Kintex-7 FPGA Device-Package Combinations and Maximum I/Os

Package <sup>(1)</sup>	FBG484			FBG676 <sup>(2)</sup>			FFG676 <sup>(2)</sup>			FBG900 <sup>(3)</sup>			FFG900 <sup>(3)</sup>			FFG901			FFG1156		
Size (mm)	23 x 23			27 x 27			27 x 27			31 x 31			31 x 31			31 x 31			35 x 35		
Ball Pitch (mm)	1.0			1.0			1.0			1.0			1.0			1.0			1.0		
Device	GTX <sup>(4)</sup>	I/O		GTX <sup>(4)</sup>	I/O		GTX	I/O		GTX <sup>(4)</sup>	I/O		GTX	I/O		GTX	I/O		GTX	I/O	
		HR <sup>(5)</sup>	HP <sup>(6)</sup>		HR <sup>(5)</sup>	HP <sup>(6)</sup>		HR <sup>(5)</sup>	HP <sup>(6)</sup>		HR <sup>(5)</sup>	HP <sup>(6)</sup>		HR <sup>(5)</sup>	HP <sup>(6)</sup>		HR <sup>(5)</sup>	HP <sup>(6)</sup>		HR <sup>(5)</sup>	HP <sup>(6)</sup>
XC7K70T	4	185	100	8	200	100															
XC7K160T	4	185	100	8	250	150	8	250	150												
XC7K325T				8	250	150	8	250	150	16	350	150	16	350	150						
XC7K355T																24	300	0			
XC7K410T				8	250	150	8	250	150	16	350	150	16	350	150						
XC7K420T																28	380	0	32	400	0
XC7K480T																28	380	0	32	400	0

**Notes:**

- All packages listed are Pb-free (FBG, FFG with exemption 15). Some packages are available in Pb option.
- Devices in FBG676 and FFG676 are footprint compatible.
- Devices in FBG900 and FFG900 are footprint compatible.
- GTX transceivers in FB packages support the following maximum data rates: 10.3Gb/s in FBG484; 6.6Gb/s in FBG676 and FBG900. Refer to *Kintex-7 FPGAs Data Sheet: DC and AC Switching Characteristics (DS182)* for details.
- HR = High-range I/O with support for I/O voltage from 1.2V to 3.3V.
- HP = High-performance I/O with support for I/O voltage from 1.2V to 1.8V.

# ▶ Hardware Description Languages (HDLs)

Verilog:

```

1
2
3 always @((S0,S1), A, B, C, D)
4     case ((S0,S1))
5         2'b00: Y = A;
6         2'b01: Y = B;
7         2'b10: Y = C;
8         2'b11: Y = D;
9     endcase
10

```

Verilog	VHDL
ASIC Designs	FPGA Designs
Weakly Typed	Strongly Typed
Low Verbosity	High Verbosity
Partially Deterministic	Very Deterministic
More "C" like	Non "C" like

VHDL:

```

2 process ((S0,S1), A, B, C, D)
3 begin
4     case (S0,S1), is
5         when "00" => Y <= A;
6         when "01" => Y <= B;
7         when "10" => Y <= C;
8         when "11" => Y <= D;
9         when others => Y <= A;
10    end case;
11 end process;

```

IEEE standard (1364)

(<https://standards.ieee.org/standard/1364-2005.html>)

IEEE standard (1076)

(<https://standards.ieee.org/standard/1076-2019.html>)

Originated from Cadence (Industry)

Originated from USA DoD

## Other HDL..


- ABEL (Advanced Boolean Expression Language)
- AHDL (Altera HDL)
- JHDL (Java HDL)
- MyHDL (Python-based HDL).
- Etc.

V = Very-High-Speed Integrated Circuits


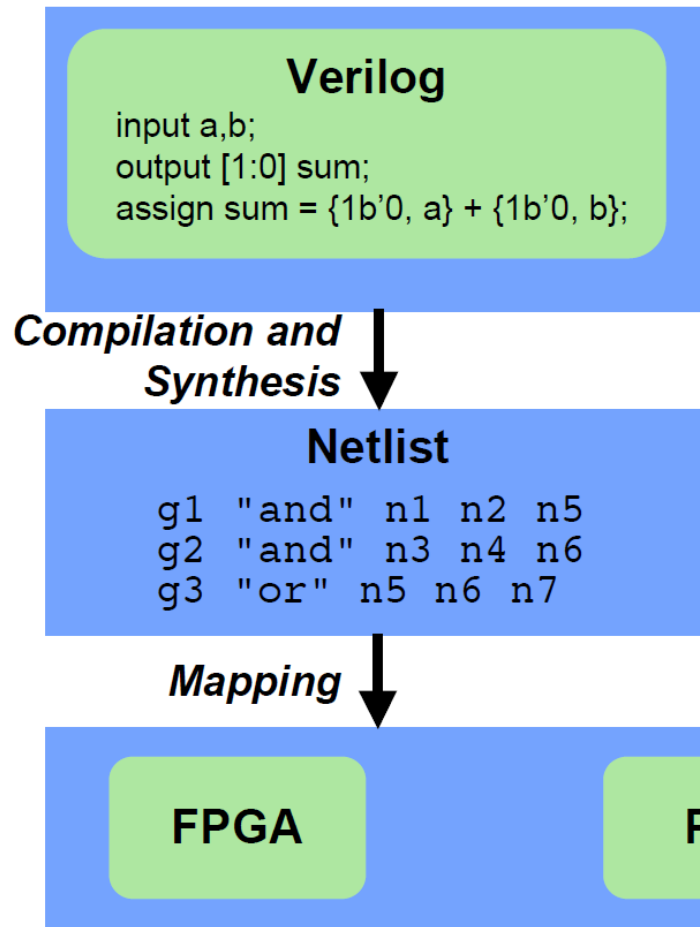
# ▶ HDLs and Synthesis

- Hardware Description Language (HDL) is a convenient, device-independent representation of digital logic



- HDL description is compiled into a **netlist**
- **Synthesis** optimizes the logic
- Mapping targets a specific hardware platform


## ► Synthesis and Mapping

- Infer macros: choose FPGA macros that efficiently implement various parts of the HDL code

```
...  
always @ (posedge clk)  
begin  
    count <= count + 1;  
end  
...
```

*HDL Code*

 
*“This section of code looks like  
a counter. My FPGA has some  
of those...”*



*Inferred Macro*
 
# ► Synthesis and Mapping

- Place-and-Route: with area and/or speed in mind, choose the needed macros by location and route the interconnect




*“This design only uses 10% of the FPGA. Let’s use the macros in one corner to minimize the distance between blocks.”*

# ▶ VHDL


- VHDL = VHSIC Hardware Description Language
  - VHSIC = Very High-Speed Integrated Circuit
- Developed in 1980's by US DOD
- ANSI/IEEE Standard 1076
- VHDL descriptions can be synthesized and implemented in programmable logic
  - NOTE: Synthesis tools can accept only subset of VHDL
- Some useful rules
  - VHDL is not case sensitive
  - Identifier must start with a letter
  - All statements end with a semi-colon
  - Comments precede with (--)
  - "<=" - signal assignment
  - ":=" - variable assignment
  - Signals have a one-time value set associated to it at any time.



# ▶ VHDL Hierarchy

 

# ▶ VHDL structure

 

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity encoder is
    Port (
        a: IN std_logic;
        b: in std_logic;
        c: in std_logic;
        d: in std_logic;
        y: out std_logic_vector(8 downto 0));
end encoder;

architecture Behavioral of encoder is
begin
    y <= "000000000" WHEN (a = '0' and b = '0' and c = '0' and d = '0') ELSE
        "000000001" WHEN (a = '0' and b = '0' and c = '0' and d = '1') ELSE
        "000000010" WHEN (a = '0' and b = '0' and c = '1' and d = '0') ELSE
        "000000011" WHEN (a = '0' and b = '0' and c = '1' and d = '1') ELSE
        "000001000" WHEN (a = '0' and b = '1' and c = '0' and d = '0') ELSE
        "000001001" WHEN (a = '0' and b = '1' and c = '0' and d = '1') ELSE
        "000100000" WHEN (a = '0' and b = '1' and c = '1' and d = '0') ELSE
        "001000000" WHEN (a = '0' and b = '1' and c = '1' and d = '1') ELSE
        "010000000" WHEN (a = '1' and b = '0' and c = '0' and d = '0') ELSE
        "100000000" WHEN (a = '1' and b = '0' and c = '0' and d = '1') ELSE
        "ZZZZZZZZZ";
end Behavioral;
    
```

- **LIBRARY declarations**
  - Contains a list of all libraries to be used in the design. (ex:ieee,std,work.etc)
- **ENTITY**
  - Specifies the I/O pins of the circuit
- **ARCHITECTURE**
  - Contains the VHDL code proper, which describes how the circuit should behave(function)

## ▶ VHDL structure


- LIBRARY declarations (like `stdio.h` in C language)
  - usually needed in a design
    - LIBRARY ieee;
      - USE `ieee.std_logic_1164.all;` ← *Semi-colon indicates the end of a statement declaration*
    - LIBRARY std;
      - USE `std.standard.all;`
    - LIBRARY work;
      - USE `work.all;`

## ▶ VHDL structure 1: Library Packages

- 'std\_logic\_1164' package
  - std\_logic (BIT)
  - std\_logic\_vector (MULTI-BITS)
  - integer
- 'numeric\_std' package
  - Mathematical operation & Signed/Unsigned
- 'textio' and 'std\_logic\_textio'
  - Used in testbench to write and read the data to the file
- Others
  - Fixed point & floating point...



# ► Data Type

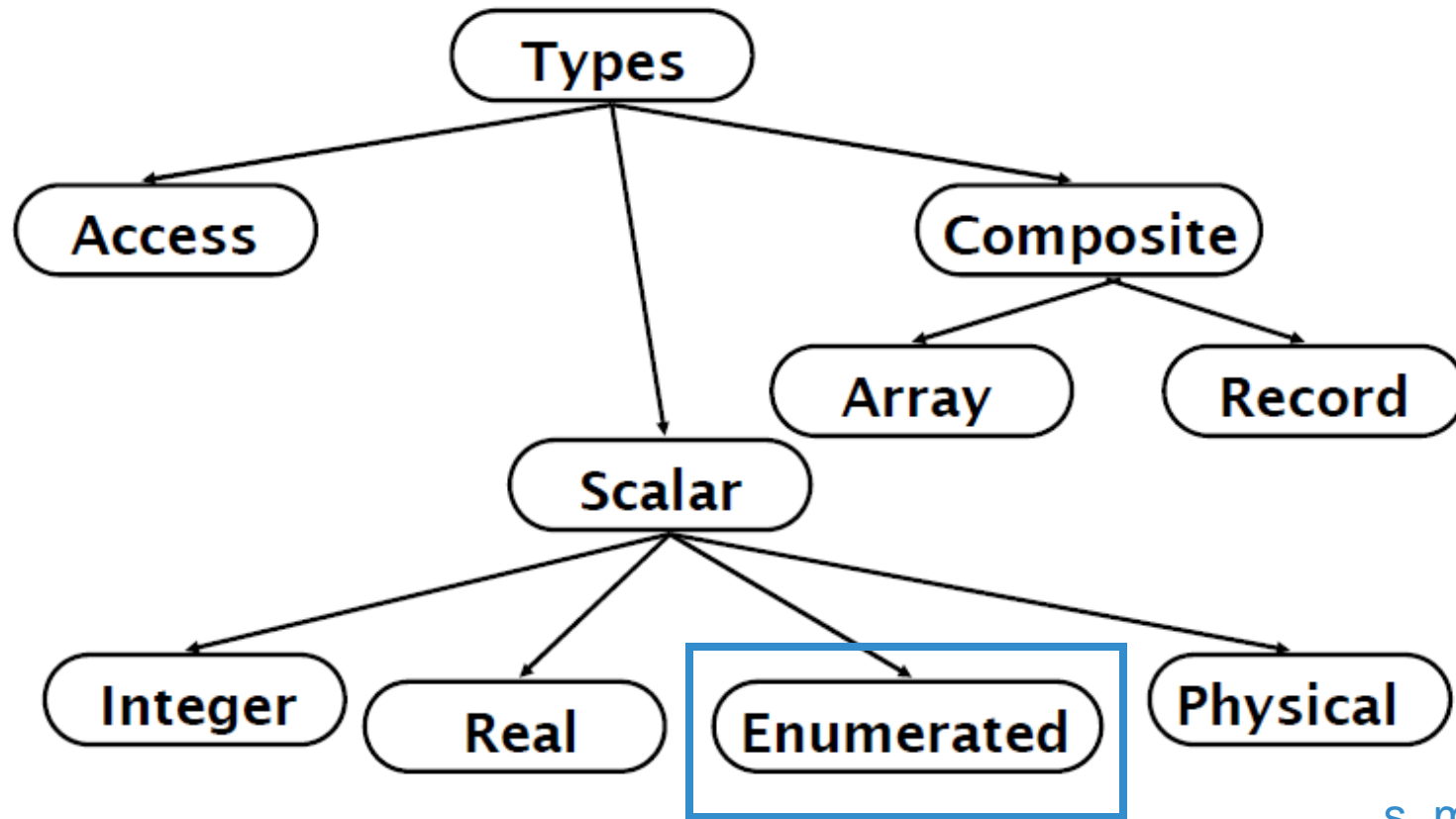

std\_logic/std\_logic\_vector  
boolean, bit, etc..

s, ms, us, ns, ps

## ► Enumerated type

- **type std\_logic is ( 'U', 'X', '0', '1', 'Z', 'W', 'L', 'H', '-' );** *Represent “Wire”*
  - 1: Logic 1
  - 0: Logic 0
  - U: Uninitialized
  - X: Unknown
  - Z: High-Z
  - W: Weak signal, (can't tell if 0 or 1)
  - L: Weak 0, pull down
  - H: Weak 1, pull up
  - -: Don't care
- **type std\_ulogic is ( 'U', 'X', '0', '1', 'Z', 'W', 'L', 'H', '-' );**
- **type state is (STATE1, STATE2, STATE 3,..);**
- **type boolean is (false,true); / type bit is ('0', '1');**

# ▶ std\_logic vs std\_logic\_vector

- std\_logic
  - 1 bit / 8 values

*Represent “Wire”*

- std\_logic\_vector
  - downto / to

**std\_logic\_vector(7 downto 0)**

A(7) MSB	A(6)	A(5)	A(4)	A(3)	A(2)	A(1)	A(0) LSB
-------------	------	------	------	------	------	------	-------------

**std\_logic\_vector(0 to 7)**

A(0) MSB	A(1)	A(2)	A(3)	A(4)	A(5)	A(6)	A(7) LSB
-------------	------	------	------	------	------	------	-------------

## ► Signal assignments

- constant a: integer := 523;
- signal b: std\_logic\_vector(11 downto 0);

b <= "000000010010";

b <= B"000000010010";

b <= B"0000\_0001\_0010";

b <= X"012";

b <= O"0022";

# ► Built-in operators

- Logic operators
  - AND, OR, NAND, NOR, XOR, XNOR (XNOR in VHDL'93 only!!)

- Relational operators

- =, /=, <, <=, >, >=

Operators	Means	Operators	Means
=	Equal to	/=	Not equal to
<	Less than	>	Greater than
<=	Less than or equal to	>=	Greater than or equal to

- Addition operators

- +, -, &

- Multiplication operators (DON'T USE IN THIS TERM PROJECT)

- \*, /, mod, rem

- Miscellaneous operators

- \*\*, abs, not



# ▶ Assign operators

- Assign a value a SIGNAL

$\leftarrow$

- Assign a value a VARIABLE, CONSTANT, or GENERIC, establishing initial values

$\therefore$

- Assign a values to individual vector elements or with OTHERS

$\Rightarrow$

# ▶ example


```

19 -----
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 use IEEE.STD_LOGIC_ARITH.ALL;
23 use IEEE.STD_LOGIC_UNSIGNED.ALL;
24
25 ---- Uncomment the following library declaration if ins
26 ---- any Xilinx primitives in this code.
27 --library UNISIM;
28 --use UNISIM.VComponents.all;
29
30 entity test1 is
31     Port ( m_a : in STD_LOGIC_VECTOR(3 downto 0);
32           m_b : in STD_LOGIC_VECTOR(3 downto 0);
33           m_c : in STD_LOGIC;
34           m_x : out STD_LOGIC_VECTOR(3 downto 0);
35           m_y : out STD_LOGIC_VECTOR(6 downto 0));
36 end test1;
37
38 architecture Behavioral of test1 is
39
40     signal s_tmp1 : std_logic_vector(3 downto 0);
41     signal s_tmp2 : std_logic;
42
43     begin
44
45         s_tmp1 <= m_a + m_b;
46         s_tmp2 <= not m_c;
47
48         m_y(6 downto 3) <= "0101"; -- or x"5"
49         m_y(2) <= s_tmp2 and s_tmp1(3);
50         m_y(1 downto 0) <= s_tmp1(3 downto 2);
51
52         m_x(3) <= '1';
53         m_x(2 downto 0) <= "010";
54
55     end Behavioral;
56
57

```
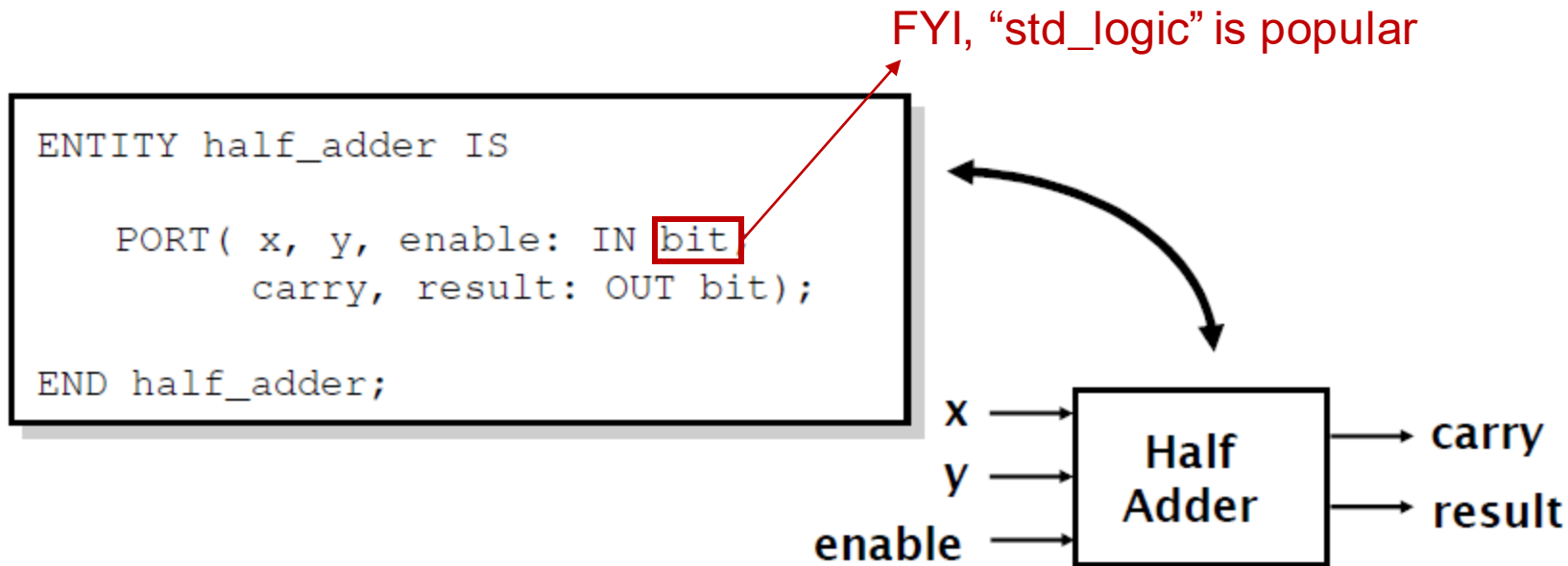
## ▶ VHDL structure 2: Entity Declaration

- An entity declaration describes the interface of the component.
- PORT clause indicates input and output ports.
- An entity can be thought of as a symbol for a component.




## ▶ VHDL structure 3: Port Declaration

- PORT declaration establishes the interface of the object to the outside world.
- Three parts of the PORT declaration
  - Name
    - Any identifier that is not a reserved word.
  - Mode
    - In, Out, Inout, Buffer
  - Data type
    - Any declared or predefined datatype.
- Sample PORT declaration syntax:

```
ENTITY test IS  
  PORT( name : mode data_type);  
END test;
```

 
```
ENTITY nand_gate IS  
  port (    x, y      : IN STD_LOGIC;  
          z          : OUT STD_LOGIC);  
END nand_gate;
```


 
## ▶ VHDL structure 4: Architecture Declaration

- Architecture declarations describe the operation of the component.
- Many architectures may exist for one entity, but only one may be active at a time.
- An architecture is similar to a schematic of the component.

```
ARCHITECTURE behave OF half_adder IS
BEGIN
  PROCESS (enable, x, y)
  BEGIN
    IF (enable = '1') THEN
      result <= x XOR y;
      carry  <= x AND y;
    ELSE
      carry  <= '0';
      result <= '0';
    END IF;
  END PROCESS;
END behave;
```






# ▶ VHDL code structure : example


```

15 -- Revision:
16 -- Revision 0.01 - File Created
17 -- Additional Comments:
18 --
19 -----
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 use IEEE.STD_LOGIC_ARITH.ALL;
23 use IEEE.STD_LOGIC_UNSIGNED.ALL;
24
25 ---- Uncomment the following library declaration if instantiating
26 ---- any Xilinx primitives in this code.
27 --library UNISIM;
28 --use UNISIM.VComponents.all;
29
30 entity test1 is
31     Port ( m_a : in STD_LOGIC;
32           m_b : in STD_LOGIC;
33           m_c : in STD_LOGIC;
34           m_y : out STD_LOGIC);
35 end test1;
36
37 architecture Behavioral of test1 is
38
39     signal s_tmp : std_logic;
40
41 begin
42
43     s_tmp <= not m_b;
44     m_y <= (m_a and s_tmp) or (m_b and m_c);
45
46 end Behavioral;
47
48

```

 

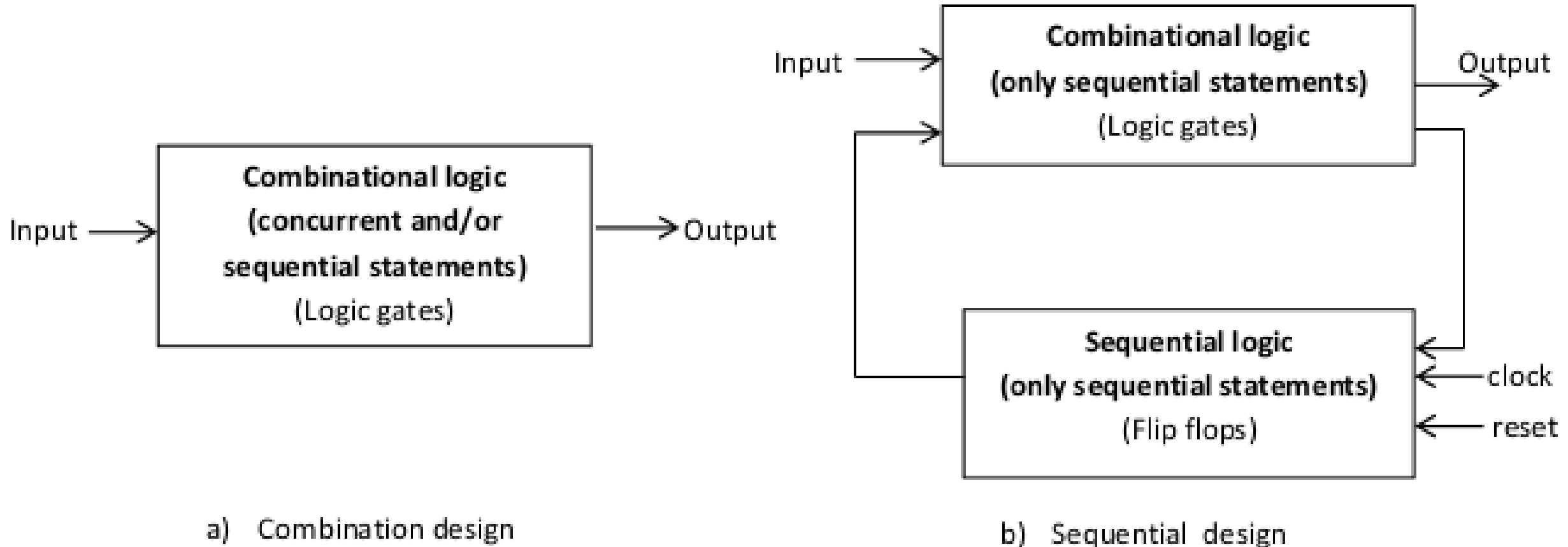
# ► Combinational logic vs Sequential Logic



 
# ► Modeling Styles

- There are three modeling styles:
  - Dataflow (Combinational)
    - LOGIC
  - Behavioral (Sequential)
    - Only PROCESS statement
  - Structural
    - Interconnection between components



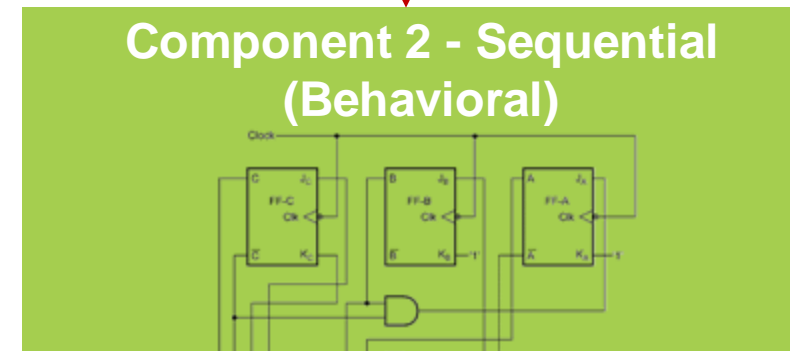**Structural**  
(components-interconnections)



# ► Modeling Styles

- Register-Transfer Level (RTL) Design
  - When designing digital integrated circuits with a HDL, the designs are usually engineered at a higher level of abstraction than transistor or logic gate level
  - But, a gate-level logic implementation (RTL design) is sometimes preferred.
  - This level describes the logic in terms of registers and the Boolean equations for the combinational logic between registers
  - For a combinational system there are no registers and the RTL logic consists only of combinational logic

# ► Modeling Styles


Design	Statement	VHDL
Sequential (Flip-flops and Logic gates)	Sequential statements only	if
		case
		loop
		wait
Combinational (Logic gates Only)	Concurrent and Sequential	not/and/or/nand/nor/xor/xnor
		when-else
		with-select
		generate

# ► Concurrent vs Sequential Statements in VHDL

- Two different types of execution: sequential and concurrent.
- Different types of execution are useful for modeling of real hardware.
  - Supports various levels of abstraction.
- Sequential statements view hardware from a “programmer” approach.
- Concurrent statements are order-independent and asynchronous.



 
## ▶ Example: XOR-gate in Sequential Style



```
process(a,b)
begin
    if (a/=b) then
        q <= '1';
    else
        q <= '0';
    end if;
end process;
```

## ► Example: XOR-gate in Dataflow Style

 


```
q <= a xor b;
```

Or in behavioral data flow style:


```
q <= '1' when a/=b else '0';
```
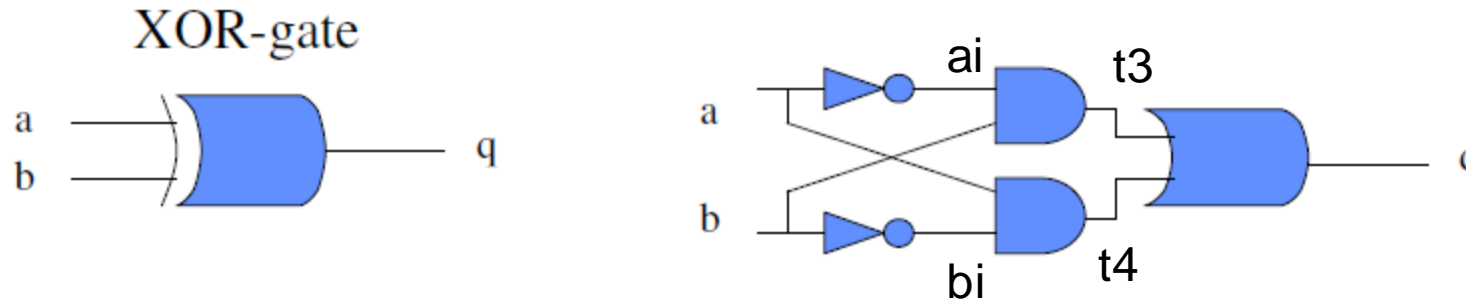
## ► Example: XOR-gate in Structural Style



```
u1: inverter port map (a, ai);  
u2: inverter port map (b, bi);  
u3: and_gate port map (ai, b, t3);  
u4: and_gate port map (bi, a, t4);  
u5: or_gate port map (t3, t4, q);
```
 
# ▶ Example: Half-adder in Sequential Style




```

1.  library ieee;
2.  use ieee.std_logic_1164.all;
3.
4.  entity half_adder is
5.    port (a, b: in std_logic;
6.          sum, carry_out: out std_logic);
7.  end half_adder;
8.
9.  architecture behavior of half_adder is
10.    begin
11.      ha: process (a, b)
12.      begin
13.        if a = '1' then
14.          sum <= not b;
15.          carry_out <= b;
16.        else
17.          sum <= b;
18.          carry_out <= '0';
19.        end if;
20.      end process ha;
21.    end behavior;
22.


```

## ▶ Example: XOR-gate in Dataflow Style

 

```
1. library ieee;
2. use ieee.std_logic_1164.all;
3.
4. entity half_adder is
5.     port (a, b: in std_logic;
6.           sum, carry_out: out std_logic);
7. end half_adder;
8.
9. architecture dataflow of half_adder is
10. begin
11.     sum <= a xor b;
12.     carry_out <= a and b;
13. end dataflow;
```
 
# ▶ Example: XOR-gate in Structural Style



```
1. u1: xor_gate port map (a, b, sum);
2. u2: and_gate port map (a, b, carry_out);
```

```
1. library ieee;
2. use ieee.std_logic_1164.all;
3.
4. entity half_adder is           -- Entity declaration for half adder
5.     port (a, b: in std_logic;
6.           sum, carry_out: out std_logic);
7. end half_adder;
8.
9. architecture structure of half_adder is -- Architecture body for half adder
10.
11.     component xor_gate           -- xor component declaration
12.         port (i1, i2: in std_logic;
13.              o1: out std_logic);
14.     end component;
15.
16.     component and_gate           -- and component declaration
17.         port (i1, i2: in std_logic;
18.              o1: out std_logic);
19.     end component;
20.
21. begin
22.     u1: xor_gate port map (i1 => a, i2 => b, o1 => sum);
23.     u2: and_gate port map (i1 => a, i2 => b, o1 => carry_out);
24. -- We can also use Positional Association
25. --     => u1: xor_gate port map (a, b, sum);
26. --     => u2: and_gate port map (a, b, carry_out);
27. end structure;
```



# ▶ Combinational: WHEN – Simple and Selected

- WHEN is a fundamental concurrent statements

- WHEN / ELSE – Simple WHEN

```
assignment WHEN condition ELSE
assignment WHEN condition ELSE
...;
```

- In WITH / SELECT / WHEN,
  - OTHERS, UNAFFECTED are often useful

Example:

```
----- With WHEN/ELSE -----
outp <= "000" WHEN (inp='0' OR reset='1') ELSE
      "001" WHEN ctl='1' ELSE
      "010";
```

```
---- With WITH/SELECT/WHEN -----
WITH control SELECT
  output <= "000" WHEN reset,
           "111" WHEN set,
           UNAFFECTED WHEN OTHERS;
```


# ▶ Combinational: WHEN – Simple and Selected

- Example: Multiplexer

```

1  ----- Solution 1: with WHEN/ELSE -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  ENTITY mux IS
6      PORT ( a, b, c, d: IN STD_LOGIC;
7              sel: IN STD_LOGIC_VECTOR (1 DOWNT0 0);
8              y: OUT STD_LOGIC);
9  END mux;
10 -----
11 ARCHITECTURE mux1 OF mux IS
12 BEGIN
13     y <=  a WHEN sel="00" ELSE
14           b WHEN sel="01" ELSE
15           c WHEN sel="10" ELSE
16           d;
17 END mux1;
18 -----

```

 


# ► Combinational: WHEN – Simple and Selected

## • Example: Encoder

```

1  ---- Solution 1: with WHEN/ELSE -----
2  LIBRARY ieee;
3  USE ieee.std_logic_1164.all;
4  -----
5  ENTITY encoder IS
6      PORT ( x: IN STD_LOGIC_VECTOR (7 DOWNT0 0);
7            y: OUT STD_LOGIC_VECTOR (2 DOWNT0 0));
8  END encoder;
9  -----
10 ARCHITECTURE encoder1 OF encoder IS
11 BEGIN
12     y <=    "000" WHEN x="00000001" ELSE
13            "001" WHEN x="00000010" ELSE
14            "010" WHEN x="00000100" ELSE
15            "011" WHEN x="00001000" ELSE
16            "100" WHEN x="00010000" ELSE
17            "101" WHEN x="00100000" ELSE
18            "110" WHEN x="01000000" ELSE
19            "111" WHEN x="10000000" ELSE
20            "ZZZ";
21 END encoder1;
22 -----

```

 

# ► Sequential Statements

- Sequentially Code are executed sequentially.
  - -With Sequential Code, We can build **Sequential Circuits** as well as **Combinational Circuits**.
  - -Allow only in **PROCESSES**, **FUNCTIONS**, and **PROCEDURES**.

# ▶ Sequential Statements

- Syntax

```

PROCESS(sensitivity_list)
    declarations;
BEGIN
    sequential statement;
    sequential statement;
    ...
END PROCESS;
    
```

- Sensitivity List

- It is a list of signals to which the process responds. (i.e., is “sensitive to”)
- If you put all input signals into the sensitivity list, a synthesizer will make it to combinational circuit. (**But, it's easy to make mistake. Don't recommend.**)
- For Synchronous design, put only “CLOCK” and “reset” (if you want to design asynchronous reset)

# ▶ Sequential Statements

- Example

```

34 entity top_test is
35     Port( reset : in std_logic;
36           clk : in std_logic;
37           en : in std_logic;
38           cnt_val : out std_logic_vector(3 downto 0));
39 end top_test;
40
41 architecture Behavioral of top_test is
42
43     signal s_cntval : std_logic_vector(3 downto 0);
44
45 begin
46
47     process(reset, clk)
48     begin
49         if reset='0' then
50             s_cntval <= "0000";
51         elsif rising_edge(clk) then
52             if en='1' then
53                 s_cntval <= s_cntval + '1';
54             end if;
55         end if;
56     end process;
57
58     cnt_val <= s_cntval;
59
60 end Behavioral;
61

```

**Synchronous Design (+ Asynchronous Reset)**

# ► Sequential Statements 1: IF

## Syntax

```
IF conditions THEN assignments;  
ELSIF conditions THEN assignments;  
...  
ELSE assignments;  
END IF;
```

## Example

```
IF (x<y) THEN temp <="11111111";  
ELSIF (x=y AND w='0') THEN temp <="11110000";  
ELSE temp <=(OTHERS =>'0');
```



# ► Sequential Statements 2: CASE

## Syntax

```
CASE identifier IS  
  WHEN value => assignments;  
  WHEN value => assignments;  
  ...  
END CASE;
```

## Example

```
CASE control IS  
  WHEN "00" => x<=a; y<=b;  
  WHEN "01" => x<=b; y<=c;  
  WHEN OTHERS => x<="0000"; y<="ZZZZ";  
END CASE;
```

## ▶ Sequential Statements 2: CASE vs IF

- STATEMENT Type
  - CASE : Concurrent Code
  - IF : Sequential Code
- The IF/ELSE statement might infer the construction of an unnecessary priority decoder. (which would never occur with CASE)
  - > It cause NEGATIVE CONSEQUENCE.!

## ► Sequential Statements 2: CASE vs IF

**Example** – The Codes below implement the ~~same~~ circuit.  
**similar**

```
CASE sel IS
  WHEN "00" => x<=a;
  WHEN "01" => x<=b;
  WHEN "10" => x<=c;
  WHEN OTHERS => x<=d;
END CASE;
```

**No priority**

```
IF (sel="00") THEN x<=a;
ELSIF (sel="01") THEN x<=b;
ELSIF (sel="10") THEN x<=c;
ELSE x<=d;
END IF;
```

**1<sup>st</sup> priority**



**Last priority**

## ► Sequential Statements 2: CASE vs WHEN

	WHEN	CASE
Statement type	Concurrent	Sequential
Usage	Only outside PROCESSES, FUNCTIONS or PROCEDURES	Only inside PROCESSES, FUNCTIONS or PROCEDURES
All permutations must be tested	Yes for WITH/SELECT/WHEN	Yes
Max # of Assignments per test	1	Any
No-Action Key-Word	UNAFECTED	NULL

## ► Sequential Statements 2: CASE vs WHEN

**Example** – Equiv. Code from a **functional** point of view.

```
CASE sel IS
  WHEN "000" => x<=a;
  WHEN "001" => x<=b;
  WHEN "010" => x<=c;
  WHEN OTHERS => NULL;
END CASE;
```

```
WITH sel SELECT
  x <= a WHEN "000",
    b WHEN "001",
    c WHEN "010",
  UNAFFECTED WHEN OTHERS;
```

# ▶ Sequential Statements 3: WAIT (for testbench)

## Syntax

```
PROCESS // No Sensitivity List!
...
WAIT UNTIL signal_condition;
WAIT ON signal1 [, signal2, ... ];
WAIT FOR time;
```

- For use WAIT statement, **No Sensitivity List**.
- **WAIT UNTIL** : accepts only one signal.
- **WAIT ON** : accept multiple signal.
- **WAIT FOR** : waiting for specific time. ( simulation only. )

## Example.

- **WAIT UNTIL** : WAIT UNTIL (clk'EVENT AND clk='1')
- **WAIT ON** : WAIT ON clk, rst;
- **WAIT FOR** : WAIT FOR 5ns;

# ▶ Sequential Statements Example: Flip-flop


```

34 entity top_test is
35     Port( reset : in std_logic;
36           clk : in std_logic;
37           en : in std_logic;
38           din : in std_logic_vector(3 downto 0);
39           dout : out std_logic_vector(3 downto 0));
40 end top_test;
41
42 architecture Behavioral of top_test is
43
44 begin
45
46 process(reset, clk)
47 begin
48     if reset='0' then
49         dout <= "0000";
50     elsif rising_edge(clk) then
51         if en='1' then
52             dout <= din;
53         end if;
54     end if;
55 end process;
56
57 end Behavioral;

```

# ▶ State Machine Example: (Moore)

## State Machine

 

## Declaration

```

ENTITY state_machine IS
  PORT(
    clk      : IN  STD_LOGIC;
    input    : IN  STD_LOGIC;
    reset    : IN  STD_LOGIC;
    output   : OUT STD_LOGIC_VECTOR(1 downto 0));
END state_machine;

ARCHITECTURE a OF state_machine IS
  TYPE STATE_TYPE IS (s0, s1, s2);
  SIGNAL state : STATE_TYPE;

```

```

BEGIN
  PROCESS (clk, reset)
  BEGIN
    IF reset = '1' THEN
      state <= s0;
    ELSIF (clk'EVENT AND clk = '1') THEN
      CASE state IS
        WHEN s0=>
          IF input = '1' THEN
            state <= s1;
          ELSE
            state <= s0;
          END IF;
        WHEN s1=>
          IF input = '1' THEN
            state <= s2;
          ELSE
            state <= s1;
          END IF;
        WHEN s2=>
          IF input = '1' THEN
            state <= s0;
          ELSE
            state <= s2;
          END IF;
      END CASE;
    END IF;
  END PROCESS;

```

## Output Decoder

```



PROCESS (state)
BEGIN
  CASE state IS
    WHEN s0 =>
      output <= "00";
    WHEN s1 =>
      output <= "01";
    WHEN s2 =>
      output <= "10";
  END CASE;
END PROCESS;

END a;

```



# ▶ Example : Mealy Machine

 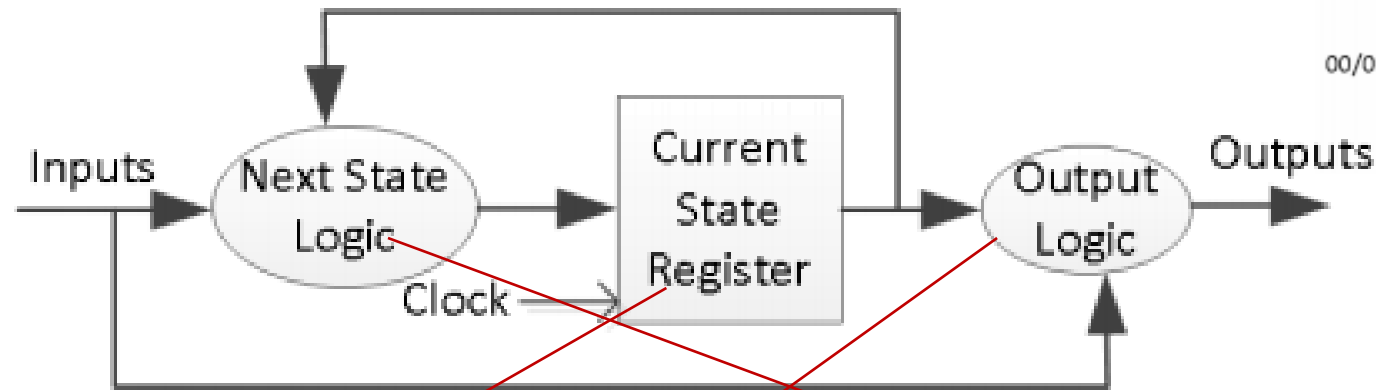

```
type state_type is (S0, S1);
signal state, next_state : state_type begin
```

```
begin
```

```
SYNC_PROC : process (clk)
begin
```

```
    if rising_edge(clk) then
        if (reset = '1') then
            state <= S0;
        else
            state <= next_state
        end if;
    end if;
end process;
```



```
OUTPUT_DECODE : process (state, x)
```

```
    parity <= '0';
    case (state) is
        when S0 =>
            if (x = '1') then
                parity <= '1';
            end if;
        when S1 =>
            if (x = '0') then
                parity <= '1';
            end if;
        when others =>
            parity <= '0';
        end case;
end process;
```

```
NEXT_STATE_DECODE : process (state, x)
begin
```

```
    next_state <= S0;
    case (state) is
        when S0 =>
            if (x = '1') then
                next_state <= S1;
            end if;
        when S1 =>
            if (x = '0') then
                next_state <= S1;
            end if;
        when others =>
            next_state <= S0;
        end case;
end process;
```

# ▶ Example : Moore Machine

 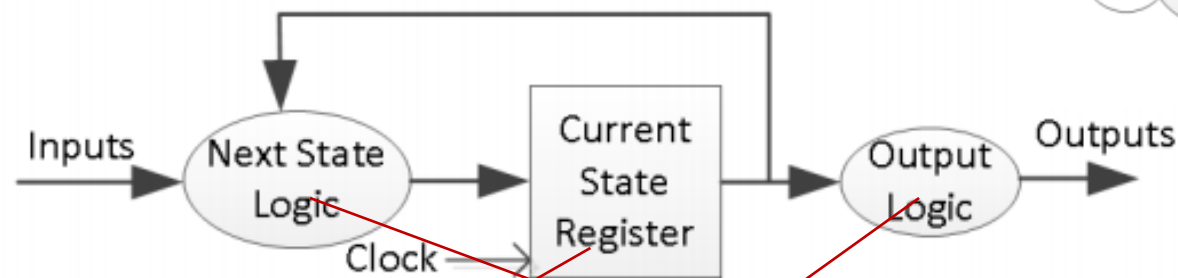

```

type state_type is (S0, S1);
signal state, next_state : state_type;

```

```
begin
```

```

SYNC_PROC : process (clk)
begin

```

```

    if rising_edge(clk) then
        if (reset = '1') then
            state <= S0;
        else
            state <= next_state;
        end if;
    end if;
end process;

```

```

OUTPUT_DECODE : process (state)
begin

```

```

    case (state) is
        when S0 =>
            parity <= '0';
        when S1 =>
            parity <= '1';
        when others =>
            parity <= '0';
    end case;
end process;

```

```

NEXT_STATE_DECODE : process (state, x)
begin


```

```

    next_state <= S0;
    case (state) is
        when S0 =>
            if (x = '1') then
                next_state <= S1;
            end if;
        when S1 =>
            if (x = '0') then
                next_state <= S1;
            end if;
        when others =>
            next_state <= S0;
    end case;
end process;

```

# ▶ Testbenches

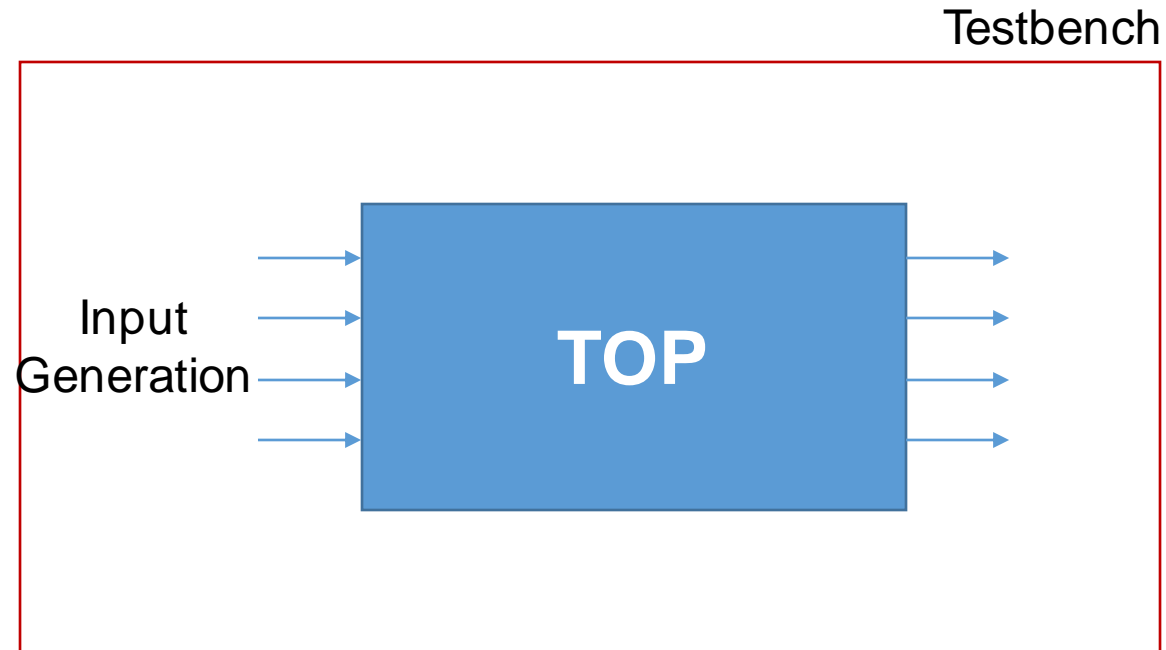

# ▶ Testbenches

```

35 ENTITY tb_lat4 IS
36 END tb_lat4;
37
38 ARCHITECTURE behavior OF tb_lat4 IS
39
40     -- Component Declaration for the Unit Under Test (UUT)
41
42     COMPONENT lat4
43     PORT(
44         reset : IN  std_logic;
45         clk   : IN  std_logic;
46         en    : IN  std_logic;
47         din   : IN  std_logic_vector(3 downto 0);
48         dout  : OUT std_logic_vector(3 downto 0)
49     );
50     END COMPONENT;
51
52
53     --Inputs
54     signal reset : std_logic := '0';
55     signal clk   : std_logic := '0';
56     signal en    : std_logic := '0';
57     signal din   : std_logic_vector(3 downto 0) := (others => '0');
58
59     --Outputs
60     signal dout : std_logic_vector(3 downto 0);
61
62     -- Clock period definitions
63     constant clk_period : time := 10 ns;
64
65 BEGIN
66
67     -- Instantiate the Unit Under Test (UUT)
68     uut: lat4 PORT MAP (
69         reset => reset,
70         clk   => clk,
71         en    => en,
72         din   => din,
73         dout  => dout
74     );
75
76

```

Initial values

```

75
76 -- Clock process definitions
77 clk_process :process
78 begin
79     clk <= '0';
80     wait for clk_period/2;
81     clk <= '1';
82     wait for clk_period/2;
83 end process;
84
85
86 -- Stimulus process
87 stim_proc: process
88 begin
89     -- hold reset state for 100 ns
90     wait for 100 ns;
91
92     reset <= '1';
93     wait for 50 ns;
94     din <= "0101";
95     en <= '1';
96
97     wait for 50 ns;
98     din <= "1010";
99
100    wait for 50 ns;
101    en <= '0';
102    din <= "0110";
103
104    wait for clk_period*10;
105
106    -- insert stimulus here
107
108    wait;
109 end process;
110
111 END;
112

```

Clock generation

Input timing control


Input

# Testbenches - Simulation

```

62  -- Clock period definitions
63  constant clk_period : time := 10 ns;
64
65
66
67  -- Clock process definitions
68  clk_process :process
69  begin
70      clk <= '0';
71      wait for clk_period/2;
72      clk <= '1';
73      wait for clk_period/2;
74  end process;
75
76
77  -- Stimulus process
78  stim_proc: process
79  begin
80      -- hold reset state for 100 ns.
81      wait for 100 ns;
82
83      reset <= '1';
84      wait for 50 ns;
85      din <= "0101";
86      en <= '1';
87
88      wait for 50 ns;
89      din <= "1010";
90
91      wait for 50 ns;
92      en <= '0';
93      din <= "0110";
94
95      wait for clk_period*10;
96
97      -- insert stimulus here
98
99      wait;
100  end process;
101
102  END;
103
104

```

 

## ► Helpful websites

### FPGA designs with VHDL

- <https://vhdlguide.readthedocs.io/en/latest/index.html>

### VHDL Tutorial, University of Pennsylvania (Jan Van der Spiegel)

- [https://www.seas.upenn.edu/~ese171/vhdl/vhdl\\_primer.html](https://www.seas.upenn.edu/~ese171/vhdl/vhdl_primer.html)