

Digital Logic Circuit (SE273 – Fall 2020)

Lecture 9: Registers and Counters

Jaesok Yu, Ph.D. (jaesok.yu@dgist.ac.kr)

Assistant Professor
Department of Robotics Engineering, DGIST

► Goal of this lecture

- Learn different types of clocked sequential circuits
 - Registers
 - Counters
- Learn practical implementations of registers and counters
 - Design procedure for registers or counters
 - Design different types of counters in Verilog


Registers

► Clocked Sequential Circuit

- It consists of a group of FFs and combinational gates
 - A circuit w/ FFs is a sequential circuit even w/o combinational gates
- Circuits with FFs are usually classified by the function
 - **Register:** a group of FFs that shares a common clock
 - A n-bit register consists of a group of n FFs capable of storing n bits of binary information
 - A register may have combinational gates that perform certain data-processing


► Simplest Register

 - Consider a four-bit data storage register
 - It consists of only flip-flops
 - Clock triggers all FFs on **positive edge**
 - (I_3, I_2, I_1, I_0) immediately before the clock edge determines (A_3, A_2, A_1, A_0) after the clock edge
- *Clear_b*: **active-low R** (reset), asynchronous reset
- It must be at logic 1 during normal clocked operation




► Register with Parallel Load

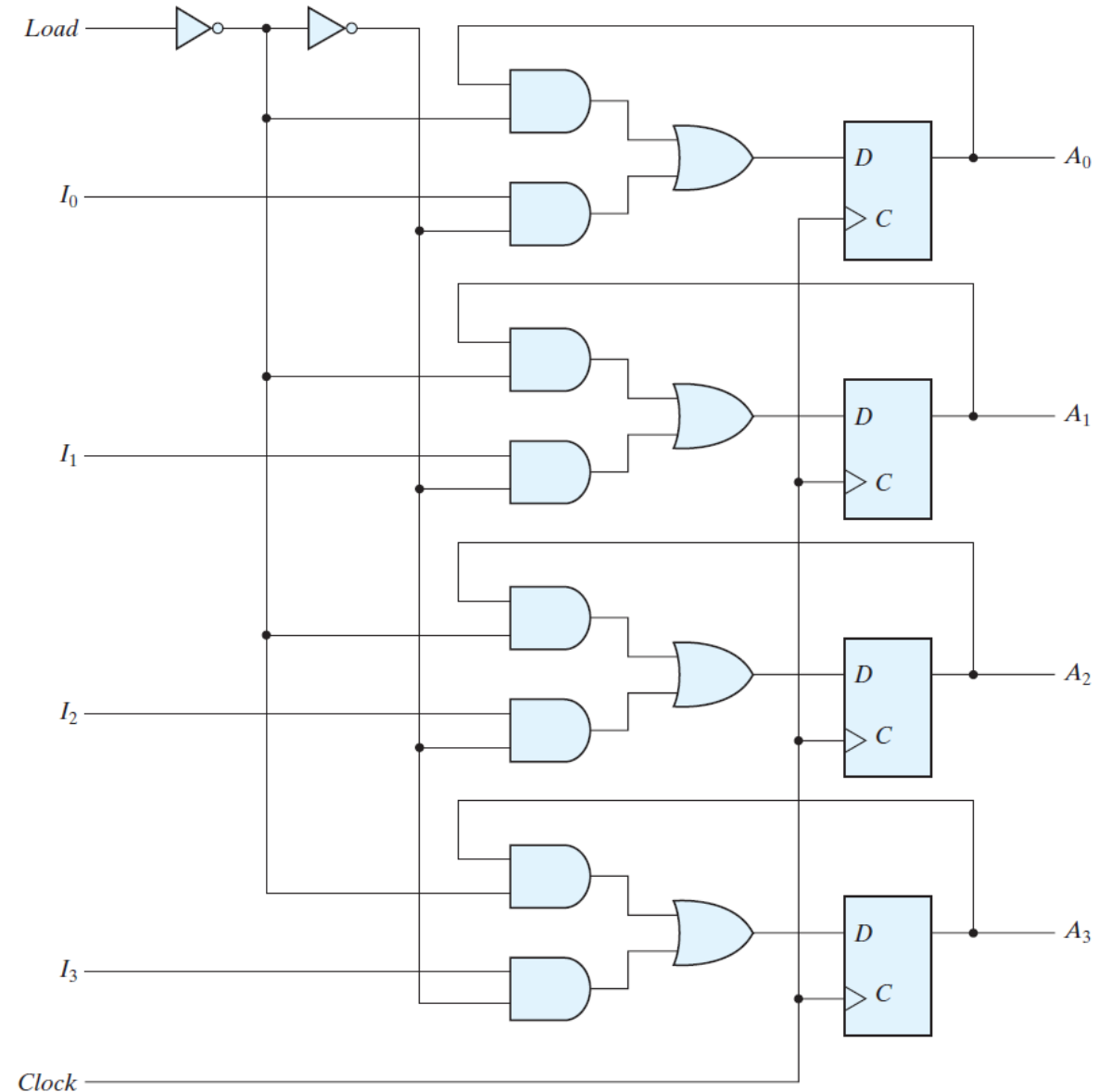- Registers w/ parallel load are a fundamental building block in digital systems
 - Transfer of new information into a register is referred to as **loading** or **updating** the register
 - Parallel load?




► Register with Parallel Load

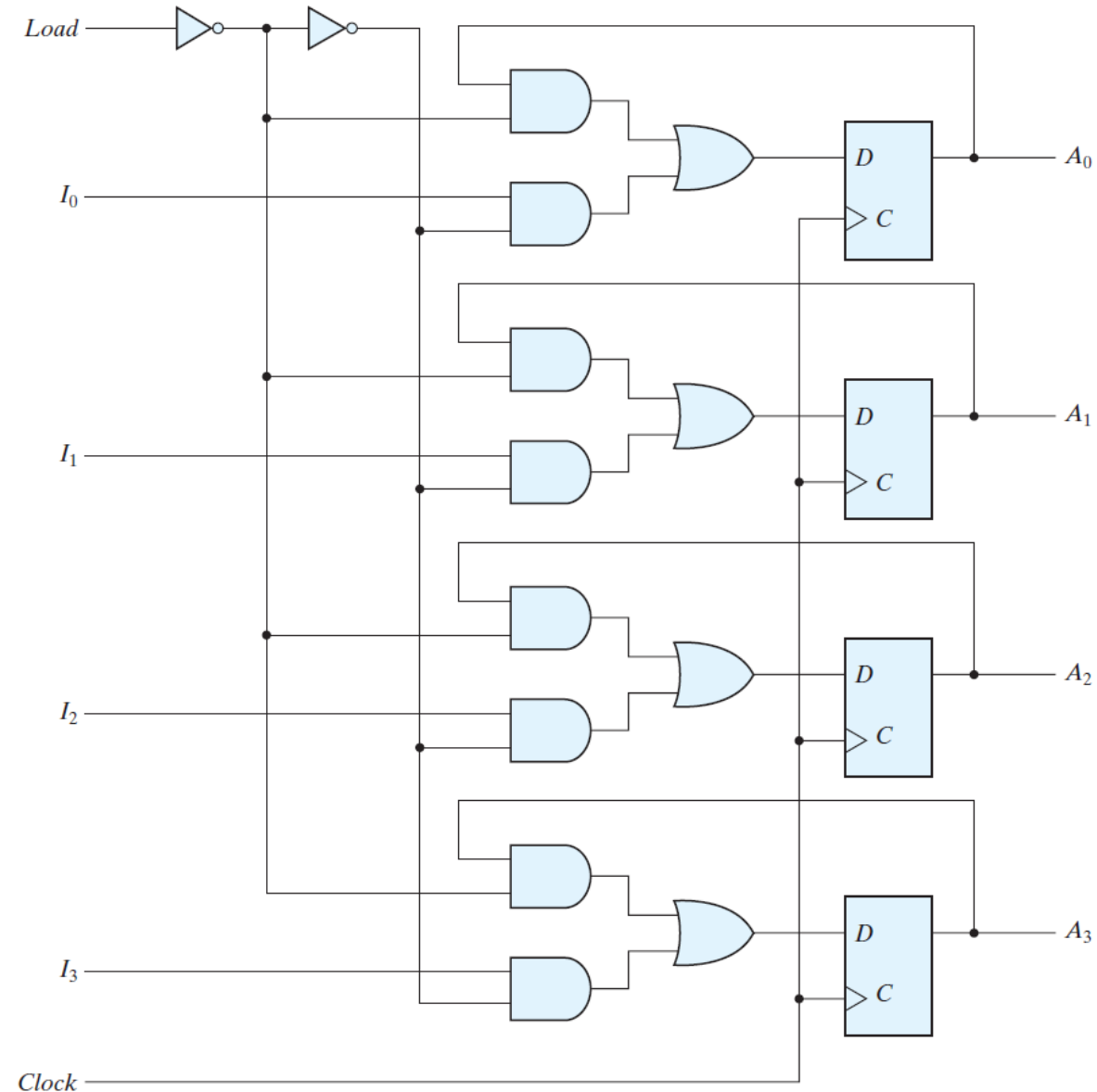- If the contents of the register must be left unchanged...
 - Inputs must be held constant, OR
 - Clock must be inhibited from the circuit
- Inserting gates into clock path is **ill advised** as it may produce **uneven propagation delays** btw the master clock and the inputs of FFs




► Shift Register

 - A register capable of shifting the binary information held in each cell to its neighboring cell, in a selected direction
 - Logical configuration: a chain of flip-flops in cascade
 - All FFs receive common clock pulses: activating the shift of data from one stage to the next



► (Unidirectional) Shift Register

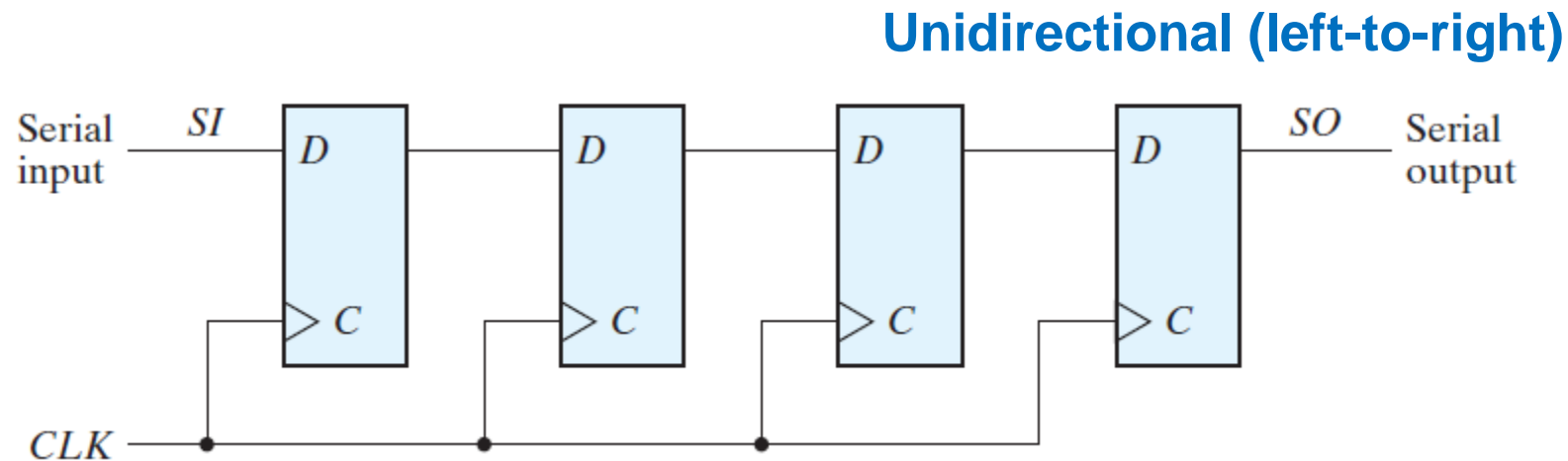- This configuration does not support a left shift
 - The **serial output** is taken from the output of the rightmost FF
 - Sometimes it is necessary to control the shift so that it occurs only w/ certain pulses (how?)




► Serial Transfer

- The datapath of a digital system is said to operate in serial mode
 - When information is transferred and manipulated one bit at a time
 - Transfer by shifting a bit **out of source register** and **into destination register**
- This type of transfer is **in contrast to parallel transfer**, whereby all the bits of the register are transferred at the same time.


▶ Block Diagram of Serial Transfer

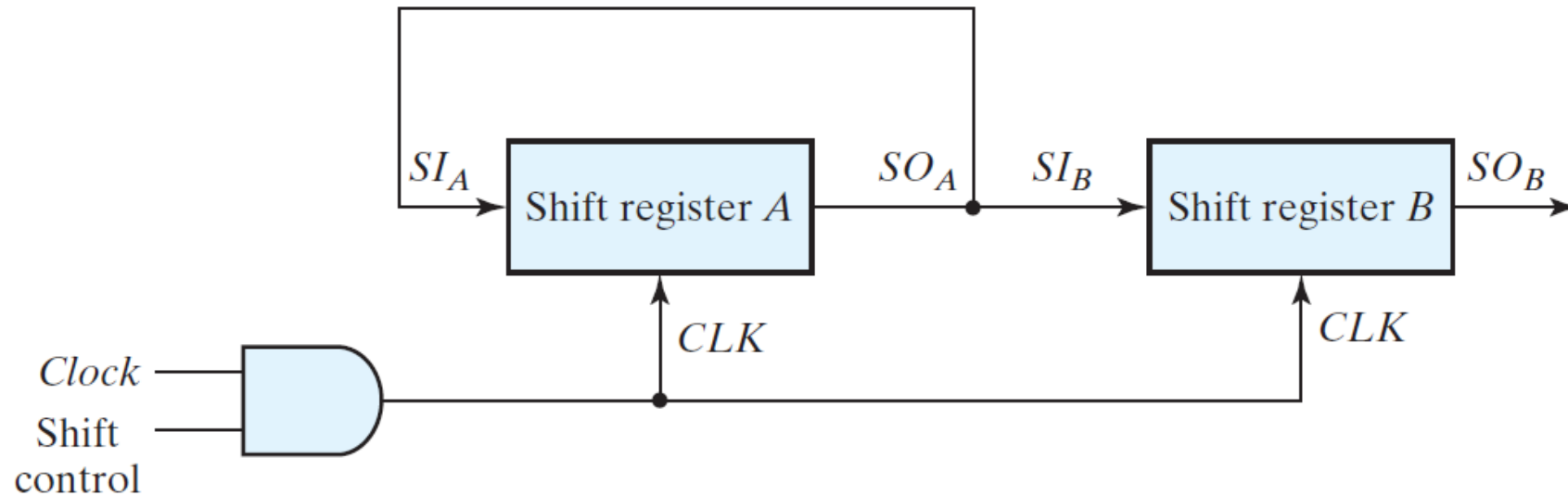- To prevent the loss of information stored in the source register
 - The information in register A is **circulated back to** its serial input
 - Initial content of register B is shifted out through its serial output and is lost




► Shift Control in Serial Transfer

 - The shift control input determines when and how many times the registers are shifted
 - Done with **an AND gate allowing clock pulses to pass** into CLK terminals
 - Note that this practice can be problematic (compromising clock path)




► Four-bit Shift Register

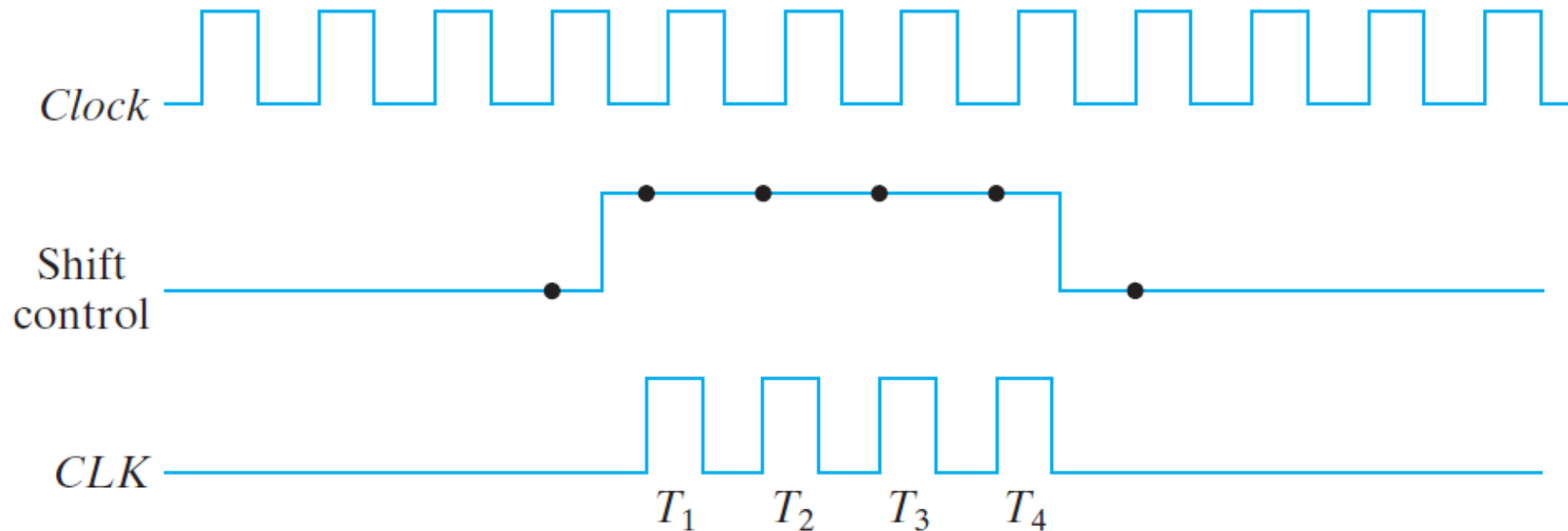- The control unit supervises the transfer for a fixed time of four clock pulses to pass an entire word
 - The shift control signal is synchronized w/ clock and changes value just after the negative edge of the clock



► Four-bit Shift Register

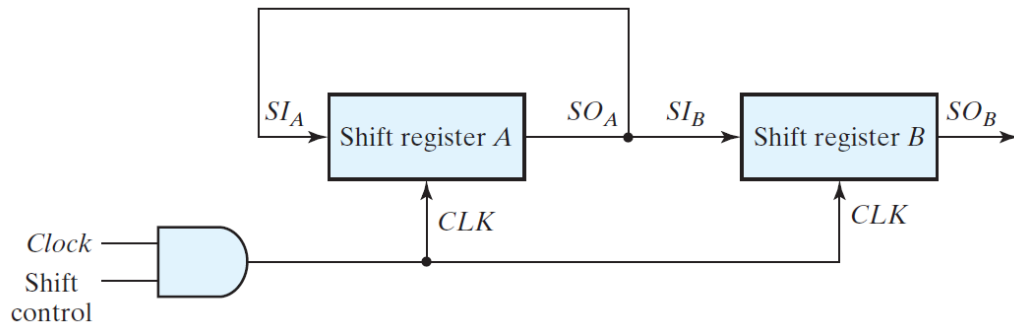- Assume that the binary content of A is 1011 and that of B is 0010
 - The rightmost bit of A is shifted into the leftmost bit of B
 - Also, it is circulated into the leftmost position of A
 - The previous serial output from B is lost



Timing Pulse	Shift Register A				Shift Register B			
Initial value	1	0	1	1	0	0	1	0
After T_1	1	1	0	1	1	0	0	1
After T_2	1	1	1	0	1	1	0	0
After T_3	0	1	1	1	0	1	1	0
After T_4	1	0	1	1	1	0	1	1

▶ 64-bits Shift Register in VHDL

```

begin
    process (clk)
    begin
        if (rising_edge(clk)) then
            if (enable = '1') then

                -- Shift data by one stage; data from last stage is lost
                sr(63 downto 1) <= sr(62 downto 0);

                -- Load new data into the first stage
                sr(0) <= sr_in;

            end if;
        end if;
    end process;

    -- Capture the data from the last stage, before it is lost
    sr_out <= sr(63);
end rtl;

```


► Serial Operations

- Operations in digital computers are usually done in parallel
 - For a faster mode of operation
 - Serial operations are slower as they require several clock cycles

► Serial Addition


• Let's look at a serial adder for an example

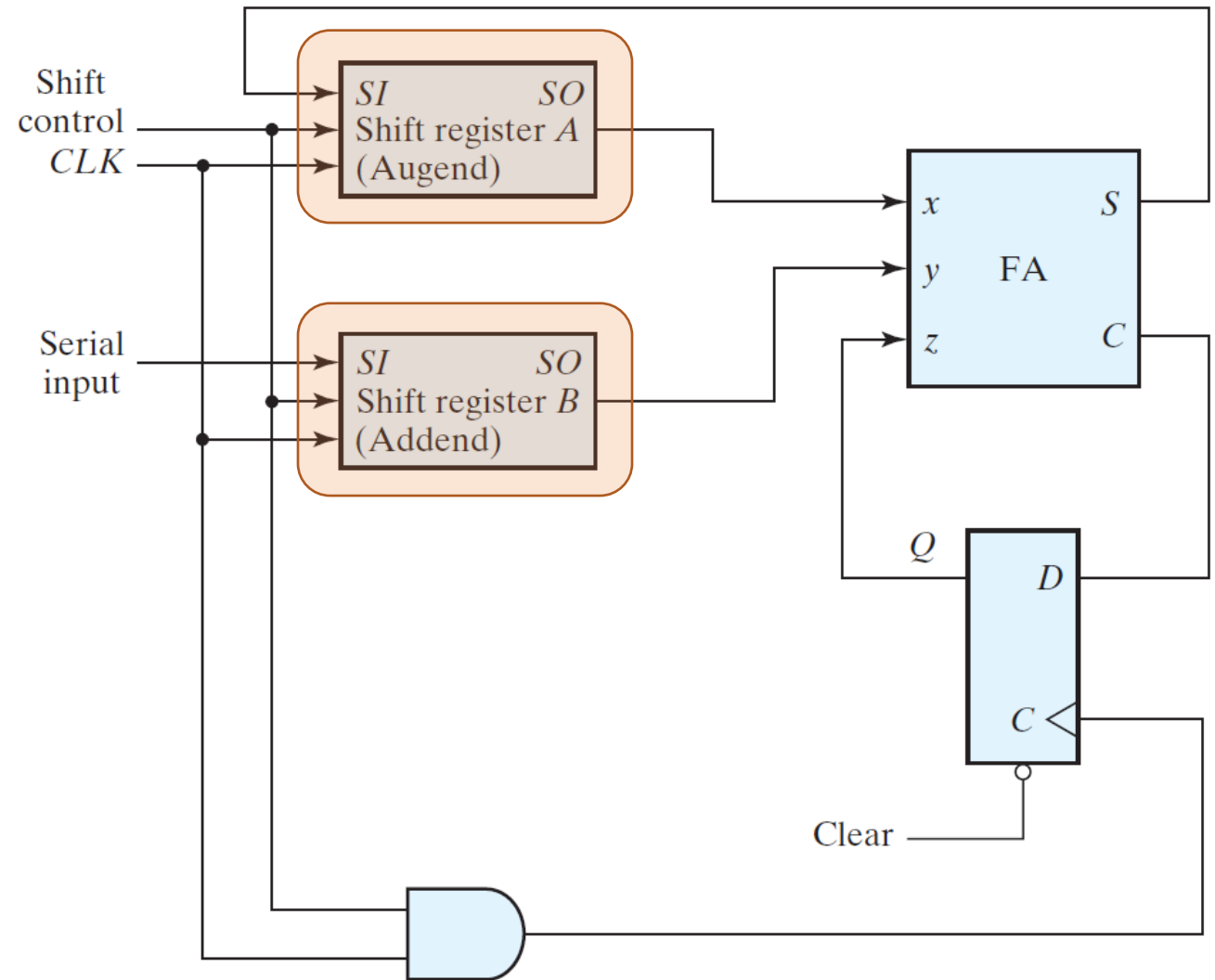- Two binary numbers are added serially
- These operands are stored in two **shift registers**




Serial Addition

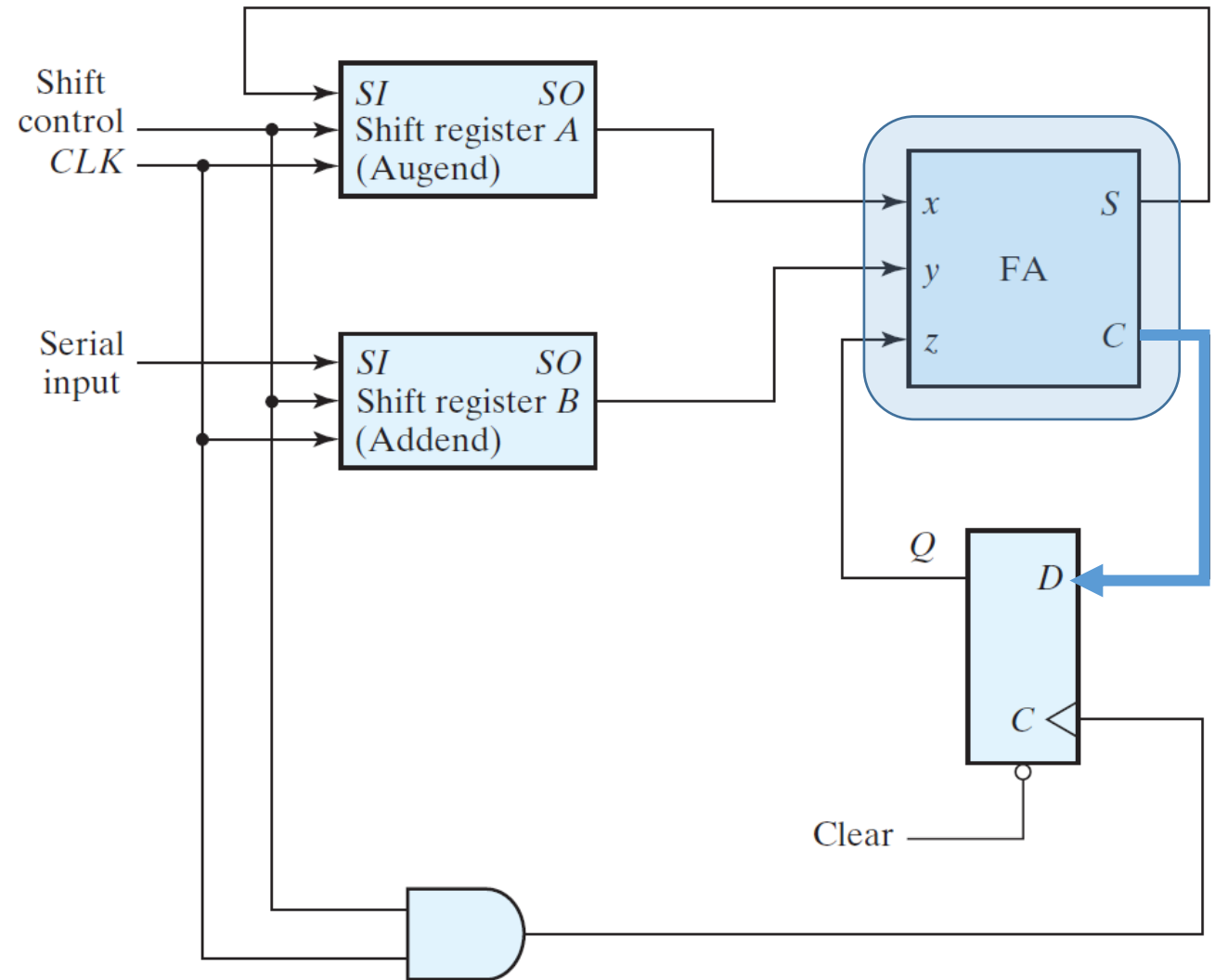- Beginning w/ the least significant pair of bits
 - A single full adder (FA) adds one pair at a time
 - The **carry out is transferred to a D FF**, then used as a carry input for the next pair



Serial Addition

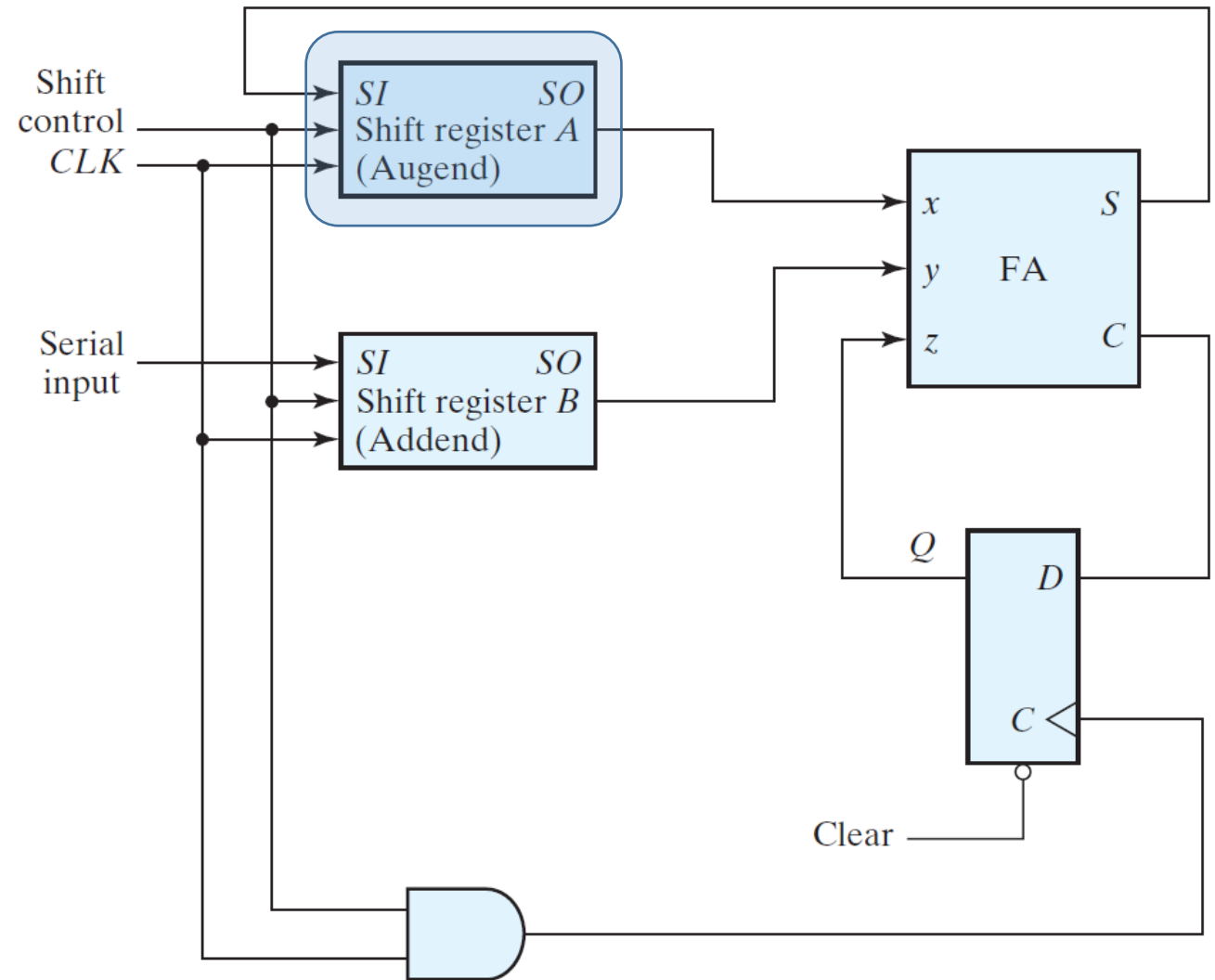
- Beginning w/ the least significant pair of bits
 - A single full adder (FA) adds one pair at a time
 - The **carry out is transferred to a D FF**, then used as a carry input for the next pair
- By shifting sum into A while the bits of A are shifted out, we can **save the additional output register**



Serial Addition

- The shift control enables both registers and D FF
 - After enabled, a bit pair is shifted once to the right
 - The sum bit from S enters the leftmost flip-flop of A
 - The output carry is transferred into flip-flop Q

Until the shift control is disabled!

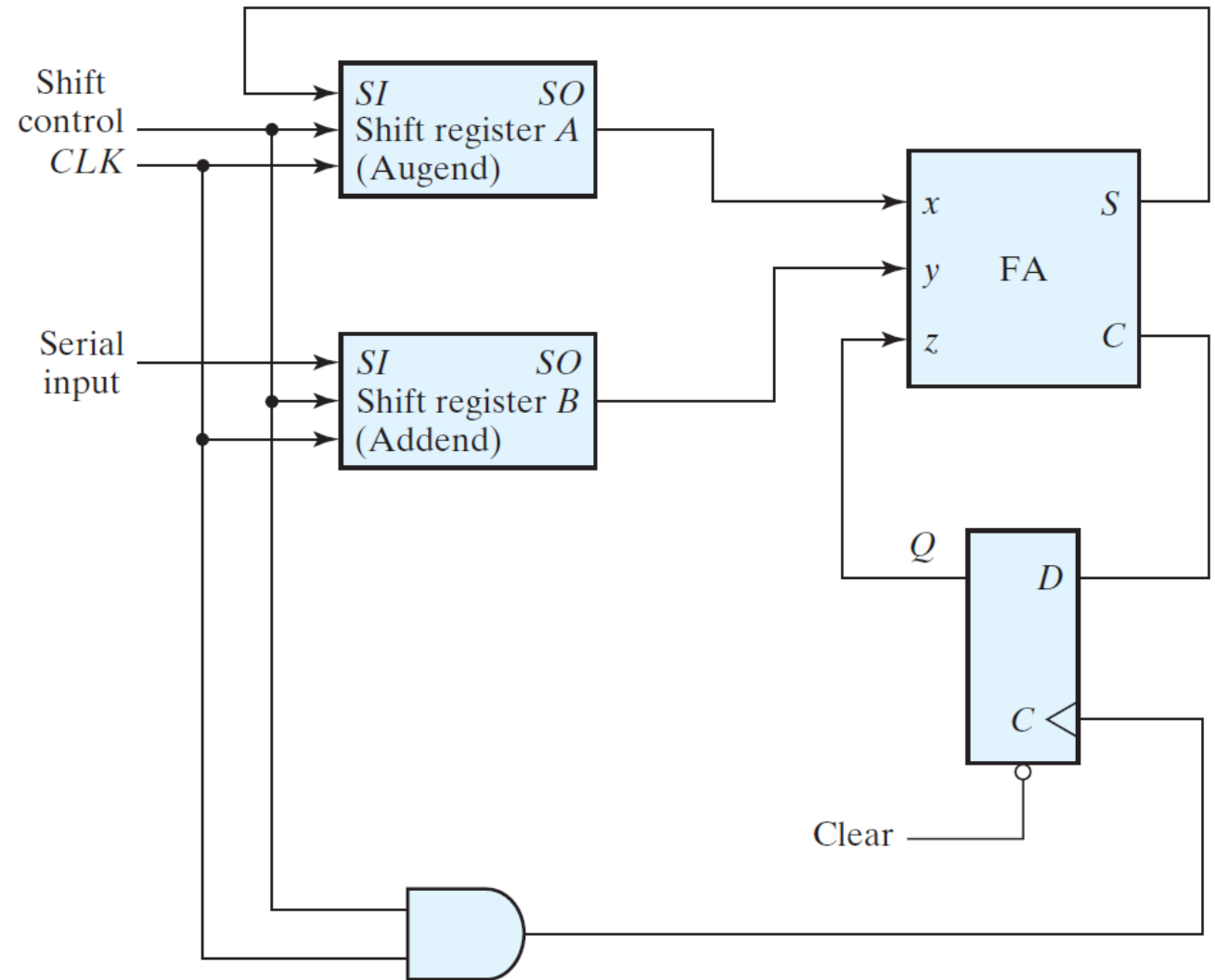

► Serial Adder vs. Parallel Adder

- The parallel adder
 - Uses registers w/ parallel load
 - # of FAs = # of bits to be added
- The serial adder
 - Uses shift registers
 - Requires only one FA + **carry flip-flop**

**Sequential circuit can be described
by a state table**

► State Table for Serial Adder

- Two shift registers are available to store the binary numbers to be added serially
 - The serial outputs from the registers are designated by x and y

Present State	Inputs		Next State	Output	Flip-Flop Inputs	
	<i>x</i>	<i>y</i>	<i>Q</i>	<i>S</i>	<i>J_Q</i>	<i>K_Q</i>
0	0	0	0	0	0	X
0	0	1	0	1	0	X
0	1	0	0	1	0	X
0	1	1	1	0	1	X
1	0	0	0	1	X	1
1	0	1	1	0	X	0
1	1	0	1	0	X	0
1	1	1	1	1	X	0


► State Table for Serial Adder

- Two inputs x and y provide a pair of significant bits, an output S generates the sum bit, and FF Q for storing the carry
 - The present state Q is the input to carry-in (added together w/ x and y)

Present State Q	Inputs $x \quad y$		Next State Q	Output S	Flip-Flop Inputs	
					J_Q	K_Q
0	0	0	0	0	0	X
0	0	1	0	1	0	X
0	1	0	0	1	0	X
0	1	1	1	0	1	X
1	0	0	0	1	X	1
1	0	1	1	0	X	0
1	1	0	1	0	X	0
1	1	1	1	1	X	0


► Universal Shift Register

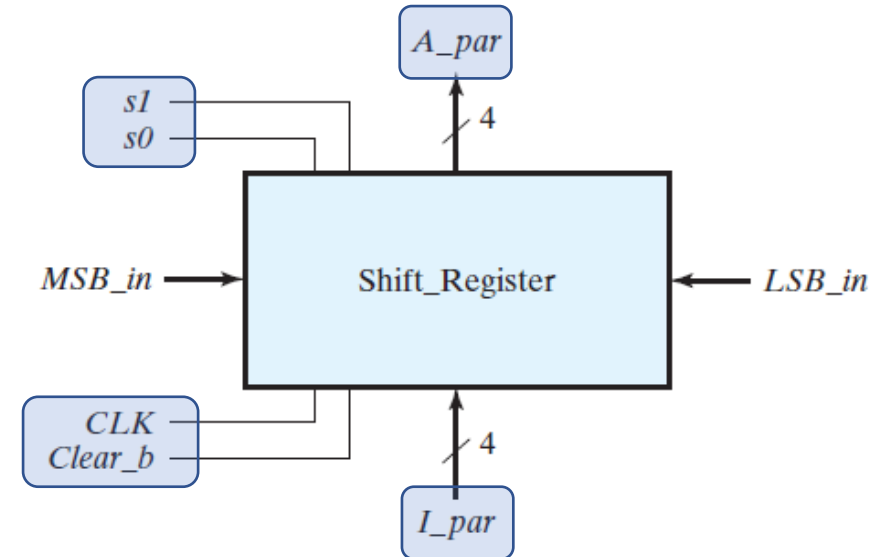- Some shift registers provide necessary input and output terminals for parallel transfer
 - If FF **outputs of a shift register are accessible**, then information entered serially by shifting can be **taken out in parallel**
 - If a **parallel load capability** is available in a shift register, then data entered in parallel can be **taken out in serial** fashion




► 4-bit Universal Shift Register

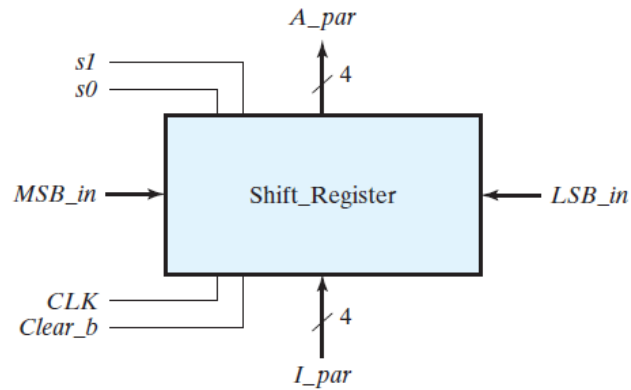- Universal: bidirectional shift + parallel-load



Mode Control		Register Operation
s_1	s_0	

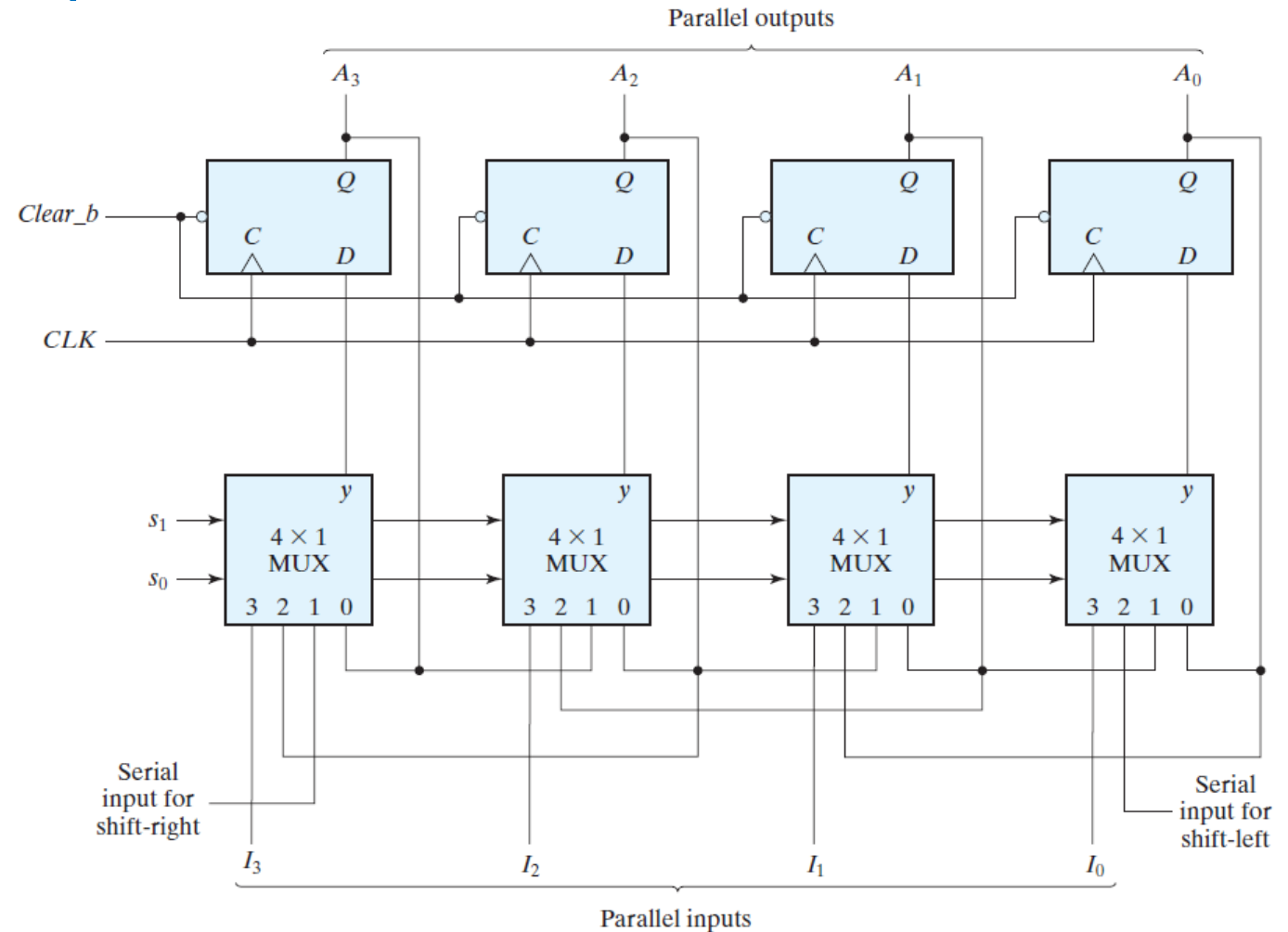

Registers

► Clocked Sequential Circuit



- It consists of a group of FFs and combinational gates
 - A circuit w/ FFs is a sequential circuit even w/o combinational gates
- Circuits with FFs are usually classified by the function
 - **Counter**: a register that goes into a **predetermined sequence of binary states**
 - Gates are connected in a way to produce the prescribed sequence of states
 - Counters are a special type of register

► Binary Counter

- A counter that follows the binary number sequence
 - 'n' flip-flops can count in binary from 0 to 2^n-1
- There are two categories
 - Ripple counters
 - Synchronous counters

▶ Binary Ripple Counter

 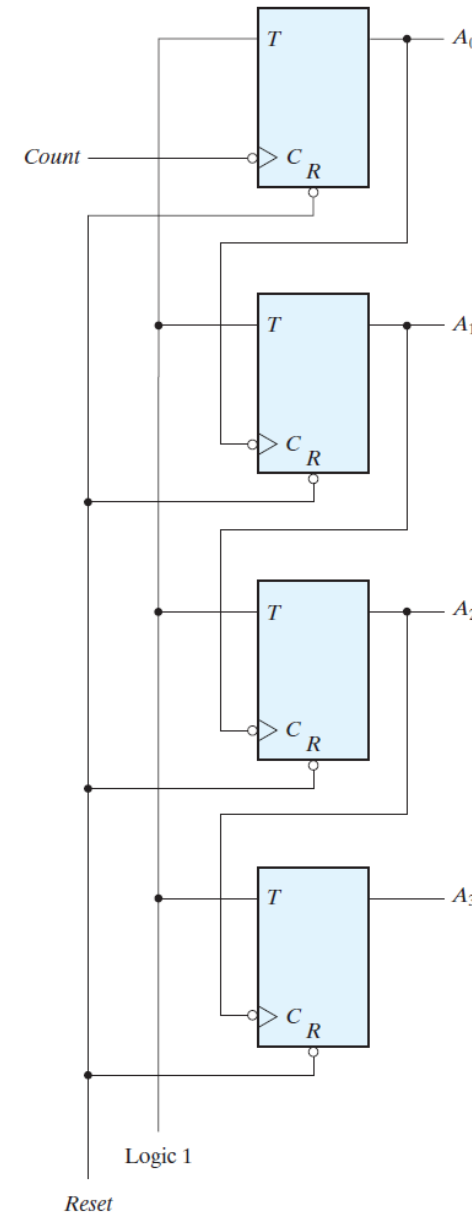- It consists of a series connection of complementing FFs
 - With **output of a FF** connected to **C** **input of the next higher-order FF**
 - The FF holding the least significant bit receives the incoming count pulses.





▶ Binary Ripple Counter

- Let's look at first nine binary numbers for its operation
 - The count starts with binary 0 and increments by 1 with each count pulse input


How to design a countdown counter?

A_3	A_2	A_1	A_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0

 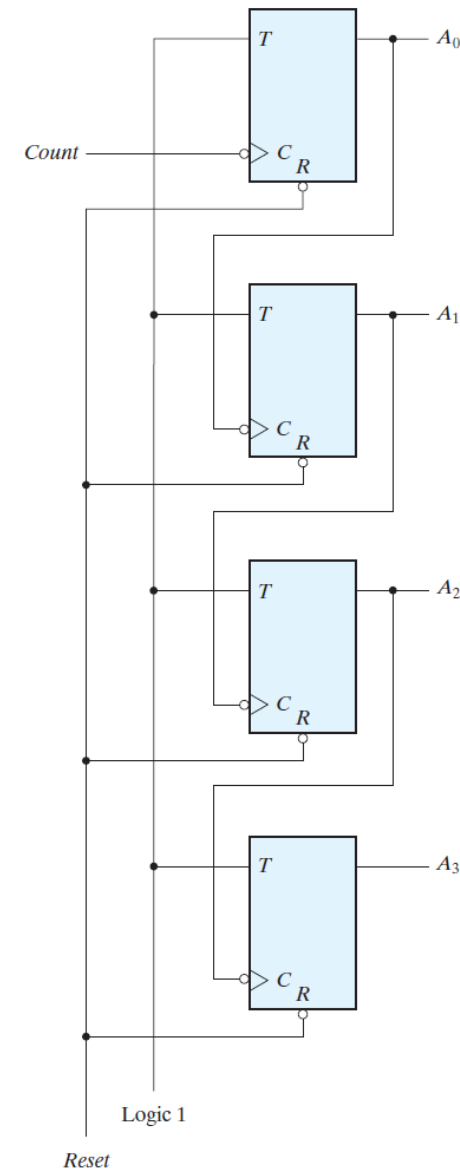

► Binary Ripple Counter

 - A decimal counter follows a sequence of 10 states and returns to 0 after the count of 9
- It must have at least four FFs to represent each decimal digit




State Diagram

JK Flip-Flop				
J	K	Q(t + 1)		
0	0	Q(t)	No change	
0	1	0	Reset	
1	0	1	Set	
1	1	Q'(t)	Complement	


Characteristic Table

Logic Diagram

 

▶ Binary Ripple Counter

 - Signals that affect the FF transition depend on the way they change from 1 to 0




State Diagram

<i>J/K Flip-Flop</i>				
<i>J</i>	<i>K</i>	<i>Q(t + 1)</i>		
0	0	<i>Q(t)</i>	No change	
0	1	0	Reset	
1	0	1	Set	
1	1	<i>Q'(t)</i>	Complement	

Characteristic Table


Logic Diagram

 

Logic 1

▶ 3-Decade Decimal BCD Counter

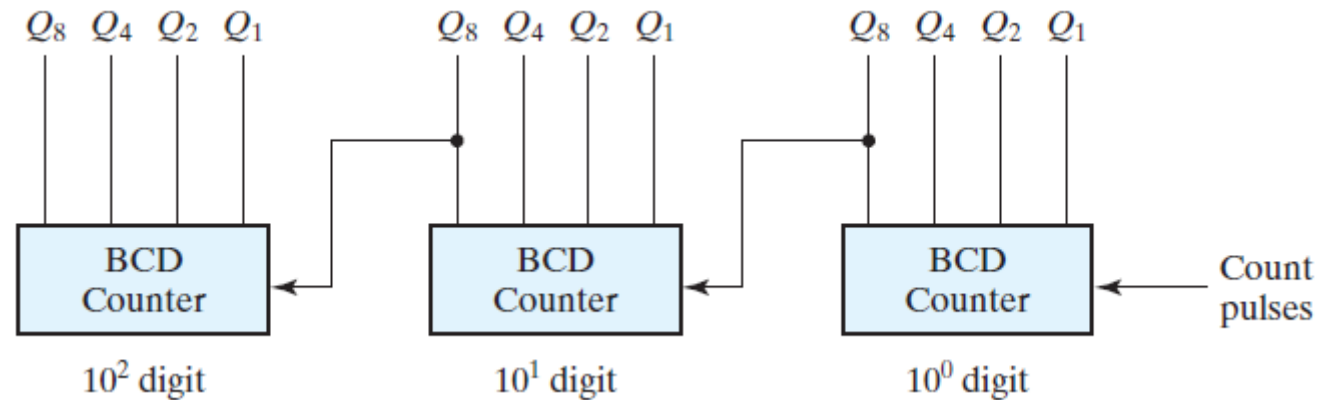- To count from 0 to 999, we need a three decade counter
 - Multiple decade counters can be constructed by connecting BCD counters in cascade (one for each decade)
 - The inputs to the second and third decades come from Q₈ of previous decade




► Synchronous Counters

- Clock pulses are applied to the inputs of all flip-flops in synchronous counters
 - The decision whether a flip-flop is to be complemented is determined from the values of the data inputs
 - If $T = 0$ or $J = K = 0$, the flip-flop does not change state
 - If $T = 1$ or $J = K = 1$, the flip-flop complements

▶ Synchronous Binary Counters

 - The least significant position is complemented w/ every pulse
- A flip-flop in any other position is **complemented** when **all the bits** in the **lower** significant **positions are equal to 1**




► Synchronous Up-Down Binary Counters

• Countdown counter

- The least significant position is complemented w/ each pulse
- A flip-flop in any other position is **complemented** when **all the bits** in the **lower** significant **positions are equal to 0**

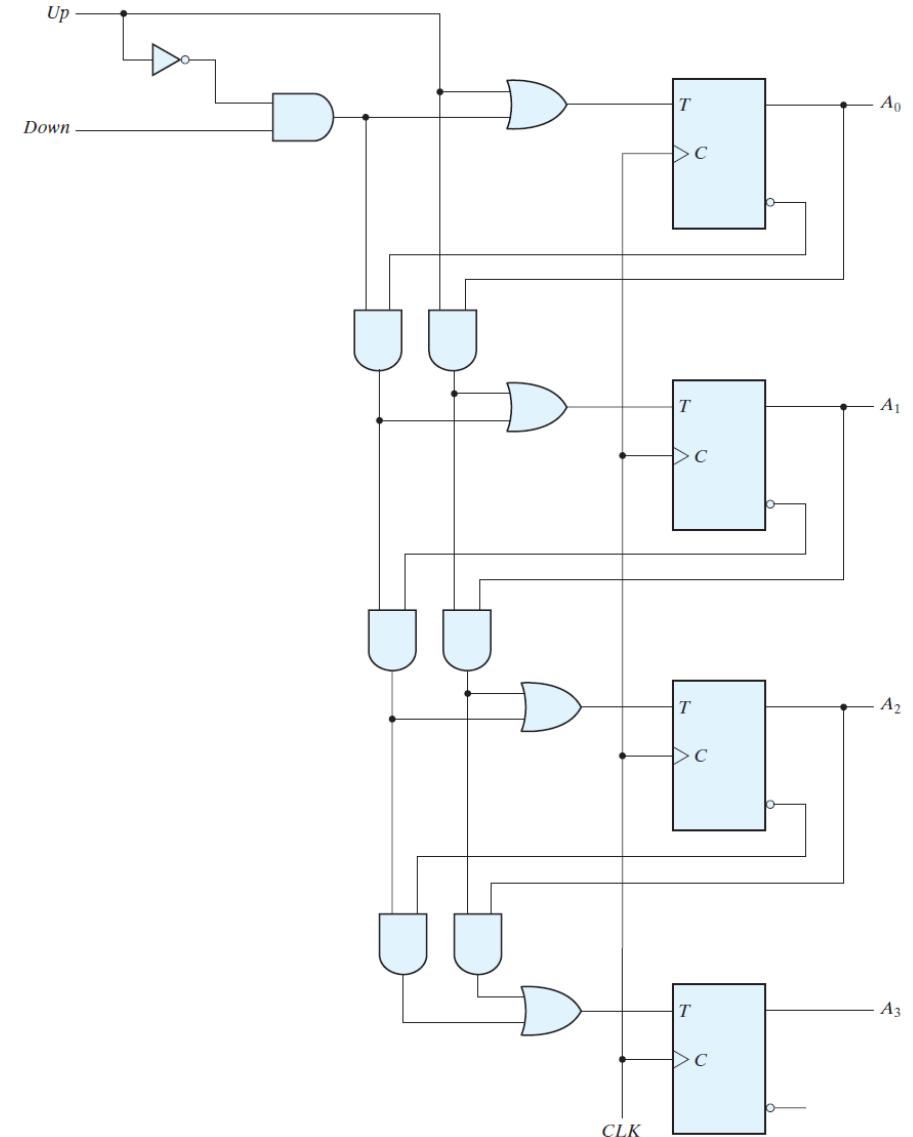Let's combine up counter with down counter



► BCD Counter

- It counts binary-coded decimal from 0000 to 1001 and back to 0000
 - As returning to 0 after a count of 9, it does not have a regular pattern
 - Thus, we need to go through a **sequential design procedure**

State Table

Present State				Next State				Output	Flip-Flop Inputs			
Q_8	Q_4	Q_2	Q_1	Q_8	Q_4	Q_2	Q_1	y	TQ_8	TQ_4	TQ_2	TQ_1
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

► Design of a BCD Counter

- The flip-flop input equations can be simplified by means of maps
 - The unused states for minterms 10 to 15 are taken as don't-care terms
 - The circuit consists of four T flip-flops, five AND gates, and one OR gate

State Table

Present State				Next State				Output	Flip-Flop Inputs			
Q_8	Q_4	Q_2	Q_1	Q_8	Q_4	Q_2	Q_1	y	TQ_8	TQ_4	TQ_2	TQ_1
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

$$T_{Q1} = 1$$

$$T_{Q2} = Q'_8Q_1$$


$$T_{Q4} = Q_2Q_1$$

$$T_{Q8} = Q_8Q_1 + Q_4Q_2Q_1$$

$$y = Q_8Q_1$$

▶ Binary Counter with Parallel Load

 - Counters quite often require a parallel-load capability
 - Ex) transferring an initial binary number into the counter prior to its operation
 - When '**Load=1**', the input load control **disables the count operation** and **causes a transfer of data**
 - If **both control inputs are 0**, clock pulses **do not change the state** of the register




Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

▶ Binary Counter with Parallel Load

- The '**C_out = 1**' if **all the flip-flops are equal to 1** while the count input is enabled
 - Expand the counter w/ more than 4 bits
 - Speed** of the counter is **increased** when the **carry is generated** directly from the outputs of **all four** flip-flops (why?)


Clear	CLK	Load	Count	Function
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

 


► BCD Counter Using a Counter w/ Parallel Load

- Using 'Load' input, we detect state 1001 (clears on next clock edge)
- Using 'Clear' input, count 1010 is detected and clears immediately

Using the 'Load' Input

 

Using the 'Clear' Input

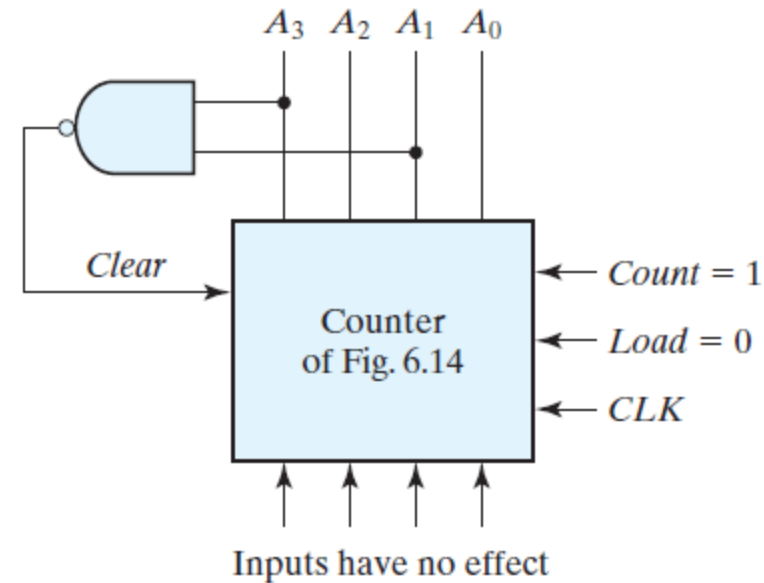

▶ Counter in VHDL

```
begin
    process (clk)
    begin
        if (rising_edge(clk)) then
            if reset = '1' then
                -- Reset the counter to 0
                cnt <= (others => '0');
            elsif enable = '1' then
                -- Increment the counter if counting is enabled
                cnt <= cnt + '1';
            end if;
        end if;

        -- Output the current count
        q <= cnt;
    end process;
end rtl;
```

► Summary

- Learned different types of clocked sequential circuits
 - Registers
 - Counters
- Learned how to implement of registers and counters
 - Design procedure for registers or counters
 - Design different types of counters in Verilog