

Digital Logic Circuit (SE273 – Fall 2020)

Lecture 4: Combinational Logic Design

Jaesok Yu, Ph.D. (jaesok.yu@dgist.ac.kr)


Assistant Professor
Department of Robotics Engineering, DGIST

► Goal

- Learn to design combinational circuits
 - Specification, formulation, optimization
 - Technology mapping, verification
- Implement a number of important functions
 - The fundamental and reusable circuits (= functional blocks)
 - Implement functions of a single variable (decoders, encoders, multiplexers,...)


► Combinational Logic vs Sequential Logic

Combinational Logic

 


$$Out = f(In)$$

Sequential Logic

 

$$Out = f(In, Previous\ In)$$

► Design Procedure

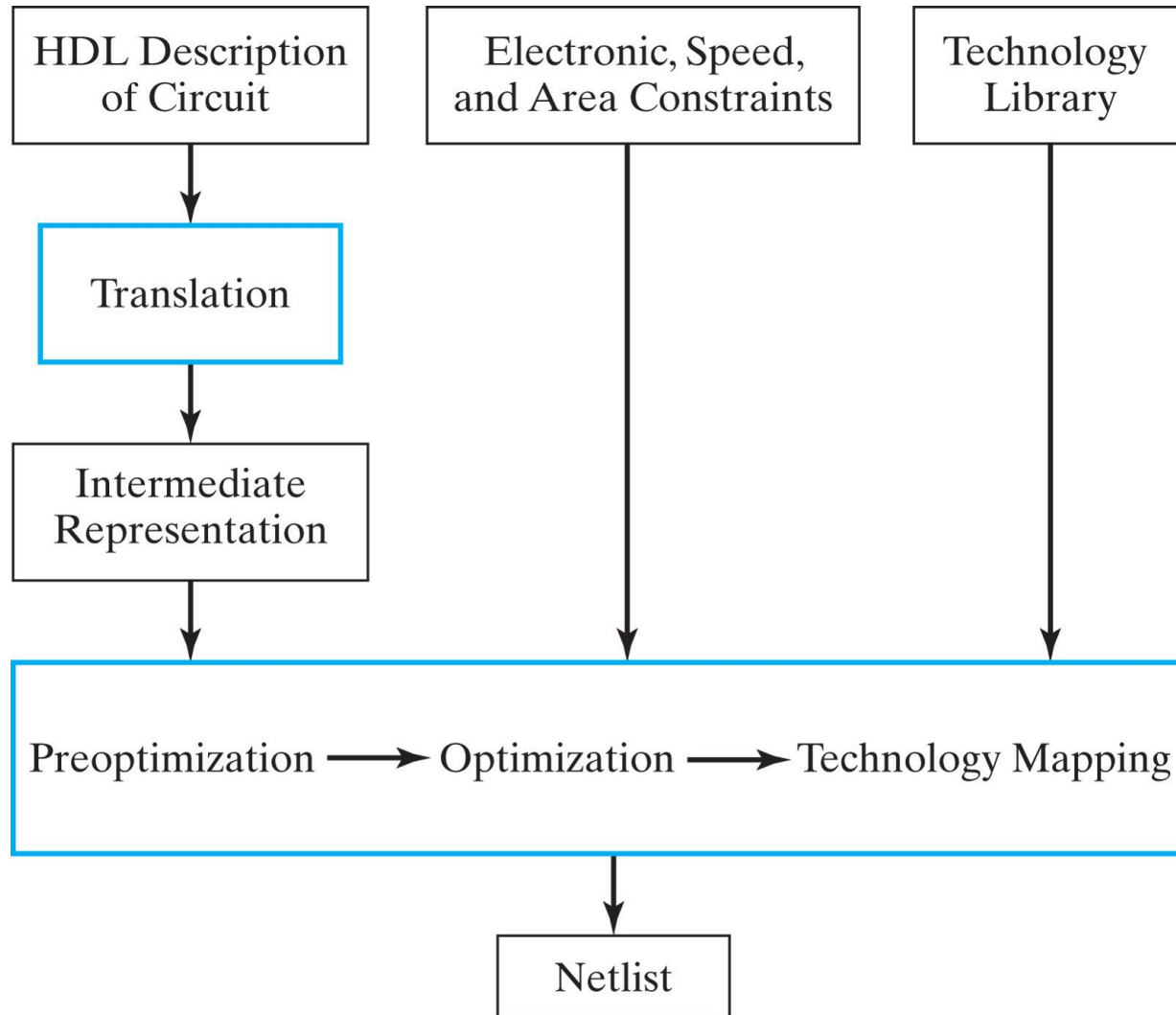

- **Specification**: write a specification for the circuit
- **Translation (Formulation)**: derive the truth table or initial Boolean equations
- **Optimization**: apply two-level and/or multi-level optimization
- **Technology Mapping**: transform the logic diagram to a new diagram using the available technology
- **Verification**: verify the correctness of the final design

► Design Example: BCD-to-Excess3 Code Converter

• Specification

- The excess-3 code for a decimal digit 'd' is the binary combination equal to 'd+3'
- The excess-3 code has desirable properties with respect to implementing decimal subtraction

Truth Table for Code-Converter Example

Decimal Digit	Input BCD				Output Excess-3			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0

► Excess3 Code?

• Self-complementary property

Truth Table for Code-Converter Example

Decimal Digit	Input BCD				Output Excess-3			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1	1
1	0	0	0	1	0	1	0	0
2	0	0	1	0	0	1	0	1
3	0	0	1	1	0	1	1	0
4	0	1	0	0	0	1	1	1
5	0	1	0	1	1	0	0	0
6	0	1	1	0	1	0	0	1
7	0	1	1	1	1	0	1	0
8	1	0	0	0	1	0	1	1
9	1	0	0	1	1	1	0	0

<taking 1's complement>

W X Y Z: 1 0 0 1 (6)

<9's complement>

$$\begin{aligned}
 &9 - 3 \\
 &= 9 + 6 \text{ (9's complement of 3)} \\
 &= 15 \text{ (1 is end-around carry, add again)} \\
 &> 5 + 1 = 6
 \end{aligned}$$

► Design Example: BCD-to-Excess3 Code Converter

• Formulation

- The excess-3 code is obtained from a BCD code by adding '0011'
- We can build a truth table accordingly
- The six combinations from 1010 through 1111 are not listed as they are never used in BCD code
- We can treat them as **don't-care conditions**





BCD(8421)				Excess-3			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X



► Design Example: BCD-to-Excess3 Code Converter

• Optimization

    - We may use the K-maps for the initial optimization of the four output functions
- Don't-care conditions (X's) are useful to further reduce # of literals/terms
- Each map represents one of the outputs of the circuit



► Design Example: BCD-to-Excess3 Code Converter

- Now, we can draw two-level AND-OR logic diagram
 - Directly from the Boolean expressions derived from the maps
 - We may **apply multiple-level optimization** as a 2nd optimization step (ex: reduce the gate input cost)
 - For the additional optimization, we **consider sharing subexpressions**

$$T_1 = C + D$$

$$W = A + BC + BD = A + BT_1$$


$$X = \overline{B}C + \overline{B}D + B\overline{C}\overline{D} = \overline{B}T_1 + B\overline{T}_1$$

$$Y = CD + \overline{T}_1$$

$$Z = \overline{D}$$

► Design Example: BCD-to-Excess3 Code Converter

- Then, the logic diagram becomes

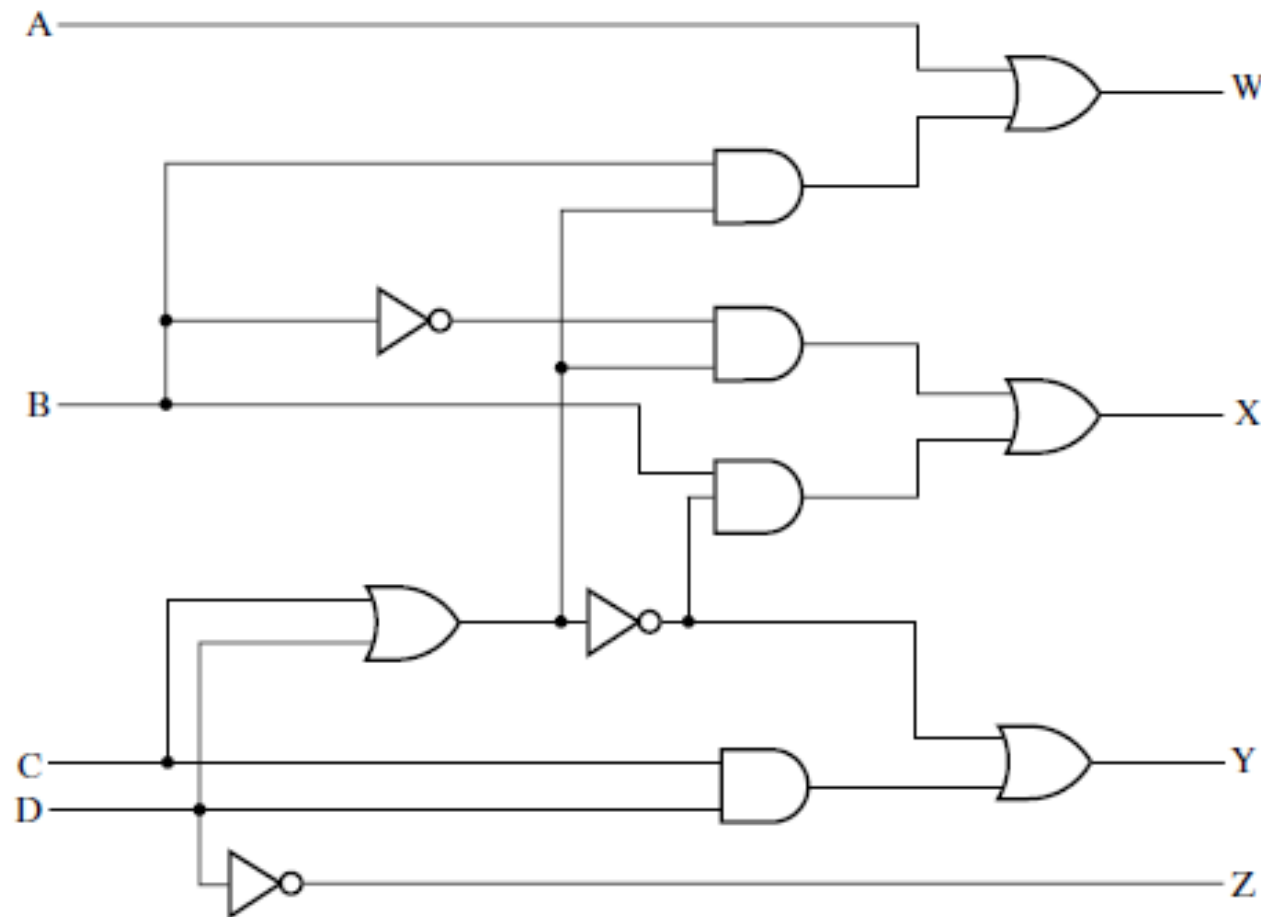

$$T_1 = C + D$$

$$W = A + BC + BD = A + BT_1$$

$$X = \overline{B}C + \overline{B}D + B\overline{C}\overline{D} = \overline{B}T_1 + B\overline{T}_1$$

$$Y = CD + \overline{T}_1$$


$$Z = \overline{D}$$

Circuit netlists


► Hierarchical Design

- Hierarchical design approach is generally used in designing a digital system (divide-and-conquer)
 - We may deal with circuit complexity as we broken down into pieces (called functional blocks)
 - If a block is still to large, it can be broken into smaller blocks
 - This process can be repeated as necessary

► Hierarchical Design Procedure

 


(a) Symbol for circuit

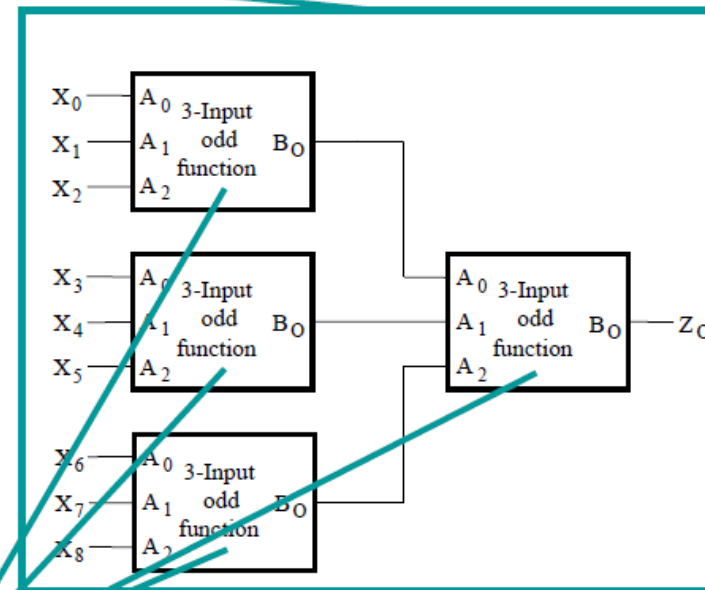

(b) Circuit as interconnected 3-input odd function blocks



 (c) 3-input odd function circuit as interconnected exclusive-OR blocks



(d) Exclusive-OR block as interconnected NANDs

► Hierarchical Design Example: 4-bit Equality Comparator


• Specification

- An equality comparator is a circuit that compares two binary vectors to determine whether they are equal or not
- Inputs: two vectors $A[3:0]$ and $B[3:0]$
- Output: a single-bit variable E ($E=1$ if vectors A and B are equal)

► Hierarchical Design Example: 4-bit Equality Comparator

• Formulation

 - We bypass the use of a truth table due to its size!!
- Step1: To compare A and B, the bit values in **each of the respective positions**, 3→0, of A and B **must be equal**
- Step2: If all of bit positions of A and B contain equal values, then $E = 1$
- Intuitively, we developed a simple 2-level hierarchy



► Hierarchical Design Example: 4-bit Equality Comparator



• Optimization

- For bit position i , we define the circuit output N_i to be 0 if A_i and B_i have the same values
- And $N_i = 1$ if A_i and B_i have different values
- Then, MX circuit can be described by

$$N_i = \bar{A}_i B_i + A_i \bar{B}_i$$


- Now, we employ four copies of this circuit
- Output E can be computed by the relation:

$$E = \overline{N_0 + N_1 + N_2 + N_3}$$

  

► Hierarchical Design Example: 4-bit Equality Comparator

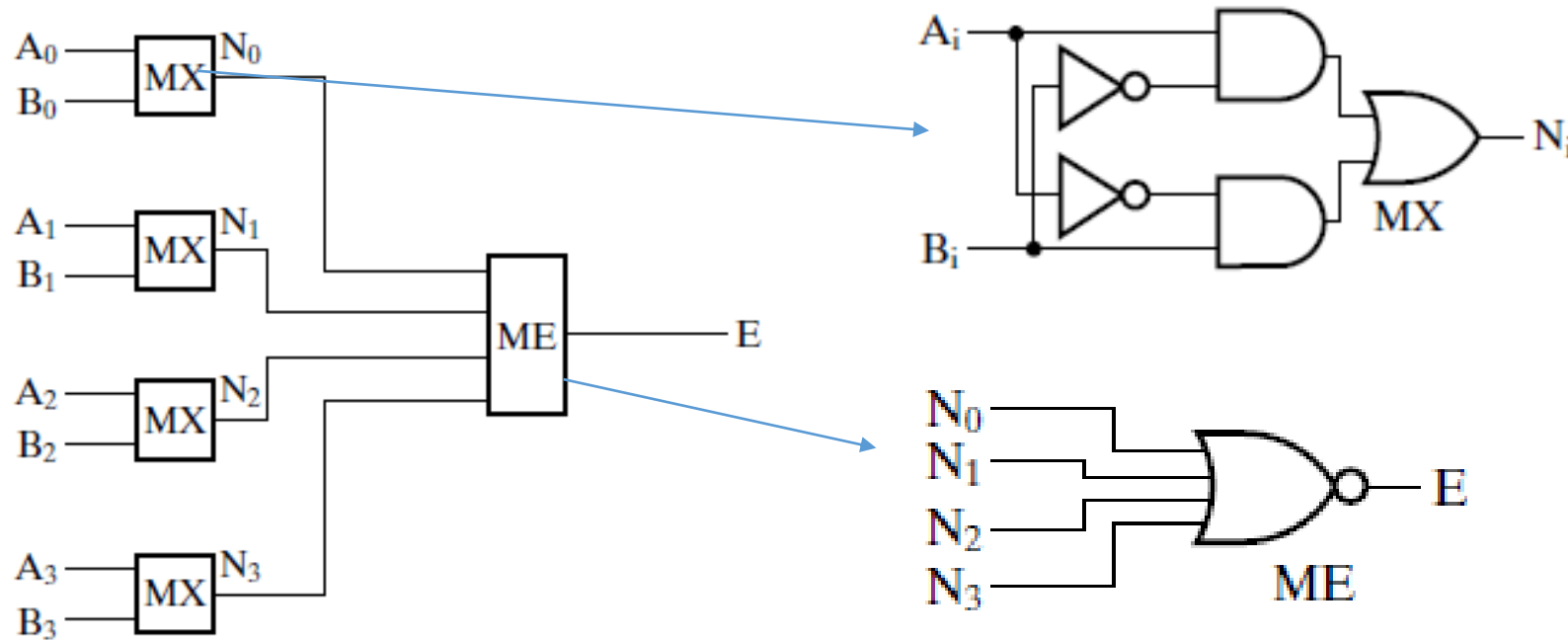
- Both circuits given are optimum two-level circuits
 - Two circuit diagrams plus the block diagram represent the hierarchical design of a 4-bit equality comparator




11 Symbols are required to represent the circuit

► Hierarchical Design Example: 4-bit Equality Comparator

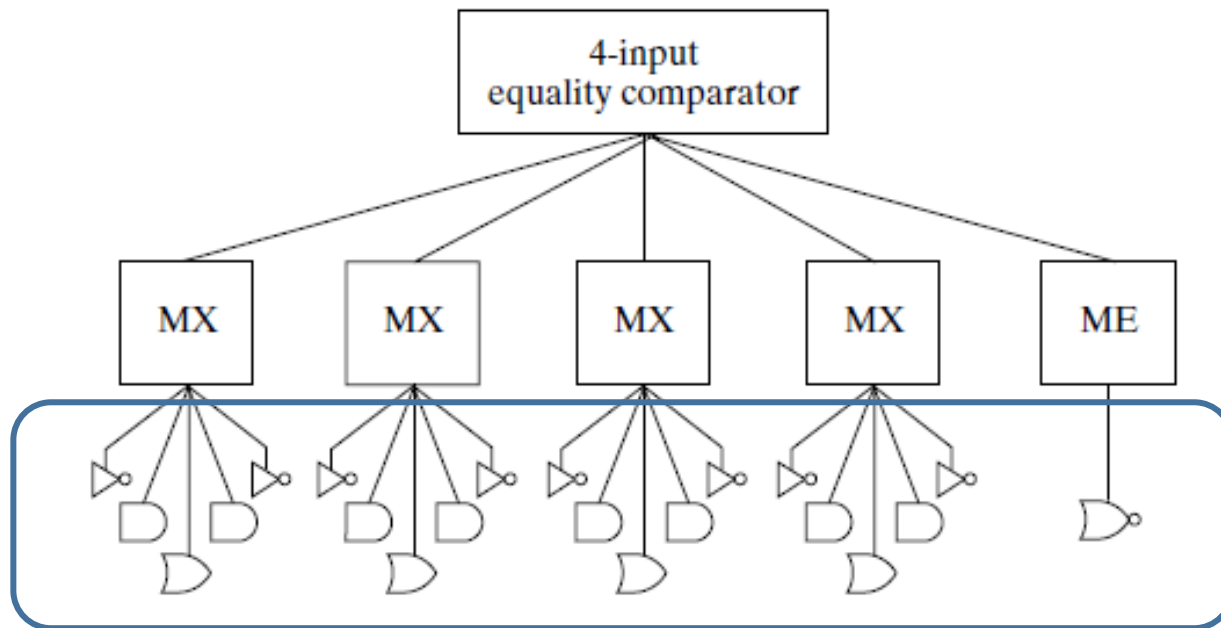- We may represent the circuit without interconnections
 - By simply starting with the top block
 - Then, connect blocks or primitives from which the block is constructed
 - The hierarchy can be easily understood




How many gates are needed?

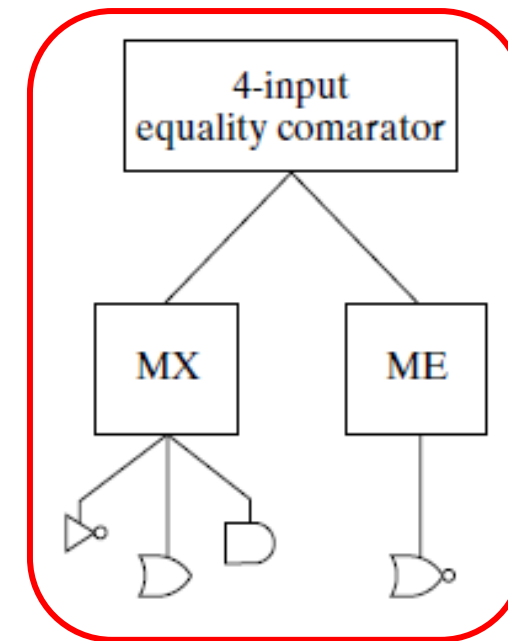

What is the purpose of this diagram?

► Primitive Blocks

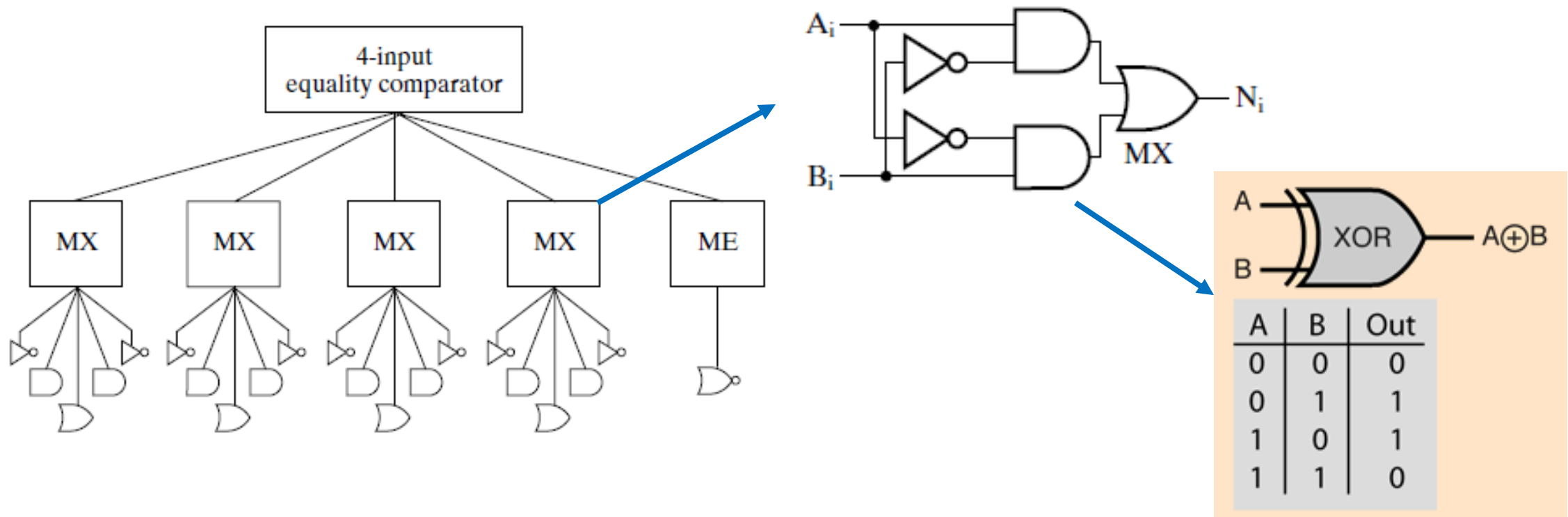- At leaves of the hierarchy tree, there are logic gates
 - These gates are commonly called **primitive blocks**
 - There can be more complex blocks, other than simple gates, as predefined blocks (**MX blocks can be considered as predefined XOR gates**)




► Reusability of Blocks

- Reusability is another important property of hierarchical design
 - There are four copies of 2-input MX blocks
 - On the right, there is only one copy of the 2-input MX block
 - That means a circuit designer need to **implement one MX block** and **use this design four times**




Why the reusability so important in designing a digital system??

 ▶ Technology – Transistors (Intel Processors)




**4004 Microprocessor
(1971)**

2,250 transistors in 12mm²
10,000 nm, 1MHz operation

 

**Pentium 4
(2000)**

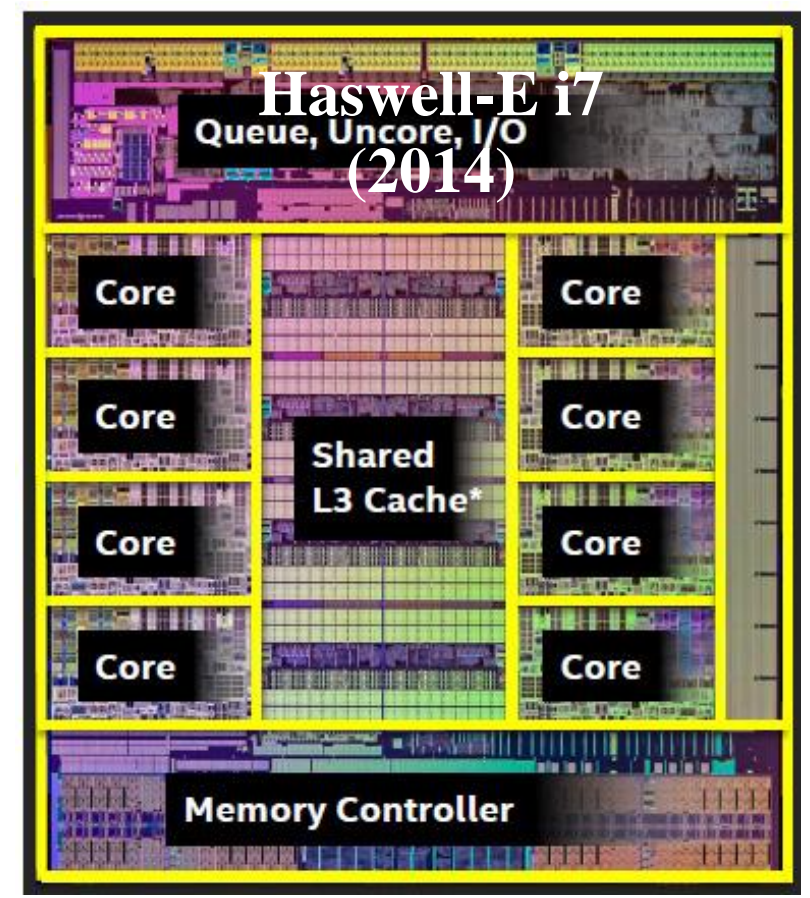
42 million transistors in 217mm²
180 nm, 1.3GHz operation



**Haswell-E i7
(2014)**

2.6 billion transistors in 355mm²
22 nm, 3GHz operation

▶ Future Technology: Light? Quantum?

 

3D Packaging

ESD and Custom IO Cells	High Speed analog and digital interfaces	Optical Fiber Attach	3D Interposer Design
-------------------------	--	----------------------	----------------------

12 Nanometer ASIC

SRAM	Custom Delay Line and Clocking	DAC Bank	Digital Activations	External I/O
		ADC Bank	Amplifiers	

90 Nanometer ASIC with Transistors + Photonics

Laser Monitor	Vector Modulator	Compute Unit Cell	High Speed Detection	Pin Sharing
Light Distribution				Monitor ADCs

Power and Performance

Mars Power

Laser
8.8%
Misc Photonics
7.5%


Weight DACs
10.3%

Vector DACs
11.3%

ADCs
12.7%

Static
0.7%

Digital Dynamic
48.7%

 

Under 3W TDP

Most power is data movement

ResNet-50 @ 99% accuracy
(ImageNet, compared to FP32)

► Technology Mapping

- Mapping AND, OR, NOT gates **to NAND / NOR gate cells** is critical in designing a digital circuit (why??)
 - A NAND technology consists of a collection of cells, each of which includes a NAND gate with a fixed # of inputs
 - Assume we have four cell types, based on # of inputs ($n = 1, 2, 3, 4$)
 - INV, 2NAND, 3NAND, and 4NAND, respectively


► Technology Mapping

- We begin with the optimized logic diagram of the circuit consisting of AND and OR gates (+ inverters)
 - Then, the function is converted to NAND logic by converting the logic diagram to NAND gates and INVs
 - Same applies for NOR gate cells


► Technology Mapping

• Procedure for technology mapping

 
- Objective: obtain a circuit diagram with the fewest INVs
- 1) Replace each AND and OR gate with NAND (NOR) gate and inverter equivalent circuits: (a) and (b)
- 2) Cancel all inverter pairs




(a) Mapping to NAND gates

 

(b) Mapping to NOR gates

 

(c) Pushing an inverter through a "dot"

 

(d) Canceling inverter pairs

► Implementation with NAND Gates


- Implement the following optimized function with NAND gates:

$$F = AB + \overline{AB}C + \overline{AB}\overline{D} + E$$

► Implementation with NAND Gates

- Implement the following optimized function with NAND gates:


 
$$F = AB + \overline{AB}C + (\overline{AB})\overline{D} + E$$



► Implementation with NAND Gates

- Implement the following optimized function with NAND gates:
  
$$F = AB + (\overline{A}\overline{B})C + (\overline{A}\overline{B})\overline{D} + E$$




Step 1 is applied!!

- 1) Replace each AND and OR gate with NAND (NOR) gate and inverter equivalent circuits

► Implementation with NAND Gates


- Implement the following optimized function with NAND gates:
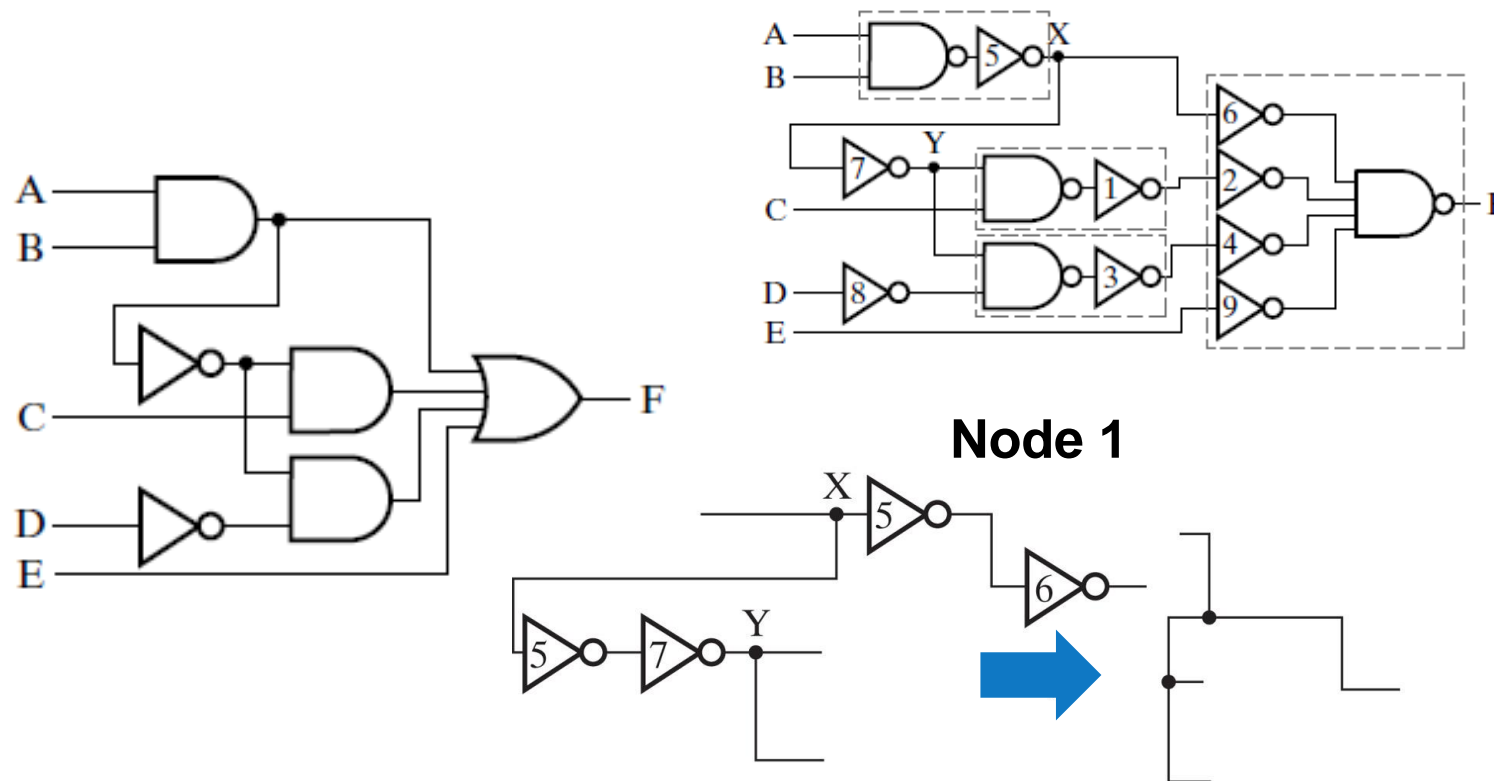
$$F = AB + \overline{(AB)}C + \overline{(AB)}\overline{D} + E$$



Step 2 is applied!!



2) Cancel all Inverter pairs

 


► Implementation with NAND Gates

- Implement the following optimized function with NAND gates:
  
$$F = AB + \overline{(AB)}C + (\overline{AB})\overline{D} + E$$



Step 1


 


Step 2

► Implementation with NOR Gates

- Implement the following optimized function with NOR gates:
  
$$F = AB + \overline{(AB)}C + \overline{(AB)}\overline{D} + E$$





Step 1 is applied!!
(Replace to NOR gate)

► Implementation with NOR Gates

- Implement the following optimized function with NOR gates:
  
$$F = AB + \overline{AB}C + (\overline{AB})\overline{D} + E$$





Step 2 is applied!!
(Cancel all inverters)


► Comparison Btw NAND and NOR Implementations

- Which implementation seems to be better and why?
  
$$F = AB + \overline{AB}C + (\overline{AB})\overline{D} + E$$



NAND

 

NOR


► Comparison Btw NAND and NOR Implementations

- Which implementation seems to be better and why?
 - Gate-input cost:
 - Depth of logic gates in series:
- The result of a technology mapping is clearly influenced by the initial circuit or equation forms prior to mapping
 - Mapping to NANDs for a circuit with an OR gate at the output produces a **NAND gate** at the output (natural)
 - For NOR counterpart, it produces **an inverter driven by a NOR gate** at the output

► Comparison Btw NAND and NOR Implementations

• Which imp

- Gate-imp
- Depth of

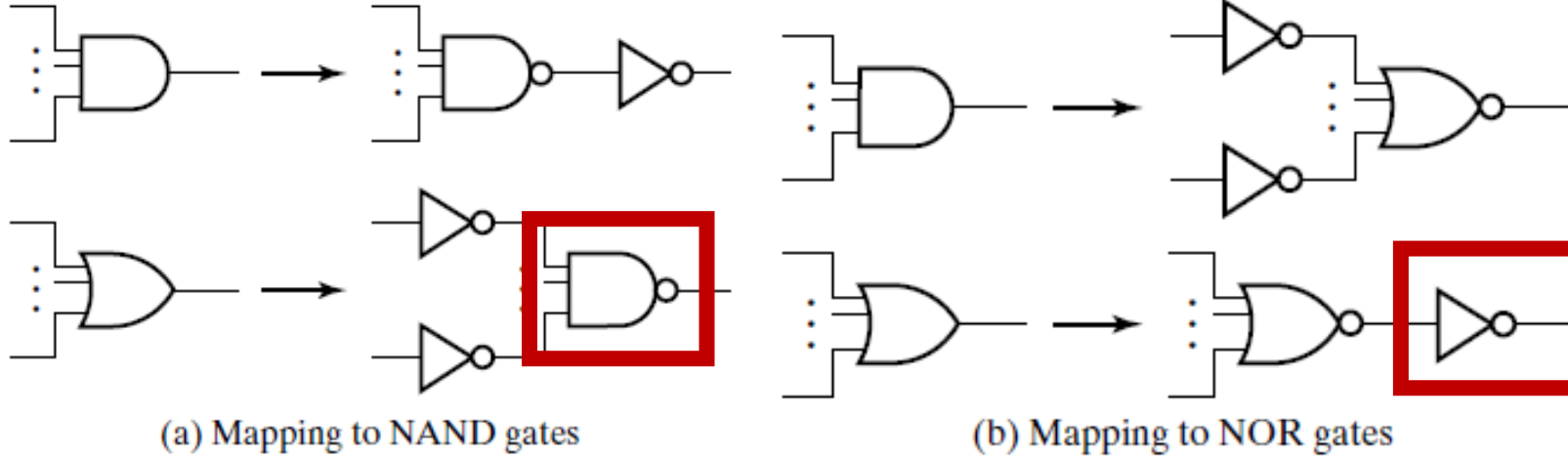

- The result of a technology mapping is clearly influenced by the initial circuit or equation forms prior to mapping
 - Mapping to NANDs for a circuit with an OR gate at the output produces a **NAND gate** at the output (natural)
 - For NOR counterpart, it produces **an inverter driven by a NOR gate** at the output

► Verification


- Determine whether or not a given circuit implements its specified function
 - Manual logic analysis
 - Computer simulation-based logic analysis
- If the circuit does not meet its specification, then it is incorrect
- Verification plays a vital role in preventing incorrect circuit designs from being manufactured

► Manual Logic Analysis

- It consists of finding Boolean equations for the circuit outputs, then finding the truth table for the circuit
 - It is often convenient to break up the circuit into subcircuit **by defining intermediate variables** at selected points
 - ***Fan-out points***: at which a gate output drives two or more gate inputs

► Manual Verification of BCD-to-Excess3 Code Converter

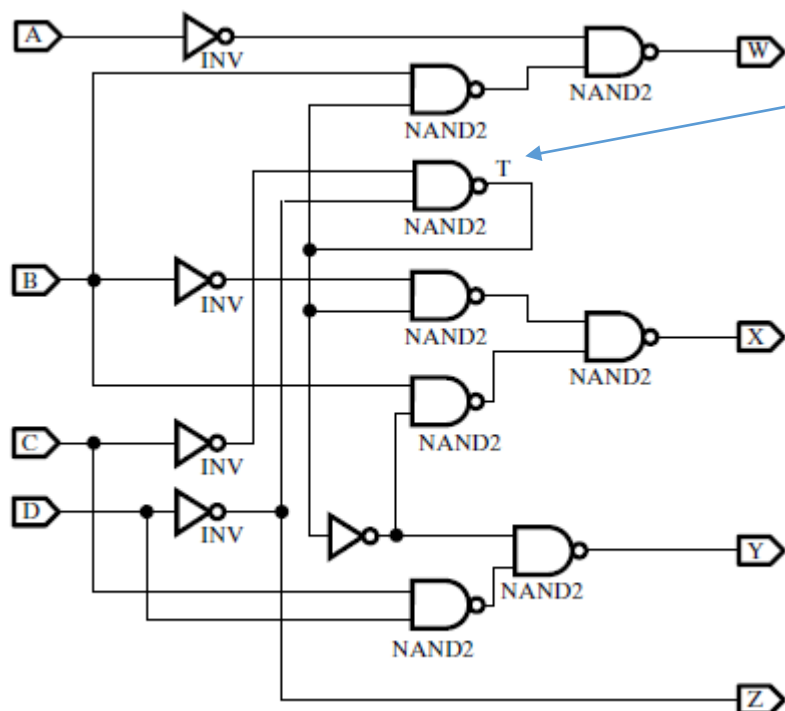- Objective is to complete the truth table from the circuit implementation
 - The intermediate point T is selected to simplify the analysis



NAND-mapped circuit implementation

$$T = \overline{\overline{C}\overline{D}} = C + D$$

$$W = \overline{\overline{A}(\overline{T \cdot B})} = A + BT$$

$$X = \overline{(\overline{B}T)(\overline{B}\overline{C}\overline{D})} = \overline{B} \cdot T + B\overline{T}$$

$$Y = CD + \overline{T}$$

$$Z = \overline{D}$$

$$W = A + B(C + D) = A + BC + BD$$

$$X = \overline{B}(C + D) + B(CD) = \overline{B}C + \overline{B}D + B\overline{C}\overline{D}$$

$$Y = CD + \overline{(C + D)} = CD + \overline{C}\overline{D}$$


Fill the remaining product terms!

Input BCD				Output Excess-3			
A	B	C	D	W	X	Y	Z
0	0	0	0				1
0	0	0	1				
0	0	1	0		1		1
0	0	1	1		1	1	
0	1	0	0				1
0	1	0	1	1			
0	1	1	0	1			1
0	1	1	1	1		1	
1	0	0	0	1			1
1	0	0	1	1			

Truth table to be completed

► Manual Verification of BCD-to-Excess3 Code Converter

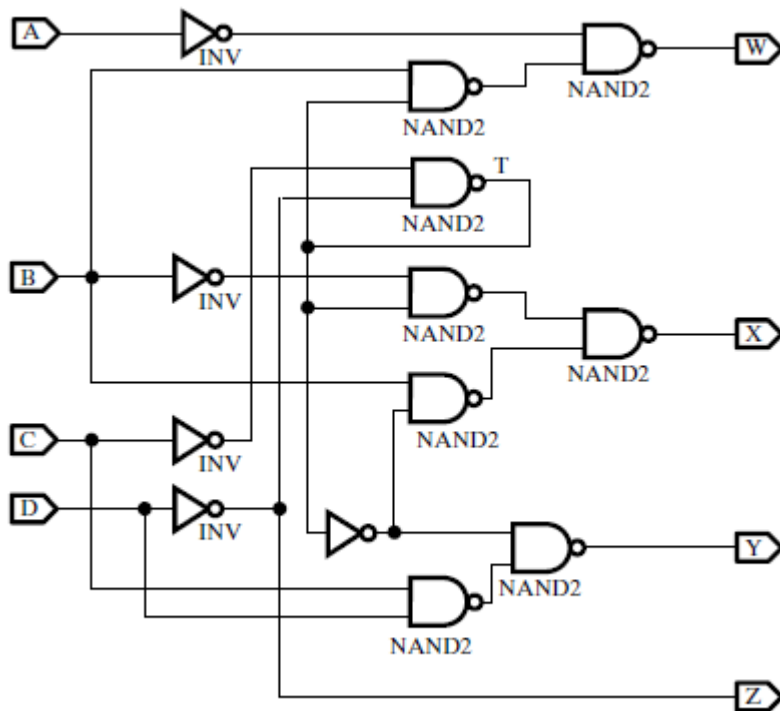- Objective is to complete the truth table from the circuit implementation
 - The intermediate point T is selected to simplify the analysis



NAND-mapped circuit implementation

Input BCD				Output Excess-3			
A	B	C	D	W	X	Y	Z
0	0	0	0				1
0	0	0	1				
0	0	1	0		1		1
0	0	1	1		1	1	
0	1	0	0				1
0	1	0	1	1			
0	1	1	0	1			1
0	1	1	1	1		1	
1	0	0	0	1			1
1	0	0	1	1			


Truth table to be completed

Input BCD				Output Excess-3			
A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

Original truth table

► Simulation-Based Verification

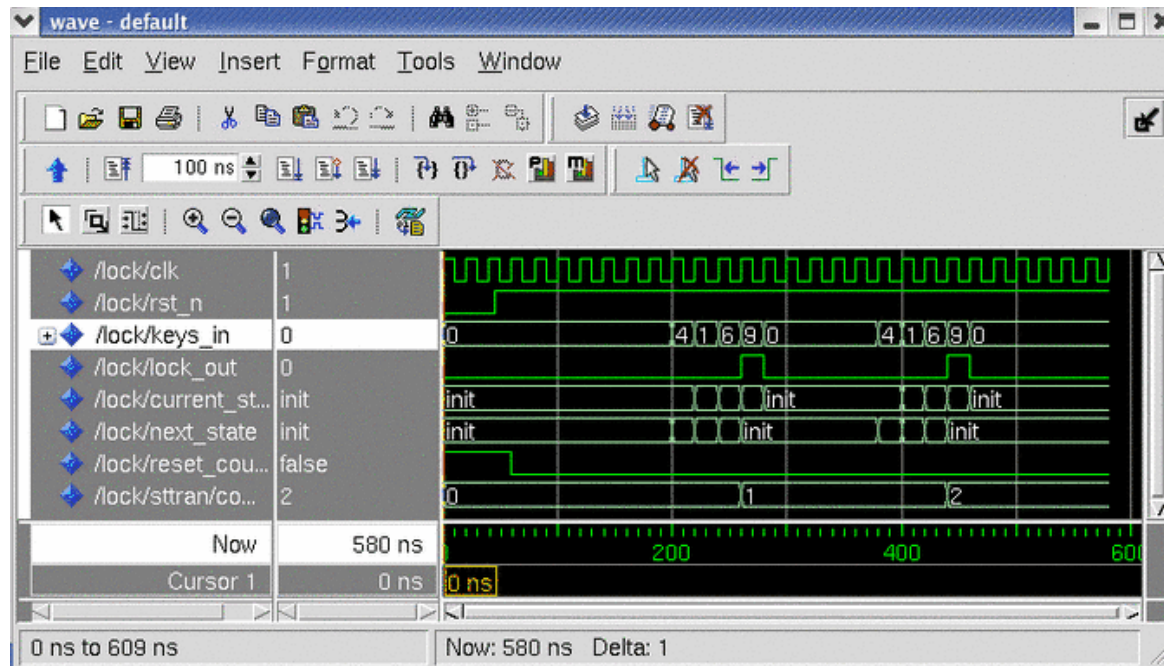
- You can use computer simulation for verification
 - A computer permits verification with significantly larger number of variables
 - Greatly reduces the tedious analysis effort
- Simulation is performed on provided input values
 - You need to apply (almost) all possible input combinations




Model*Sim*®

► Simulation-Based Verification

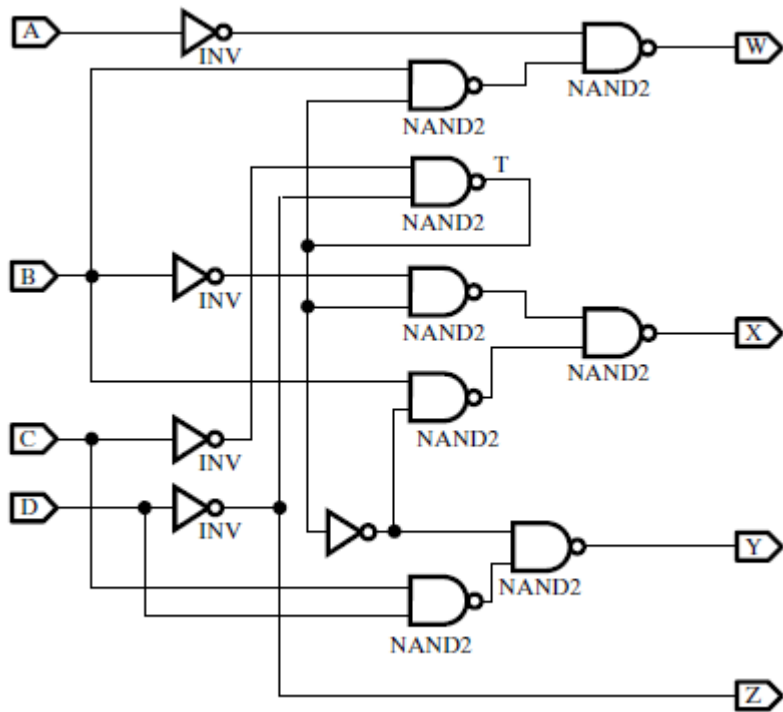- In addition to entering the circuit schematic, input combinations are given as a waveform




NAND-mapped circuit implementation

 

Simulation results of computer-based verification

► Combinational Functional Blocks

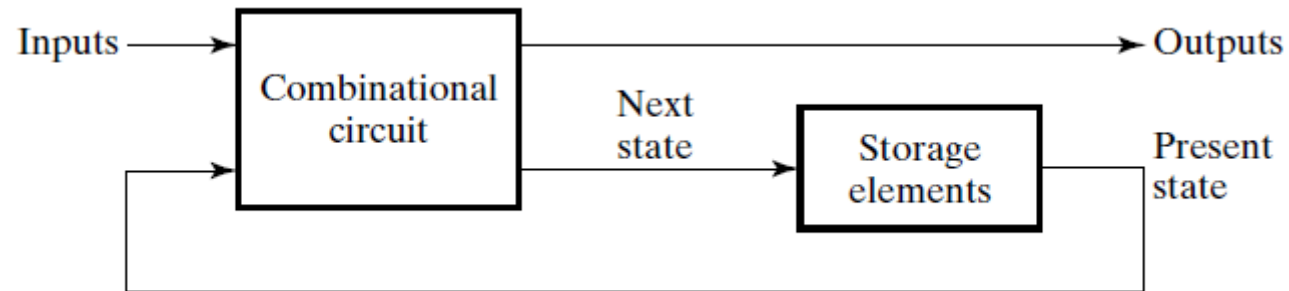- **Functional blocks:** a pre-defined combinational circuit that is specific to a certain combinational function
- Normally, a large-scale integrated circuits are almost always sequential
 - It is a combination of a combinational circuit and storage elements
 - To ease the design process, some frequently-used blocks are pre-designed



Block diagram of a sequential circuit


► Rudimentary Logic Functions

- What are the most basic functions?
 - Value-fixing, transferring, inverting, and enabling

Functions of One Variable


X	F = 0	F = X	F = \bar{X}	F = 1
0	0	0	1	1
1	0	1	0	1

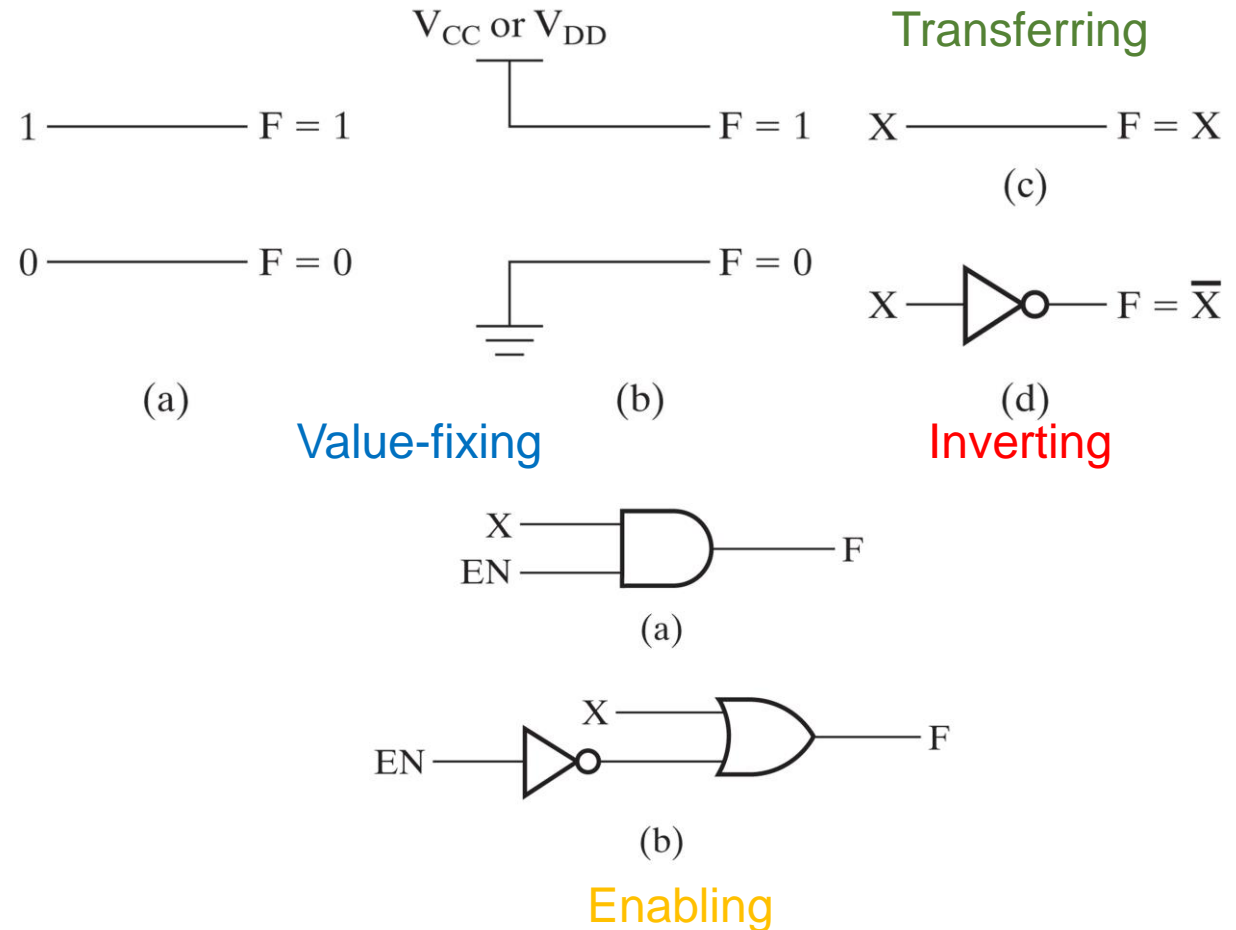Value-fixing (pointing to F=0 and F=1 columns)
 Transferring (pointing to F=X column)
 Inverting (pointing to F= \bar{X} column)





► Multi-Bit Functions

 - The functions defined so far can be applied to multiple bits on a bitwise basis
 - We can think of multiple-bit functions as vectors of single-bit functions
 - With $F = (0, 1, A, \bar{A})$, it becomes $(0, 1, 0, 1)$ with $A = 0$
 - For multiple-bit wires, we use a single line with greater thickness with a slash, representing the bit-width



► Enabling

  - The enabling permits an input signal to pass through to an output
 - With $EN=1$, input X reaches the output
 - With $EN=0$, output is fixed at 0
- When do we need enabling signal?
 - One example is a three-state buffer



INPUT		OUTPUT
A	B	C
0	1	0
1		1
X	0	Z (high impedance)




Tri-state buffer

► Decoding

- In digital computers, discrete quantities of information are represented by binary codes
 - An n-bit binary code is capable of representing 2^n distinct elements
 - **Decoding**: conversion of an input code to an m-bit code with $n \leq m \leq 2^n$
 - Decoding is performed by a circuit called *decoder*
- We design functional blocks, called n-to-m line decoders, which are the most important building blocks in a digital system

A	D ₀	D ₁
0	1	0
1	0	1

 


1-to-2 line decoder

▶ Decoder Design Example

• A 2-to-4 line decoder

- Output D_i is equal to 1 whenever the two input values on A_1 and A_0 are the binary code for the number ' i '
- There are four possible minterms in total


A_1	A_0	D_0	D_1	D_2	D_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 

► Larger Decoders

- Larger decoders require a high gate-input cost (why?)
 - We use **a hierarchical design approach**
 - The resulting decoder will have **the same or a lower gate-input cost** than the one constructed by simply enlarging each AND gate

Can you design a 6-to-64 line decoder?

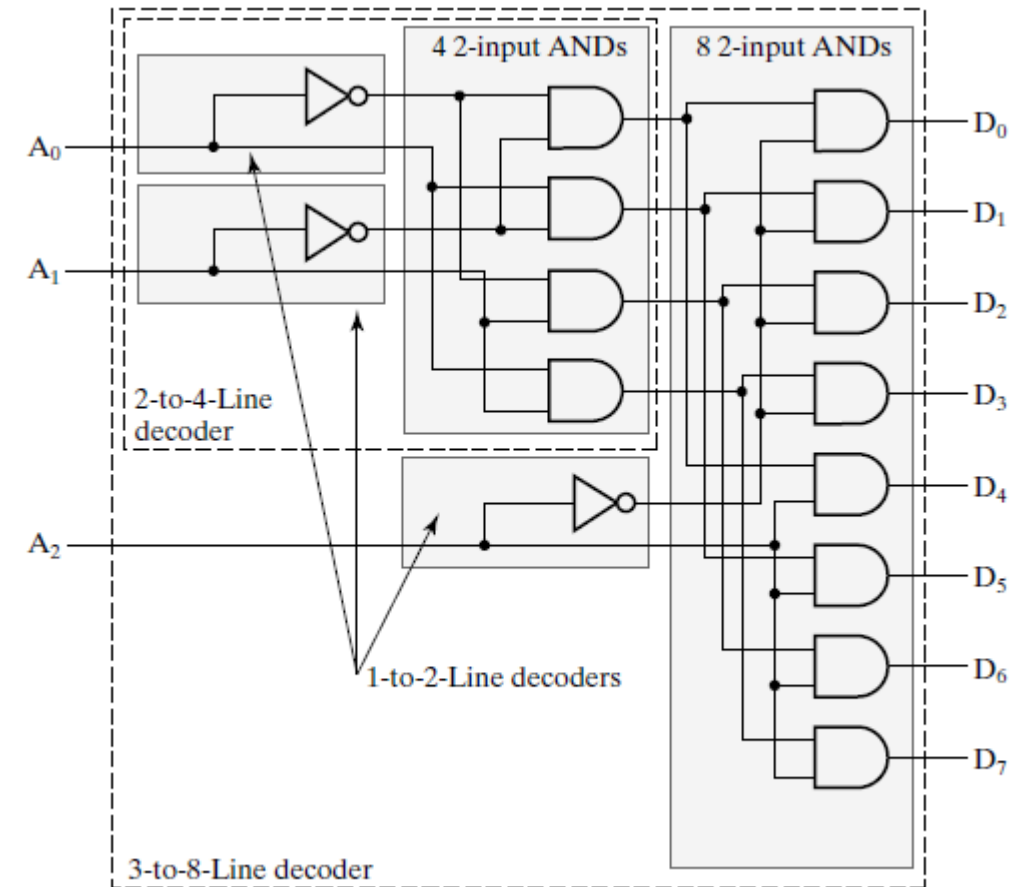


▶ Decoding and Enabling Combinations

- The n-to-m line decoding with enabling can be implemented by attaching 'm' enabling circuits to the outputs

With $EN=0$, it resets all D_i signals

EN	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

 


What about for larger decoders?

► Demultiplexer (DEMUX)


- How can we transmit the information from a single line to one of 2^n possible output lines?
 - Such distribution is done by a circuit, called demultiplexer
 - An 1-to-4 line demultiplexer can be implemented by a 2-to-4 line decoder

EN	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	X	X	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

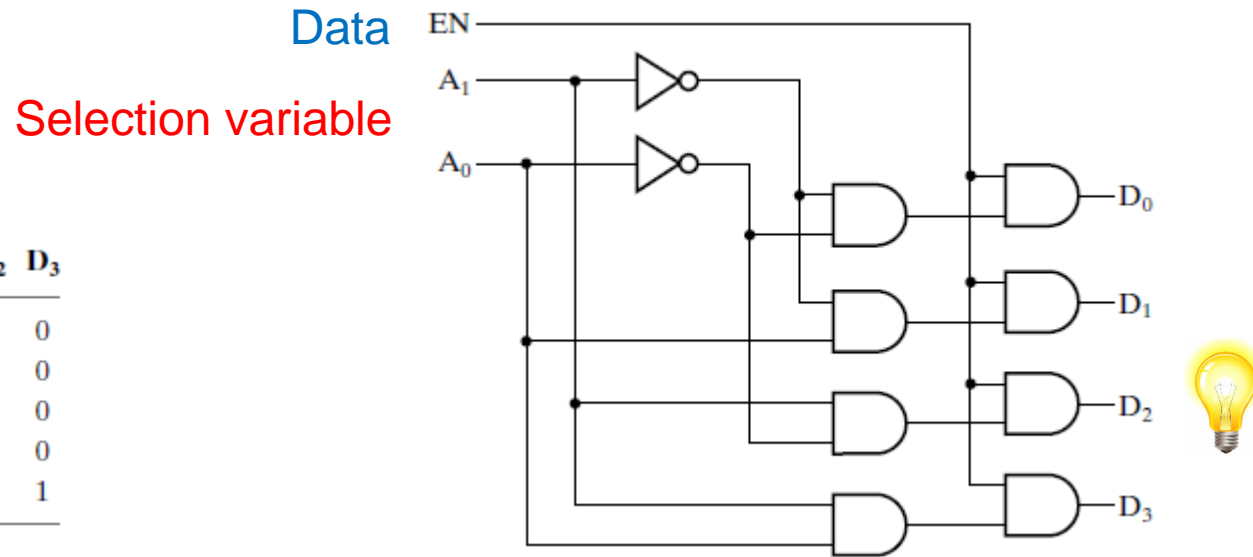

► Decoder-Based Combinational Circuits

 - Any Boolean function can be expressed as a sum of minterms
 - One can use a decoder to generate the minterms and combine them with OR gate to form a sum-of-minterms implementation
 - A Boolean function can be expressed as a sum-of-minterms from the truth table or K-map



► 1-bit Binary Adder with Decoder and OR-Gate Implementation

• Let's consider binary addition


- The sum bit S and the carry bit C can be derived from three input bits
- X and Y: two bits being added
- Z: incoming carry

Truth Table for 1-Bit Binary Adder

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S(X, Y, Z) = \sum m(1, 2, 4, 7)$$

$$C(X, Y, Z) = \sum m(3, 5, 6, 7)$$

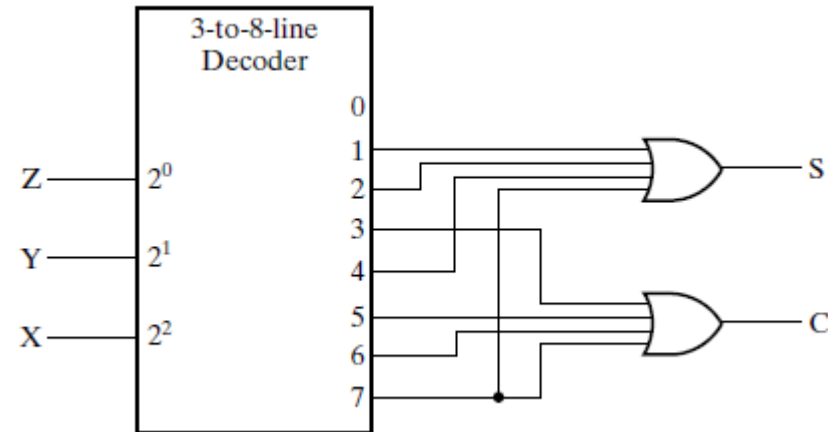

Minterm 0 is not used

What happens with a long list of minterms?

► Encoding

• Inverse operation of a decoder

- An encoder has ' 2^n ' (or fewer) input lines and ' n ' output lines
- The output generates a binary code for the input value
- Example: octal-to-binary encoder

Truth Table for Octal-to-Binary Encoder

Inputs								Outputs		
D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0	A_2	A_1	A_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

The remaining 56 rows of binary combinations are considered don't cares

► Octal-to-Binary Encoder

- $A_i = 1$ for the columns in which $D_j = 1$ only if subscript 'j' has a binary representation with a 1 in the i^{th} position
 - Only one input becomes active at any given time
 - Sometimes, two inputs may be active simultaneously which results in incorrect output (**ambiguity**)

Truth Table for Octal-to-Binary Encoder

Inputs								Outputs		
D_7	D_6	D_5	D_4	D_3	D_2	D_1	D_0	A_2	A_1	A_0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

$$A_0 = D_1 + D_3 + D_5 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$

Four-input OR gates

► Octal-to-Binary Encoder

- To resolve such ambiguity, some encoder circuits must establish an input priority
- Ensure only one input to be encoded
- Ex: put a higher priority for inputs with higher subscript numbers

Truth Table for Octal-to-Binary Encoder

Inputs								Outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

The output will be still 110, because D₆ has higher priority than D₃

► Priority Encoder

- A combinational circuit that implements a priority function
 - If two (or more) inputs are equal to 1, the input having the highest priority takes precedence
 - The truth table for a four-input priority encoder is as follows
 - No conflict of representing a minterm should appear when using 'X'

Truth Table of Priority Encoder

Inputs				Outputs		
D ₃	D ₂	D ₁	D ₀	A ₁	A ₀	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1


Valid bit

► Priority Encoder

- A combinational circuit that implements a priority function
 - Consider the case when input D_3 has the highest priority
 - If $D_3=1$, then output becomes '11 (binary 3)'
 - The output is 10 if $D_2=1$, provided that $D_3=0$

Truth Table of Priority Encoder


Inputs				Outputs		
D_3	D_2	D_1	D_0	A_1	A_0	V
0	0	0	0	X	X	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1

 


Simplification using map reduction

► Priority Encoder

 - A combinational circuit that implements a priority function
 - Consider the case when input D_3 has the highest priority
 - If $D_3=1$, then output becomes '11 (binary 3)'
 - The output is 10 if $D_2=1$, provided that $D_3=0$



Simplification using map reduction

 

Logic diagram of a 4-input priority encoder

► Selecting

- Selection of information to be used in a computer is a very important function
 - Selection circuits have a set of inputs from which selections are made, a single output, and a set of control lines
 - **Multiplexers** are widely used as selection circuits

► Multiplexer (MUX)

- A multiplexer selects binary information from one of many input lines and directs it to a single output line
 - The selection is governed by 'selection inputs'
 - Normally, there are 2^n input lines with 'n' selection inputs

$$Y = \bar{S}I_0 + SI_1$$

Truth Table for 2-to-1-Line Multiplexer

S	I ₀	I ₁	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

► 4-to-1 Line Multiplexer

- The output Y depends on four inputs I_0 , I_1 , I_2 , and I_3 and two select inputs S_1 and S_0
 - We can form a condensed truth table by putting information variables in the output column
 - Simply, it can be implemented by using two inverters, four 3-input AND gates, and a 4-input OR gate (**gate-input cost: 18**)

Condensed Truth Table for 4-to-1-Line Multiplexer

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

Any different implementations?

$$Y = \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_1 S_0 I_1 + S_1 \bar{S}_0 I_2 + S_1 S_0 I_3$$


► 4-to-1 Line Multiplexer

- A different implementation is obtained by factoring the AND terms
 - Its implementation is combining a 2-to-4 line decoder, four AND gates (enabling circuit), and a 4-input OR gate
 - The resulting circuit has a gate-input cost of 22 (more costly!!)

Condensed Truth Table for 4-to-1-Line Multiplexer


S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3
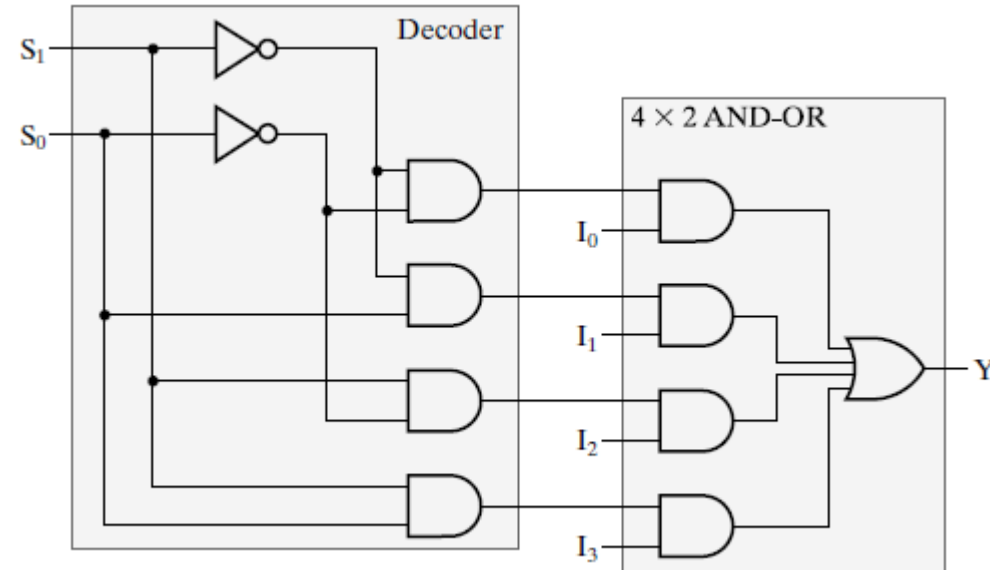
$$Y = (\bar{S}_1 \bar{S}_0)I_0 + (\bar{S}_1 S_0)I_1 + (S_1 \bar{S}_0)I_2 + (S_1 S_0)I_3$$




► 64-to-1 Multiplexer

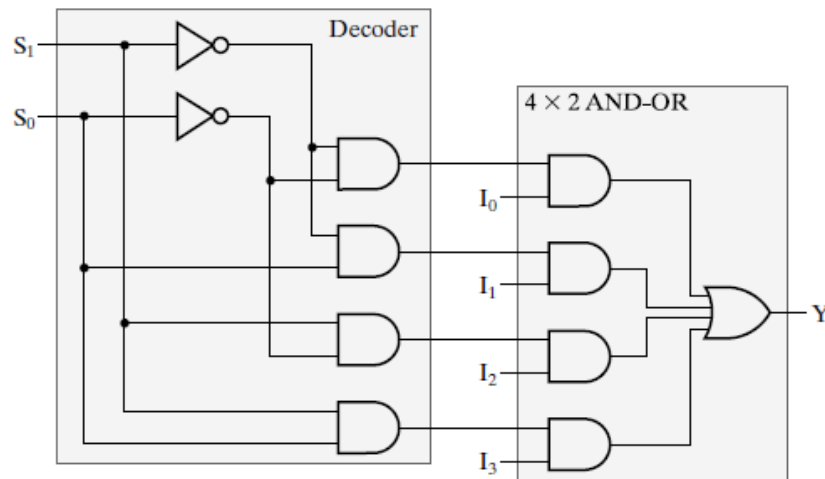- A multiplexer design can be easily expanded to 64-to-1 MUX
 - (6-to-64 decoder) + (64 x 2 AND-OR gate)
 - This structure has a gate-input cost of $183 + 128 + 64 = 374$
 - If this implementation is replaced by inverters and 7-input AND gates, the gate-input cost becomes $6 + 448 + 64 = 518!!$




4-to-1 MUX

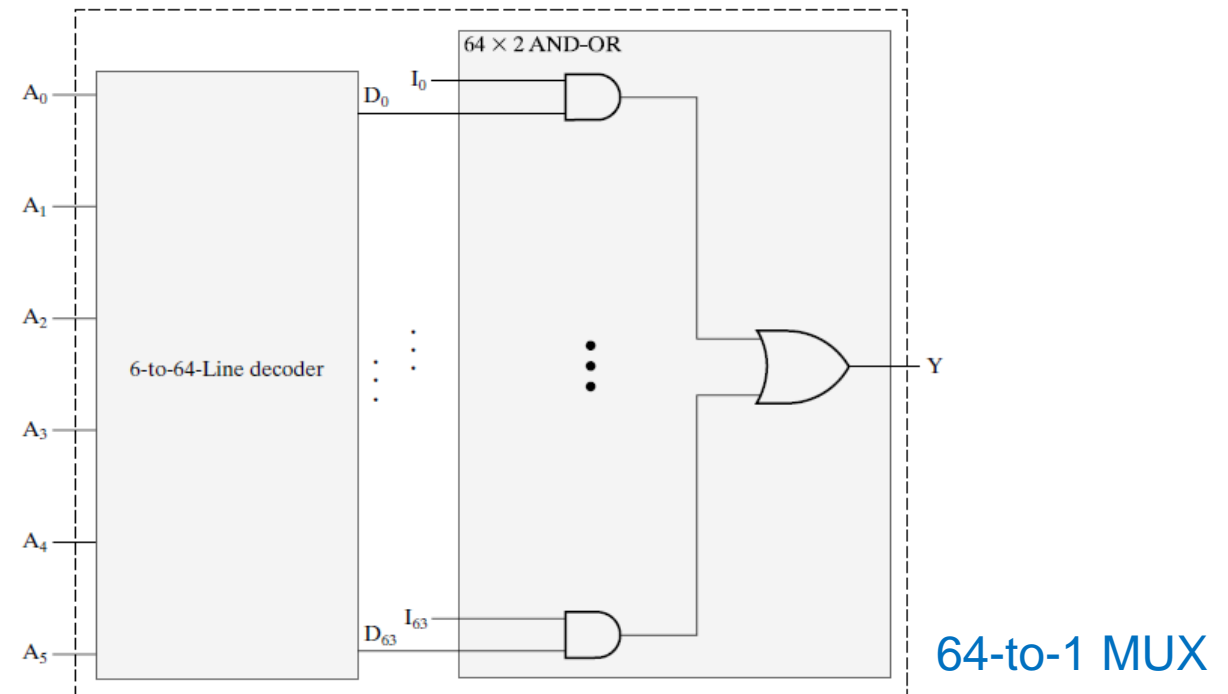


► 4-to-1 Quad Multiplexer

- It has two selection bits and each information input is replaced by a vector of four inputs
- Since the information inputs are a vector, the output Y becomes a four-element vector

Gate-input cost?

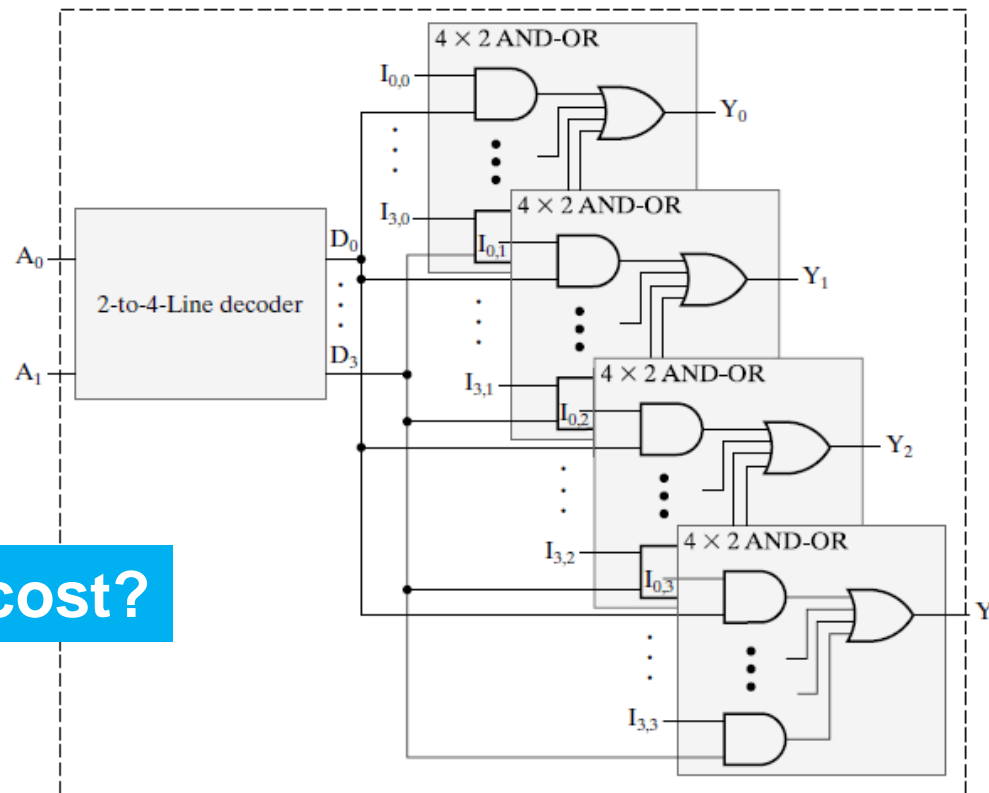

▶ VHDL example – 4 to 1 Multiplexer

 

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux_4to1_top is
    Port ( SEL : in  STD_LOGIC_VECTOR (1 downto 0);    -- select input
          A   : in  STD_LOGIC_VECTOR (3 downto 0);    -- inputs
          X   : out STD_LOGIC);                      -- output
end mux_4to1_top;

architecture Behavioral of mux_4to1_top is
begin
    with SEL select
        X <= A(0) when "00",
              A(1) when "01",
              A(2) when "10",
              A(3) when "11",
              '0'  when others;
end Behavioral;
```

► Design Constraints

- Fan-out

- The number of gate inputs driven by the output of another single logic gate.

- Power Dissipation (Primary design constraint in the last 15 years!)

- As a result of applied voltage and currents flowing through the logics, some power will be dissipated in it in the form of heat.

- Propagation Delay

- Propagation delay is the length of time taken for a signal to reach its destination
 - Wires have an approximate propagation delay of 1 ns for every 6 inches (15 cm) of length. Logic gates can have propagation delays ranging from more than 10 ns down to the picosecond range, depending on the technology being used.

- Noise Margin

- the noise margin is the amount by which the signal exceeds the threshold for a proper '0' or '1'.

► Summary

- There are five-step design procedure in designing a digital circuit
 - Specification, formulation, optimization, technology mapping, verification
 - These steps apply to both **manual** and **computer-aided** design
- We have dealt with functional blocks, combinational circuits that are frequently used to design larger circuits
 - Decoders
 - Encoders
 - Multiplexers