



# Digital Logic Circuit (SE273 – Fall 2020)

## Lecture 5: Arithmetic Functions

Jaesok Yu, Ph.D. (jaesok.yu@dgist.ac.kr)

Assistant Professor  
*Department of Robotics Engineering, DGIST*


# ► Goal

- Continue to focus on functional blocks
  - Specifically, functional blocks that perform arithmetic operations
  - Iterative circuits made up of arrays of combinational cells
  - Complement-based arithmetic (**simplify the design**)

# ► Iterative Combinational Circuits

- The arithmetic blocks are designed to operate on binary input vectors and produce binary output vectors
  - The function implemented often requires the same subfunction be applied to each bit position
  - Thus, a simple functional block can be used repetitively for each bit position

[Array of cells]

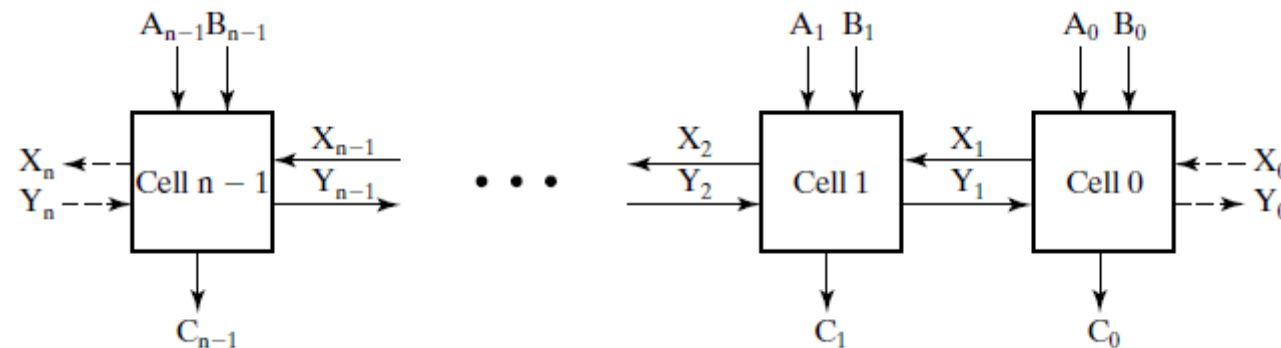

Also, called an iterative array

- [Array of cells]



# ► Binary Adders


- We begin with the simple arithmetic unit that performs the addition of two binary digits
  - Four possible elementary operations:  $0+0=0$ ,  $0+1=1$ ,  $1+0=1$ ,  $1+1=10$
  - The case  $1+1$  requires two bits as an output (otherwise, 1bit is sufficient)
  - Thus, we define the carry and the sum
  - There are two types of binary adders: **half adder** and **full adder**

## ► Half Adder

- A half adder is an arithmetic circuit that generates the sum of two binary digits (augend and addend)
  - We set two output bits: S for “sum” and C for “carry”
  - The Boolean functions for the two outputs are as follows:

Truth Table of Half Adder

Inputs		Outputs	
X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

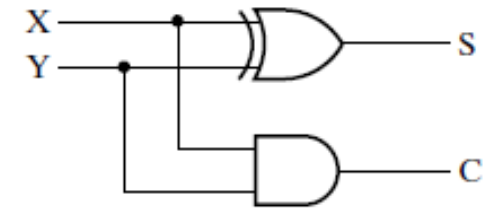



Logic diagram of half adder

# ► Full Adder

- A full adder is a circuit that forms the arithmetic sum of three input bits
  - Two of input variables are X and Y (two bits to be added)
  - The third input, Z, represents **the carry from the previous** lower significant position


Truth Table of Full Adder

Inputs			Outputs	
X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

  
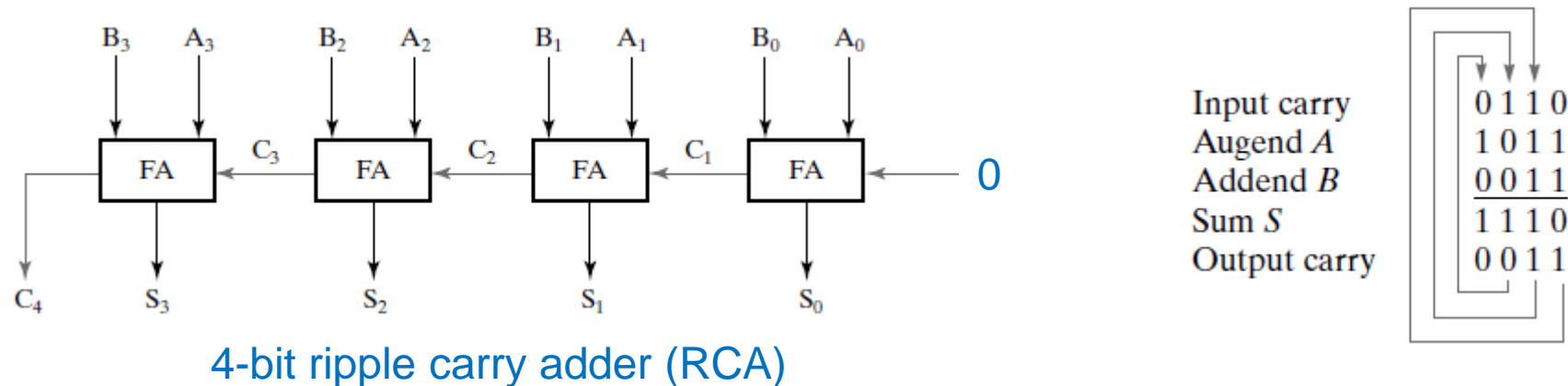
# ► Binary Ripple Carry Adder


- A parallel binary adder is a digital circuit that produces the arithmetic sum of two (binary) numbers
  - It uses 'n' full adders in parallel, with all input bits applied simultaneously
  - They are connected in cascade, with **rippled carry** connections




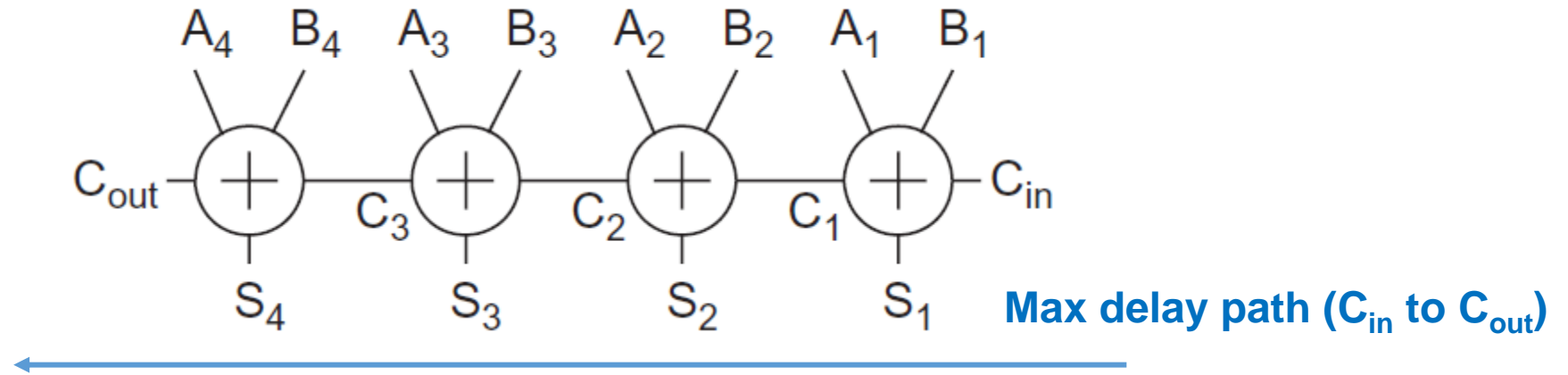
## ► Drawback: Binary Ripple Carry Adder

- The simplest design of multi-bit adder is to connect carry-out of one bit to the carry-in to the next bit




**How to minimize?**

**Delay increases linearly with number of bits:  $t_d = O(N)$**
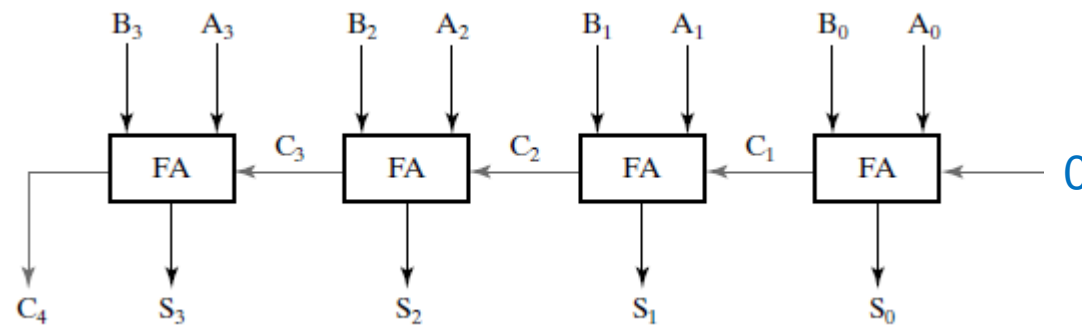
## ► More on Adders

- Prior to moving to the design of efficient multipliers, let's look at a couple of design choices for adders
  - **Ripple Carry** Adder (RCA): the simplest design!
  - Carry **Lookahead** Adder (CLA): it predicts the carry!
  - Carry **Save** Adder (CSA)




4-bit ripple carry adder (RCA)

# ► Carry Lookahead Adder: Useful Definitions

- A fast parallel adder as it reduces the propagation delay
- We first need to understand Carry **P**ropagate and **G**enerate signals
  - Propagate:  $P_i = A_i \oplus B_i$
  - Generate:  $G_i = A_i \cdot B_i$


A	B	C	G	P	C <sub>out</sub>	S
0	0	0	0	0	0	0
		1			0	1
0	1	0	0	1	0	1
		1			1	0
1	0	0	0	1	0	1
		1			1	0
1	1	0	1	0	1	0
		1			1	1

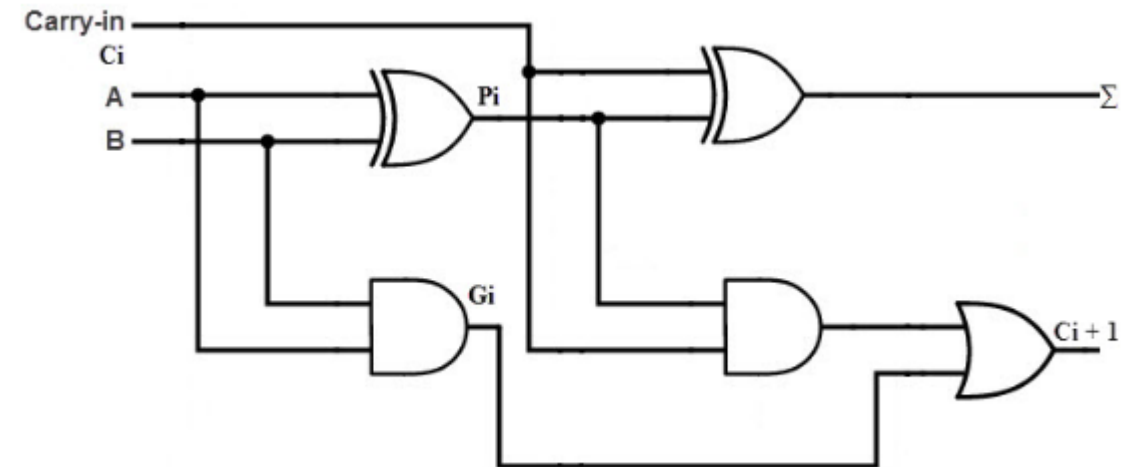
 
# ► Carry Lookahead Adder: $C_{out}$ Boolean Function

- The main idea is to predict internal carry signals by looking at only  $A_i$  and  $B_i$  (+  $C_{in}$ )


- $C_1 = G_0 + P_0 \cdot C_{in}$
- $C_2 = G_1 + P_1 \cdot C_1 = G_1 + P_1 \cdot G_0 + P_1 \cdot P_0 \cdot C_{in}$
- $C_3 = G_2 + P_2 \cdot C_2 = G_2 + P_2 \cdot G_1 + P_2 \cdot P_1 \cdot G_0 + P_2 \cdot P_1 \cdot P_0 \cdot C_{in}$
- $C_4 = G_3 + P_3 \cdot C_3 = ?$



Carry generator for  $C_2$ ,  $C_3$ , and  $C_4$
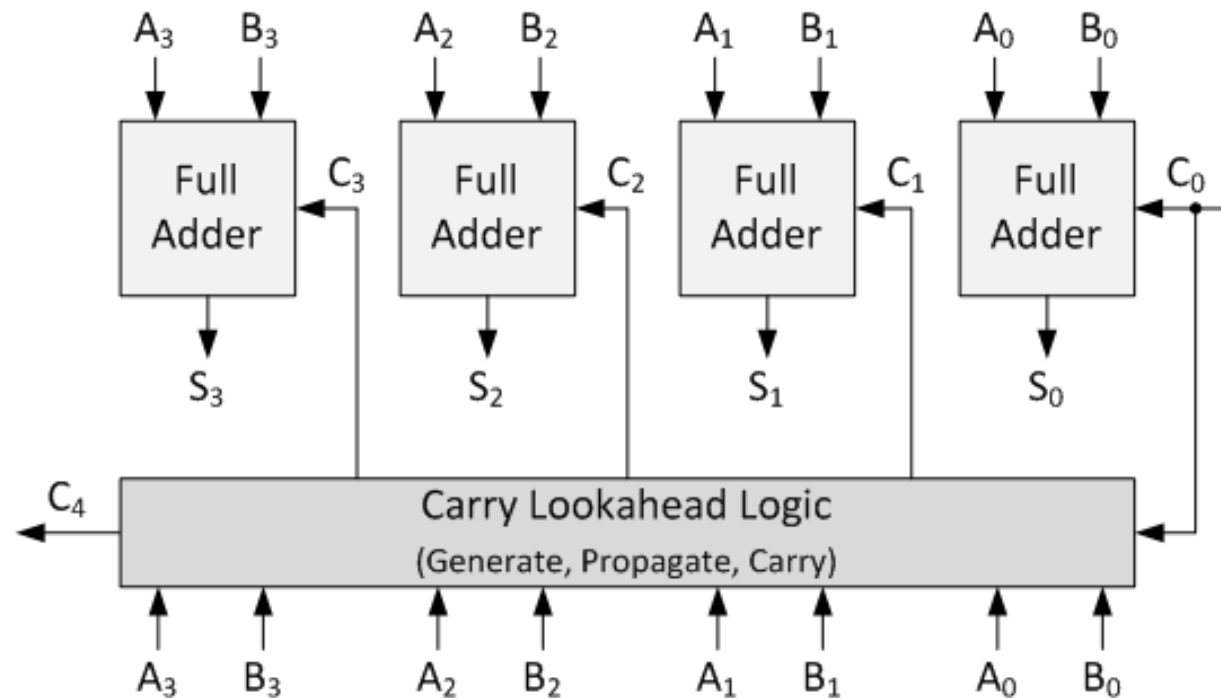
## ► 4-bit Carry Lookahead Adder

- Now, the carry at intermediate nodes can be computed even without waiting for previous FAs complete their computations



# ► Carry Save Adder (CSA)

- In CSA, three bits are added in parallel at a time
- Each CSA is simply an independent Full Adder without Carry propagation
- A Parallel Adder is required only at the last stage

$$\begin{array}{r}
 X: \quad 1\ 0\ 0\ 1\ 1 \\
 Y: +\ 1\ 1\ 0\ 0\ 1 \\
 Z: +\ 0\ 1\ 0\ 1\ 1 \\
 \hline
 C: \quad 1\ 1\ 0\ 1\ 1
 \end{array}$$

$$\begin{array}{r}
 X: \quad 1\ 0\ 0\ 1\ 1 \\
 Y: +\ 1\ 1\ 0\ 0\ 1 \\
 Z: +\ 0\ 1\ 0\ 1\ 1 \\
 \hline
 S: \quad 0\ 0\ 0\ 0\ 1
 \end{array}$$


$$\begin{array}{r}
 X: \quad 1\ 0\ 0\ 1\ 1 \\
 Y: +\ 1\ 1\ 0\ 0\ 1 \\
 Z: +\ 0\ 1\ 0\ 1\ 1 \\
 \hline
 S: \quad 0\ 0\ 0\ 0\ 1 \\
 C: +1\ 1\ 0\ 1\ 1 \\
 \hline
 1\ 1\ 0\ 1\ 1\ 1
 \end{array}$$

A set of full adders generate  
Carry and Sum bits in parallel

The Sum and Carry vectors are added  
at the last stage (with proper shifting)
 
## ► Carry Save Adder (CSA)

- In CSA, three bits are added in parallel at a time
  - The carry is not propagated through stages





# ► Carry Save Adder (CSA)


- Benefit for adding  $m$  Numbers

$n = 4$

$n = 3$

 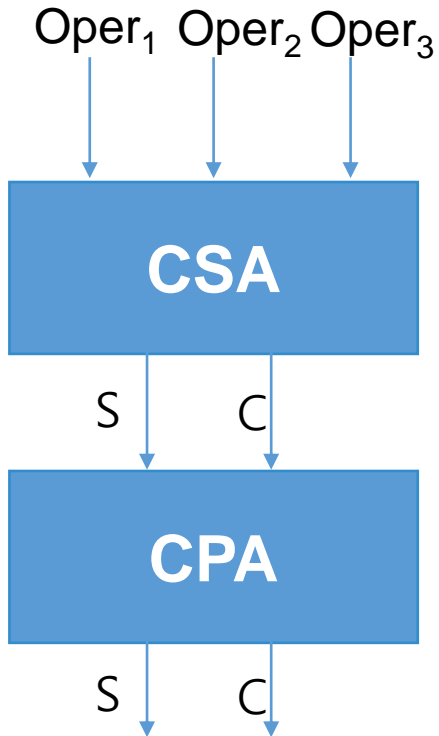





$n = 6$

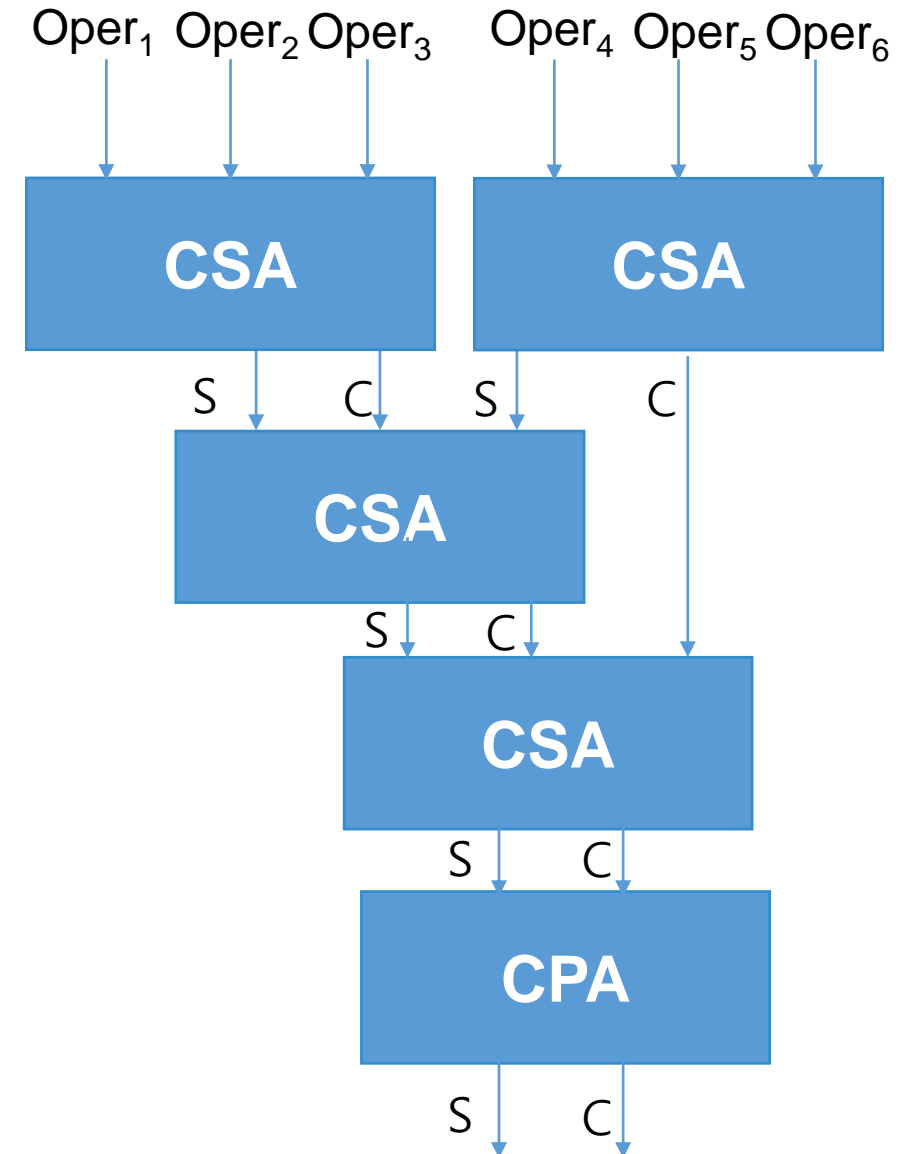


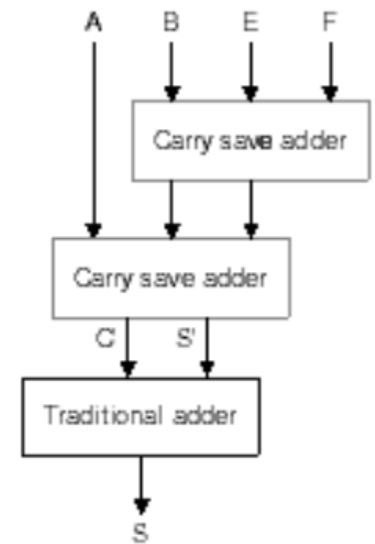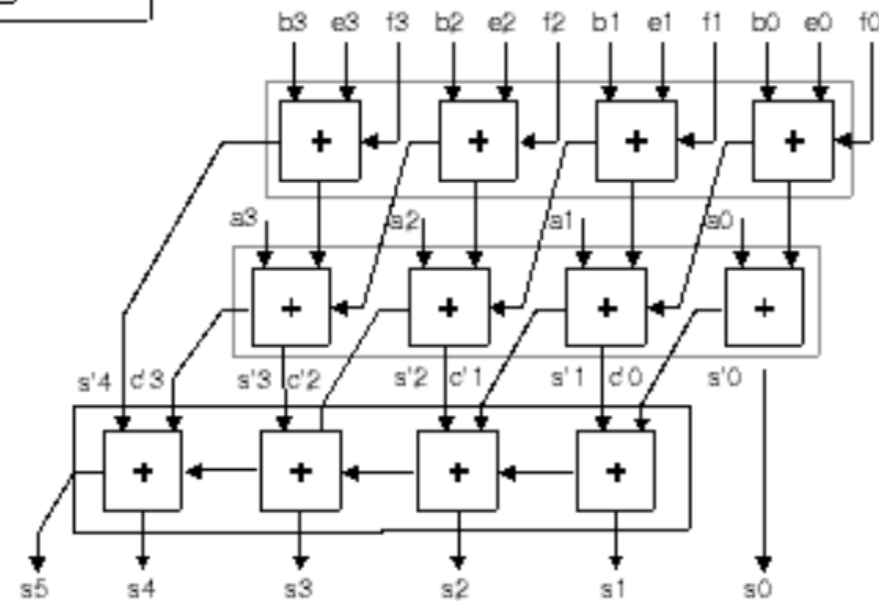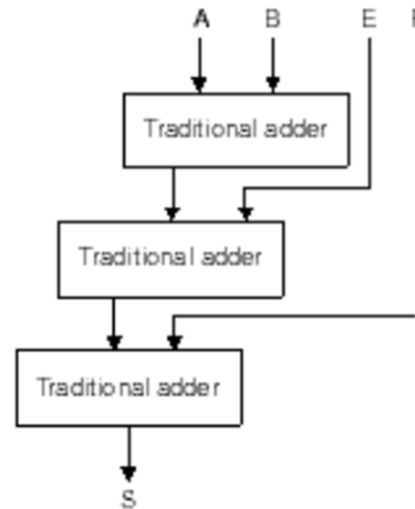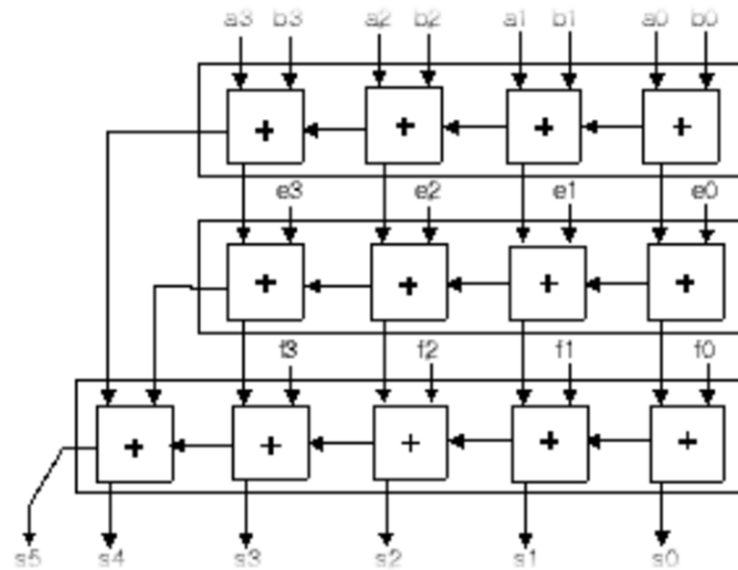
# ► Critical Path Delay

- Let's briefly compare critical path delay RCA and CSA



# ▶ Binary Subtraction

- Let's consider the subtraction of unsigned binary numbers
  - It is used in signed-magnitude addition and subtraction algorithms
  - Later we will compare it with the complement arithmetic

Borrows into:	11100	
Minuend:	10011	
Subtrahend:	<u>-11110</u>	
Difference:	10101	$M - N + 2^n$
Correct Difference:	-01011	$2^n - (M - N + 2^n) = N - M$

If **borrow occurs** into the MSB, it means that **minuend is smaller** than subtrahend

Then, the result must be negative!

# ▶ Two's Complement (Subtraction in Binary System)

- Subtraction of a binary number from  $2^n$  to obtain an  $n$ -digit result is called taking the 2s complement of the number
  - The subtraction of two  $n$ -digit numbers in base 2 is as follows:

1. Subtract the subtrahend  $N$  from the minuend  $M$ .
2. If no end borrow occurs, then  $M \geq N$ , and the result is nonnegative and correct.
3. If an end borrow occurs, then  $N > M$ , and the difference,  $M - N + 2^n$ , is subtracted from  $2^n$ , and a minus sign is appended to the result.



Taking 2s complement of  $M - N + 2^n$

# ▶ Example: Unsigned Binary Subtraction

- Perform binary subtraction  $01100100 - 10010110$

Borrows into:


Minuend:  $01100100$

Subtrahend:  $- \underline{10010110}$

Initial Result
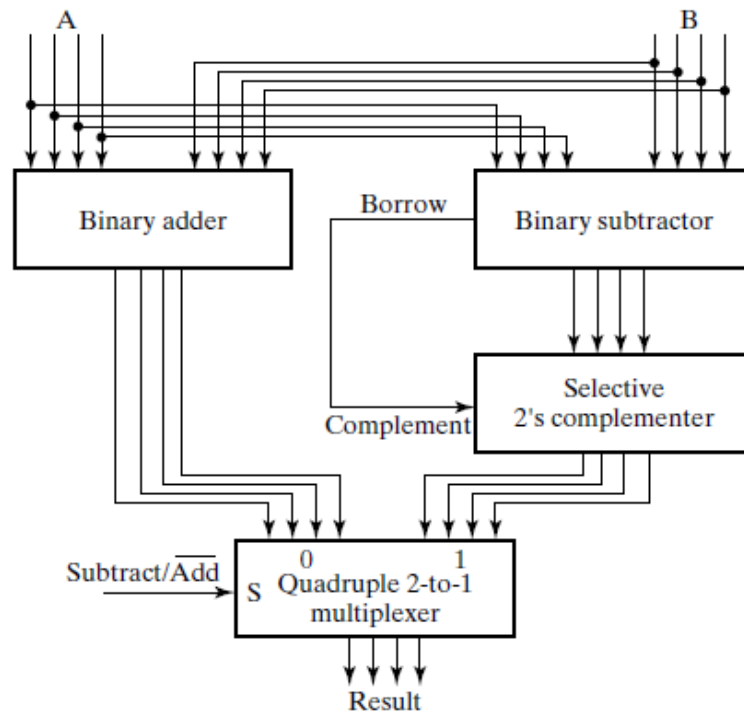
# ► Binary Adder-Subtractor

- As a general arithmetic unit, we can design binary adder-subtractor
  - The inputs are applied to both adder and subtractor
  - Both operations are performed in parallel



If an **end borrow value of 1 occurs** in subtraction, then the selective **2's complementer is activated**

This circuit is more complex than necessary  
**Later, we will see how to share logic btw adder and subtractor**

# ► Complements

- There are two types of complements for base-r system
  - The radix complement: **r's complement**
  - The diminished radix complement: **(r-1)'s complement**
  - For binary number system, 2's complement and 1's complement exist

## 1's complement

$$(2^n - 1) - N$$

→ Subtract each digit from 1

The 1's complement of 1011001 is 0100110.

The 1's complement of 0001111 is 1110000.

## 2's complement

$$2^n - N \text{ for } N \neq 0$$

$$0 \text{ for } N = 0$$

→ Add 1 to the 1's complement

# ► Subtraction Using 2s Complement

## • Now, let's perform subtraction armed with complements

- Add 2s complement of the subtrahend (N) to minuend (M)
  - $M + (2^n - N) = M - N + 2^n$
- If  $M \geq N$ , the sum produces an end carry  $2^n$ . Discard the end carry.
- If  $M < N$ , the sum does not produce an end carry. Perform a correction, **taking the 2s complement** of the sum and **placing a minus sign**

X = 1010100

Y = 1000011

X - Y

X = 1010100

2s complement of Y = 0111101

Sum = 10010001

Discard end carry  $2^7 = -\underline{10000000}$

Answer:  $X - Y = 0010001$

Y - X

2s complement of X = 0101100

Sum = 1101111

There is no end carry.

Answer:  $Y - X = -(2s \text{ complement of } 1101111) = -0010001$

# ▶ Recap: 2's complement

- Representation of signed integer
- ex) Representation of “-7”

0111



1000



1001

Step 1: Positive number  
(= 7)

Step 2: Take a 1's complement  
(Invert each bit)

Step 3: +1 (if negative)  
2's Complement

Bit pattern: 1000 1001 1010 1011 1100 1101 1110 1111 0000 0001 0010 0011 0100 0101 0110 0111

1's complement: -7 -6 -5 -4 -3 -2 -1 0 0 1 2 3 4 5 6 7

2's complement: -8 -7 -6 -5 -4 -3 -2 -1 0 1 2 3 4 5 6 7


- Why? > Faster (in perspective of the hardware)



# ► Recap: 2's complement

- Representation of signed integer

N=4

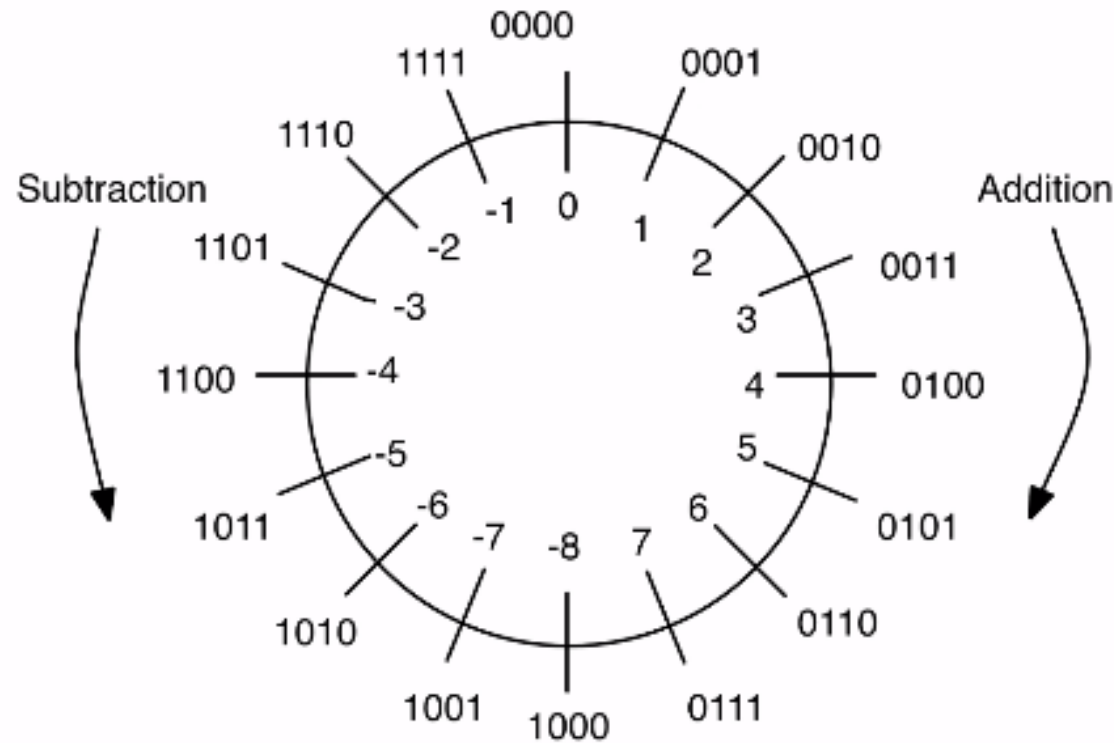

**Bit pattern:** 1000 1001 1010 1011 1100 1101 1110 1111 0000 0001 0010 0011 0100 0101 0110 0111

**1's complement:** -7 -6 -5 -4 -3 -2 -1 0 0 1 2 3 4 5 6 7

**2's complement:** -8 -7 -6 -5 -4 -3 -2 -1 0 1 2 3 4 5 6 7

# ▶ Recap: 2's complement

- ex) Subtraction 6-3

Case 1: 6 - 3

$$\begin{array}{r}
 \begin{array}{|c|c|c|c|} \hline 0 & 1 & 1 & 0 \\ \hline \end{array} \\
 - \begin{array}{|c|c|c|c|} \hline 0 & 0 & 1 & 1 \\ \hline \end{array} \\
 \hline
 \begin{array}{|c|c|c|c|} \hline 0 & 0 & 1 & 1 \\ \hline \end{array}
 \end{array}$$

Case 2: 6+(-3) by 2's complement

$$\begin{array}{r}
 \begin{array}{|c|c|c|c|} \hline 0 & 1 & 1 & 0 \\ \hline \end{array} \\
 + \begin{array}{|c|c|c|c|} \hline 1 & 1 & 0 & 1 \\ \hline \end{array} \\
 \hline
 \begin{array}{|c|c|c|c|} \hline 0 & 0 & 1 & 1 \\ \hline \end{array}
 \end{array}$$

# ► Recap: 2's complement


- ex) Overflow in subtraction

Case 1: -5 - 5

$$\begin{array}{cccc}
 1 & 0 & 1 & 1 \\
 + & 1 & 0 & 1 \\
 \hline
 1 & 0 & 1 & 1 & 0
 \end{array}
 \begin{array}{l}
 -5 \\
 -5 \\
 \\
 6 \text{ (Overflow)}
 \end{array}$$

Overflow

N=4

 

# ► Signed Binary Addition Using 2s Complement

- It does not require comparison or subtraction!
  - Simply add two numbers in signed 2s complement form, and **discard any carry out if happens**

+ 6	00000110	- 6	11111010	+ 6	00000110	- 6	11111010
+ 13	<u>00001101</u>	+ 13	<u>00001101</u>	- 13	<u>11110011</u>	- 13	<u>11110011</u>
+ 19	00010011	+ 7	00000111	- 7	11111001	- 19	11101101

# ▶ Signed Binary Subtraction Using 2s Complement

- The subtraction is simple as well


- Take 2s complement of the subtrahend (including sign bit)
- Add it to the minuend (including sign bit)
- A carry out of the sign bit position is discarded

$\begin{array}{r} -6 \\ -(-13) \\ \hline +7 \end{array}$	$\begin{array}{r} 11111010 \\ -11110011 \\ \hline \end{array}$	$\begin{array}{r} 11111010 \\ +00001101 \\ \hline 00000111 \end{array}$	$\begin{array}{r} +6 \\ -(-13) \\ \hline +19 \end{array}$	$\begin{array}{r} 00000110 \\ -11110011 \\ \hline \end{array}$	$\begin{array}{r} 00000110 \\ +00001101 \\ \hline 00010011 \end{array}$
--	--	---	---	--	---

Then how can we design the adder-subtractor for signed binary numbers (in 2s complement)?
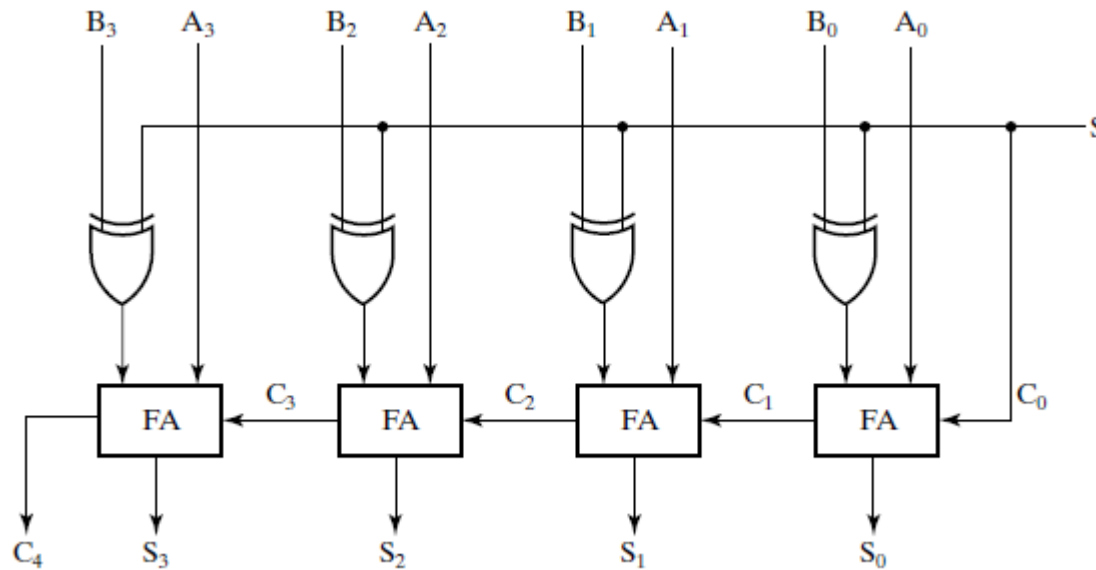
# ► Simplified Binary Adder-Subtractor

- Using 2s complement, we can eliminate the subtraction operation
  - Only the complementer and an adder are needed
  - When performing subtraction, we do complement on the subtrahend



For **subtraction**,  
we need inverters placed btw each B  
and the adder input, then add 1

What is the difference btw  $A \geq B$  and  $A < B$ ?

# ► Signed Binary Numbers

- So far, we considered arithmetic operations on unsigned numbers
  - To represent negative integers, we need a notation for negative values
  - Conventionally, '0' is for positive numbers and '1' is for negative numbers

0	1	0	0	1
---	---	---	---	---

Unsigned binary: 9

Signed binary: +9

Signed-magnitude system!

# ▶ Signed-Magnitude Addition and Subtraction



- For n-bit numbers, we separate the single sign bit and (n-1) magnitude bits for processing
  - Magnitude bits are processed as unsigned binary numbers
  - To avoid correction step in subtraction, we use a **signed-complement** system
  - Either 1s or **2s complement** can be used

Decimal	Signed 2s Complement	Signed Magnitude
+7	0111	0111
+6	0110	0110
+5	0101	0101
+4	0100	0100
+3	0011	0011
+2	0010	0010
+1	0001	0001
+0	0000	0000
-0	—	1000
-1	1111	1001
-2	1110	1010
-3	1101	1011
-4	1100	1100
-5	1011	1101
-6	1010	1110
-7	1001	1111
-8	1000	—


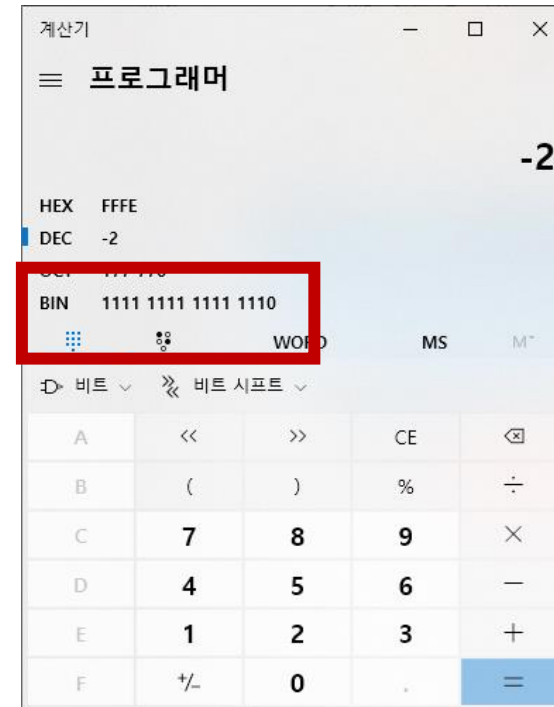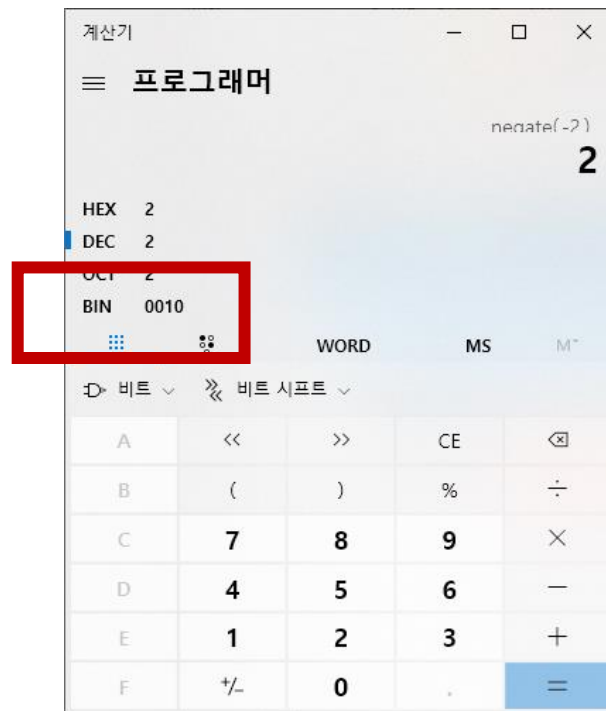
# ► Note on Signed Number System

- It is used in ordinary arithmetic, but is awkward when employed in computer arithmetic
  - Mainly due to separate handling of the sign and the correction step for subtraction
  - Thus, the **signed complement is normally used** in computers



2's complement representation

## ► Overflow

- To obtain the correct answer, we must ensure the result has a sufficient number of bits to accommodate the sum
  - If we add two  $n$ -bit numbers, the sum may occupy  $n+1$  bits (overflow!!)
  - In computers, the number of bits that holds the result is fixed
  - Thus, we need to **detect and handle the overflow**

# ► Overflow in Binary Numbers

- For unsigned numbers,
  - An overflow is detected from the end carry out of the MSB (for addition only)
- For signed numbers,
  - An overflow may occur if two numbers added are both positive or negative
  - Also, overflow may occur for either addition or subtraction

Carries: 0 1

$$\begin{array}{r}
 + 70 \quad 01000110 \\
 + 80 \quad 01010000 \\
 \hline
 + 150 \quad 10010110
 \end{array}$$

Carries: 1 0


$$\begin{array}{r}
 - 70 \quad 10111010 \\
 - 80 \quad 10110000 \\
 \hline
 - 150 \quad 01101010
 \end{array}$$

# ► Overflow Detection

- An overflow can be detected by observing the **carry into** the sign bit position and the **carry out** of the sign bit position
  - If these two carries do not match, an overflow has occurred
  - XOR gate can be used!

Carries: 0 1  
 + 70    0 1000110  
 + 80    0 1010000  
 + 150   1 0010110

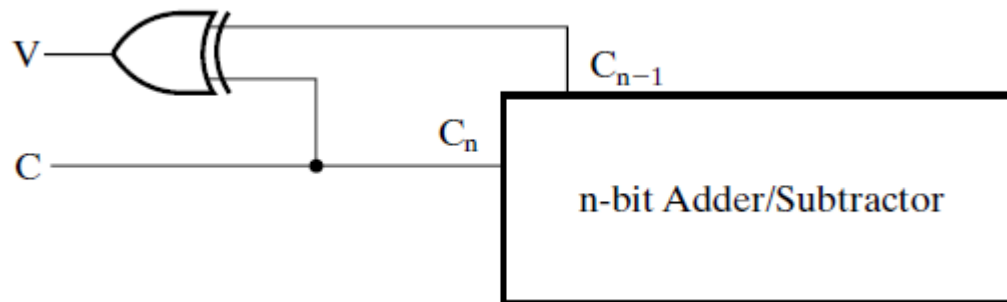Carries: 1 0  
 - 70    1 0111010  
 - 80    1 0110000  
 - 150   0 1101010



What is the use of 'V' and 'C'??