

Digital Logic Circuit (SE273 – Fall 2020)

Lecture 8: Sequential Circuits Design

Jaesok Yu, Ph.D. (jaesok.yu@dgist.ac.kr)

Assistant Professor
Department of Robotics Engineering, DGIST


► Goal

- Learn how to analyze sequential circuits
 - State equations, state table, state diagram
 - Finite state machines
- Learn how to design sequential circuits
 - Sequential circuit design procedure
 - Design sequential circuits in Verilog

► General Digital Systems

• General Digital Systems

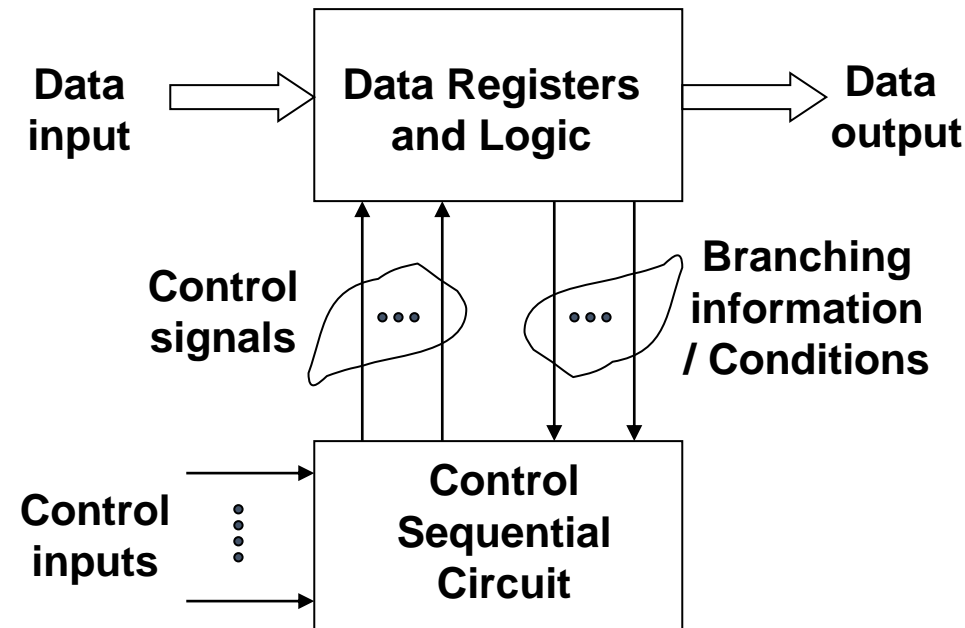- Most digital systems can be partitioned into a control section and data flow section containing registers and logic
 - Data flow section: Register transfer operations > Register-Transfer-Level (RTL) design
 - Digital sequencer > Finite State Machine (FSM)/Algorithmic State Machine (ASM) design



► General Digital Systems

- Model for a general synchronous sequential-logic circuit

Mealy machine


Outputs

$$= f(\text{inputs}, \text{present states})$$



Moore machine

Outputs


$$= f(\text{present states})$$

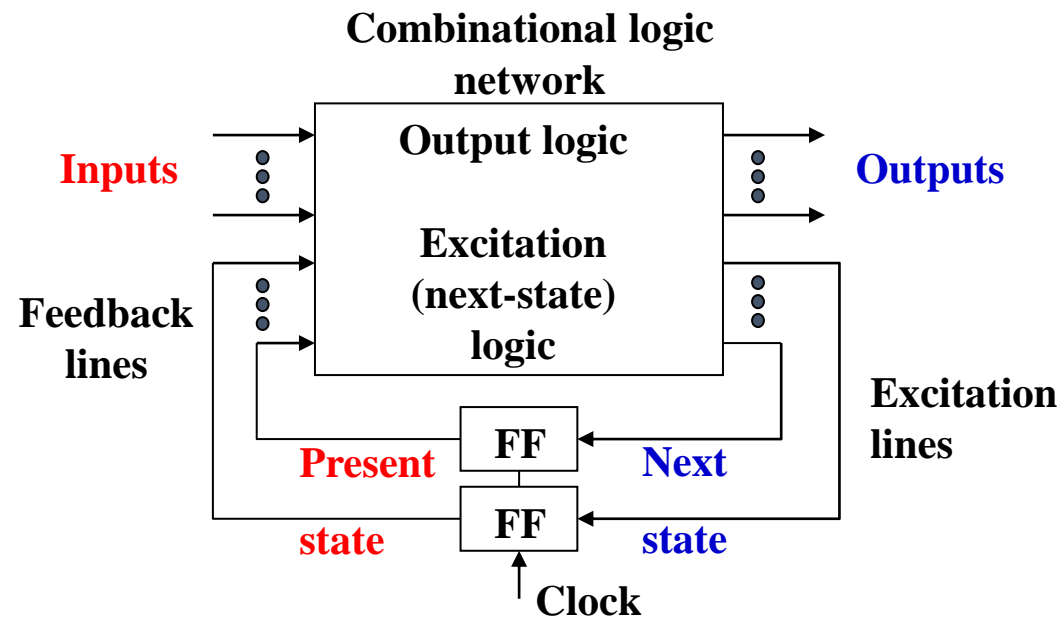

 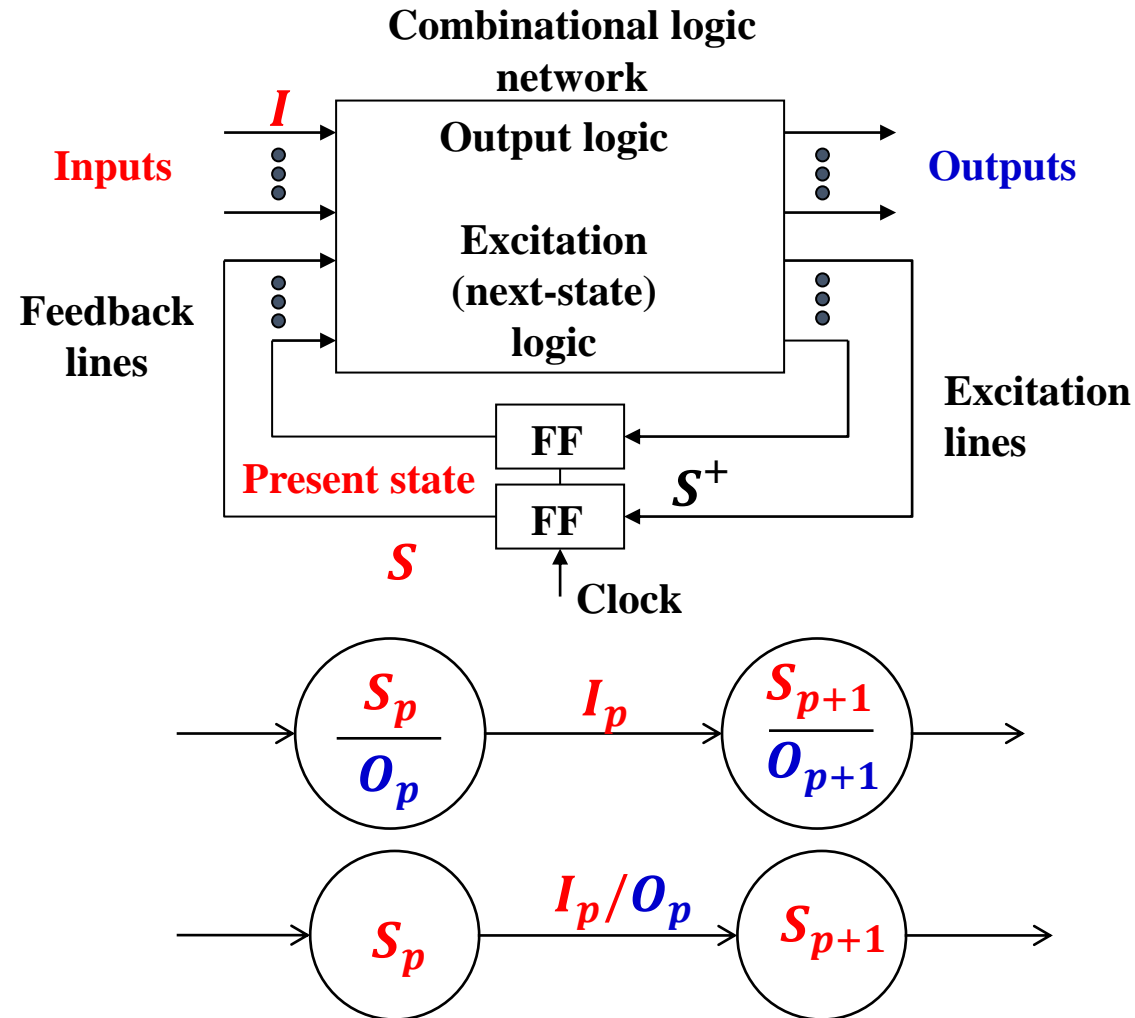▶ Clock cycle and Update of State / Output



▶ Minimum Cycle Time

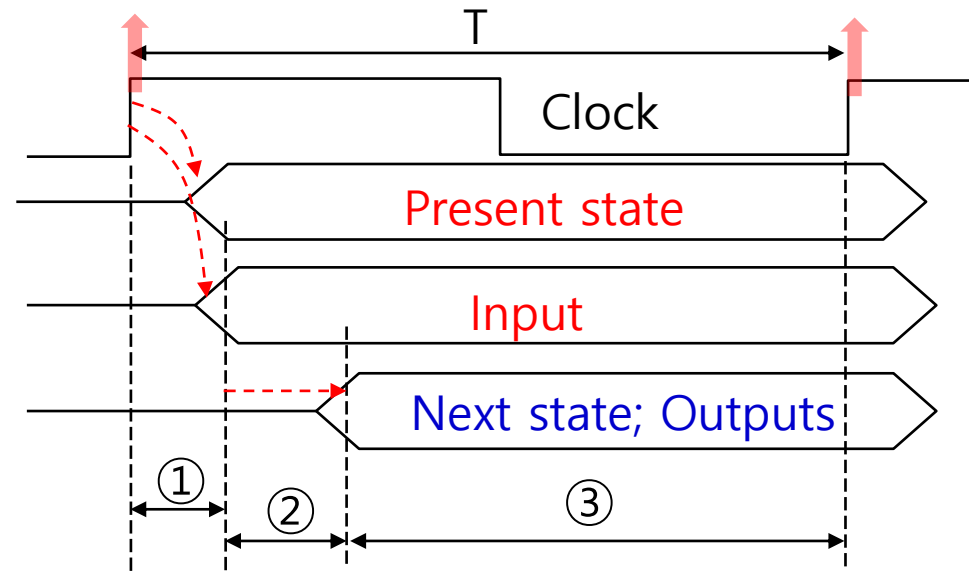


$$T \geq ① + ② + ③$$

① Clock to input stable delay

② Propagation delay of next state generation logic

$$\text{Next state} = f(\text{inputs}, \text{present states})$$


③ Setup time of state memories

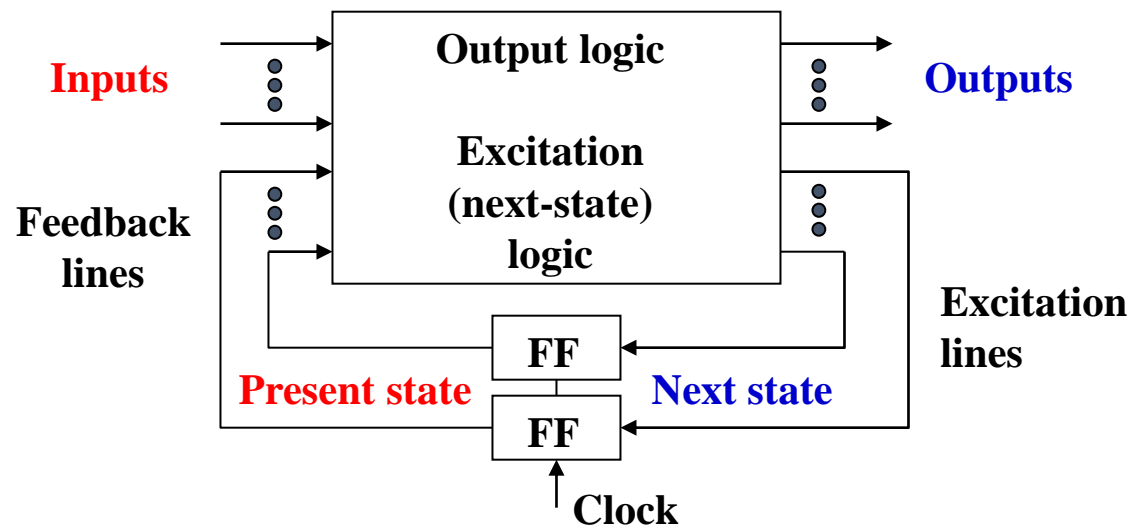

Analysis

► State Equations

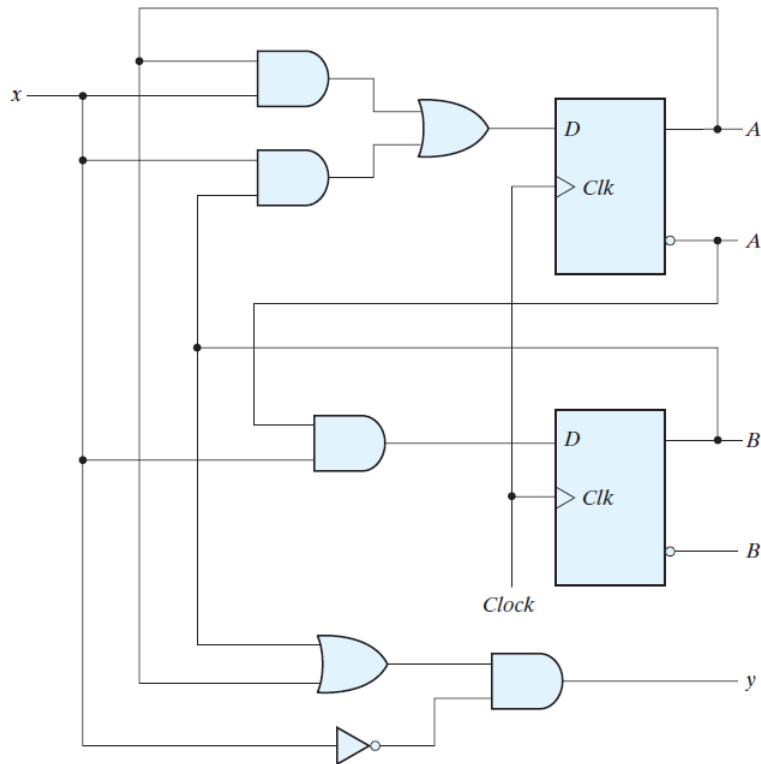
- A clocked sequential circuit can be described by state equations
 - Also called a transition equation
 - It specifies the next state as a function of the present state and inputs



How can we describe this circuit?

► 0 detector

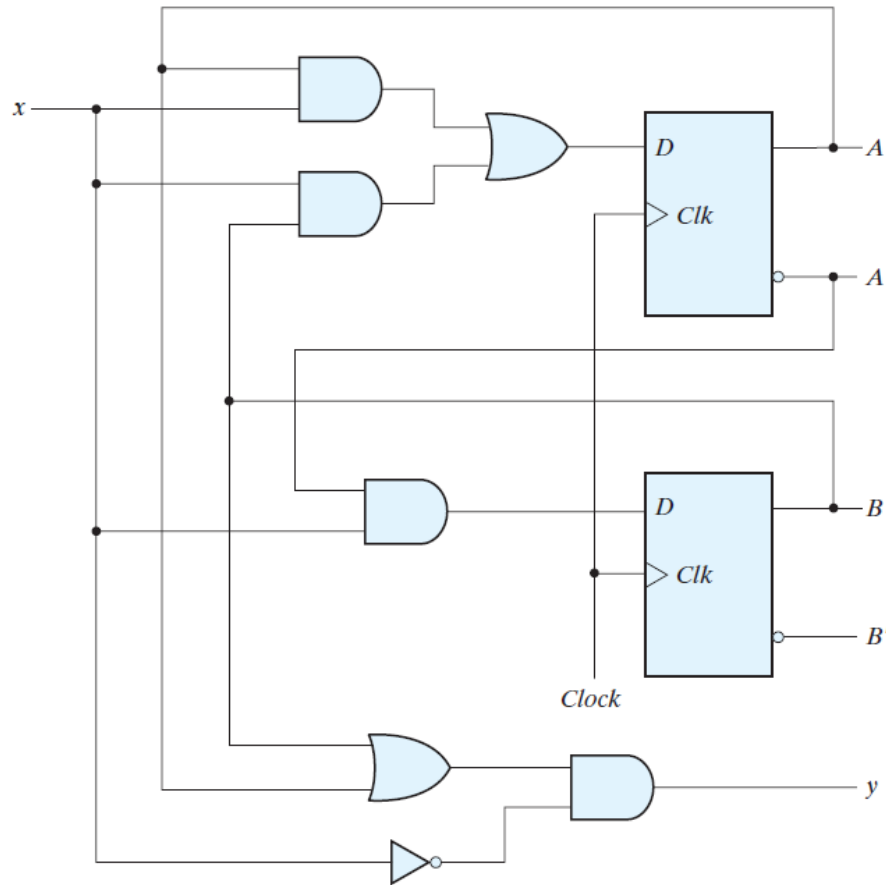- Makes the output 'high' when a 0 is detected in a stream of 1's



$$A(t + 1) = A(t)x(t) + B(t)x(t)$$

$$B(t + 1) = A'(t)x(t)$$

$$y(t) = [A(t) + B(t)]x'(t)$$

► State Table

- The time sequences of inputs, outputs, and FF states can be enumerated in a state table (transition table)

$$A(t+1) = Ax + Bx$$

$$B(t+1) = A'x$$

$$y = Ax' + Bx'$$

Present State		Input x	Next State		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0



Alternative form of a state table

Present State		Next State				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
A	B	A	B	A	B	y	y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

► State Diagram


- We can graphically present the sequential circuit as a state diagram
 - State: circle
 - Directed line: transitions btw states

Present State		Next State				Output	
		$x = 0$		$x = 1$		$x = 0$	$x = 1$
A	B	A	B	A	B	y	y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

  

► Flip-Flop Input Equations

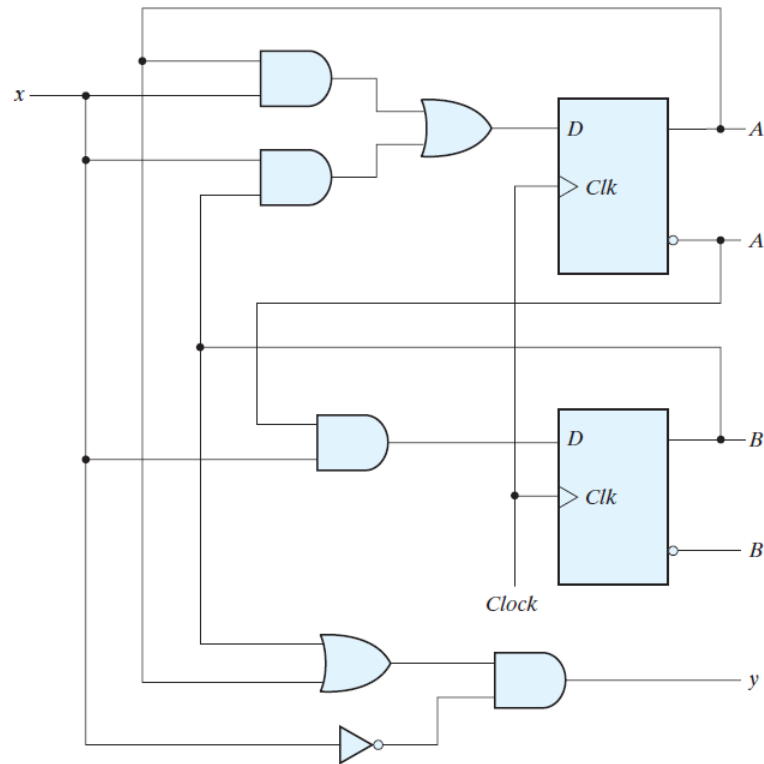- A set of Boolean equations that generates the inputs to FFs
 - Type of flip-flops
 - A list of Boolean equations for combinational circuits



$$D_A = Ax + Bx$$

$$D_B = A'x$$

$$y = (A + B)x'$$

► Analysis with D Flip-Flops



- The circuit we want to analyze is as follows:

$$D_A = A \oplus x \oplus y$$

D_A symbol implies a D FF with output A

State equation is identical to input equation


Present state	Inputs		Next state
A	x	y	A
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

  

► Analysis with JK Flip-Flops

- The circuit we want to analyze is as follows:

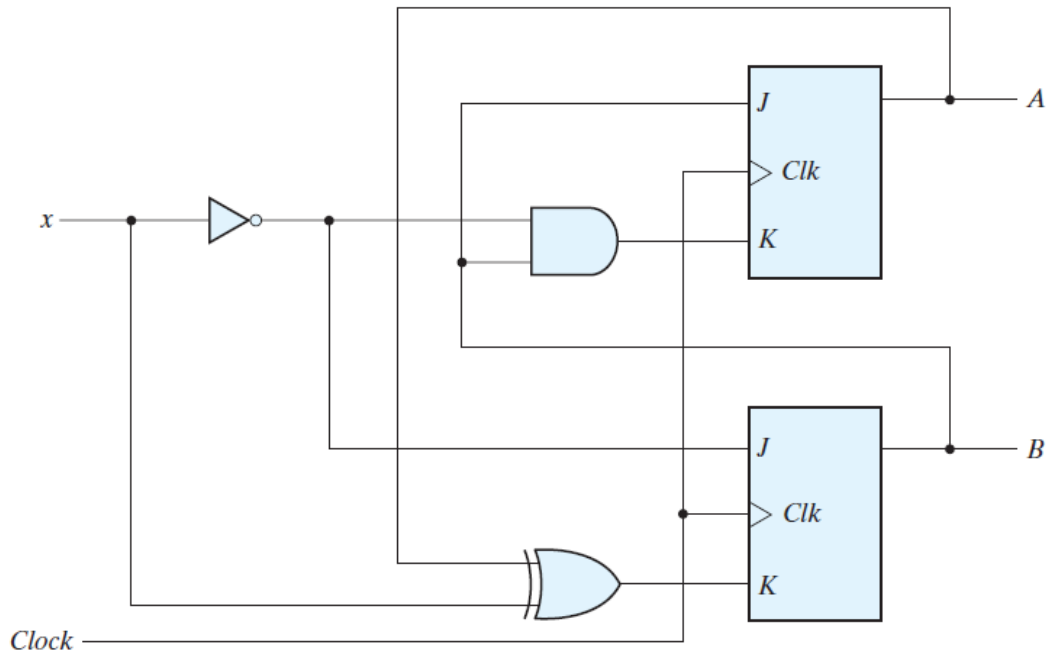Need to refer to the corresponding characteristic table



Present State		Input x	Next State		Flip-Flop Inputs			
A	B		A	B	J_A	K_A	J_B	K_B
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

► Analysis with JK Flip-Flops

- The circuit we want to analyze is as follows:

$$J_A = B \quad K_A = Bx'$$

$$J_B = x' \quad K_B = A'x + Ax' = A \oplus x$$

Present State		Input x	Next State		Flip-Flop Inputs			
A	B		A	B	J_A	K_A	J_B	K_B
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	1	0	0	0

$$A(t + 1) = JA' + K'A$$

$$B(t + 1) = JB' + K'B$$



$$A(t + 1) = A'B + AB' + Ax$$

$$B(t + 1) = B'x' + ABx + A'Bx'$$

► Analysis with T Flip-Flops

- The circuit we want to analyze is as follows:

$$Q(t + 1) = T \oplus Q = T'Q + TQ'$$

 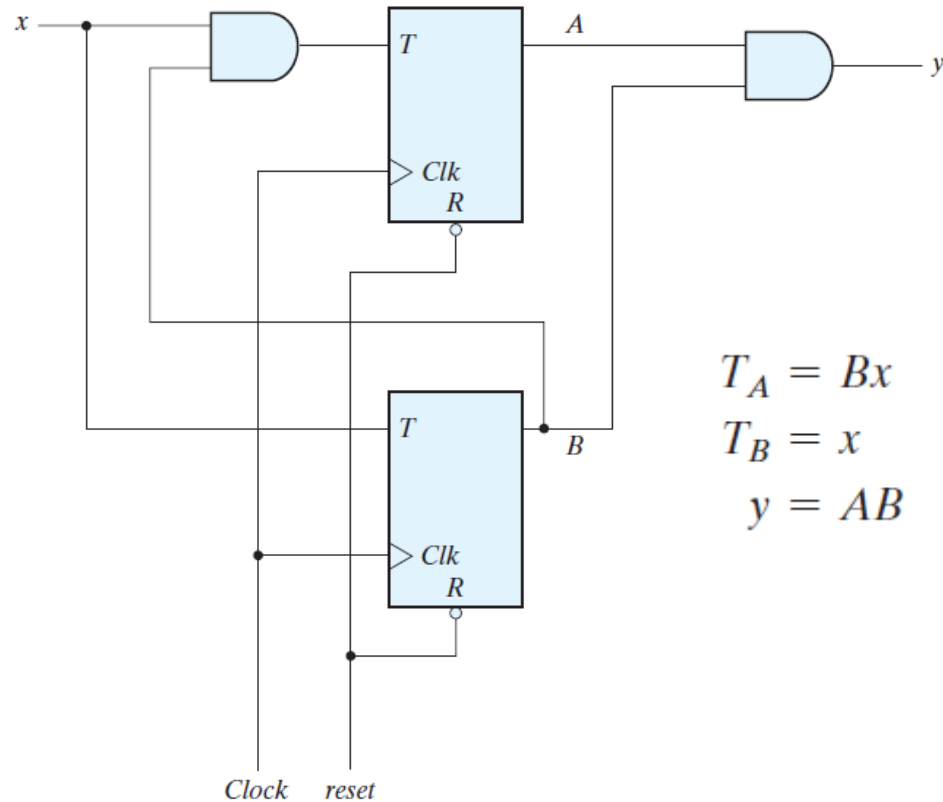


Present State		Input x	Next State		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

► Finite State Machine (FSM)

- There are two types of FSMs (we've already covered)

Example w/ D FF

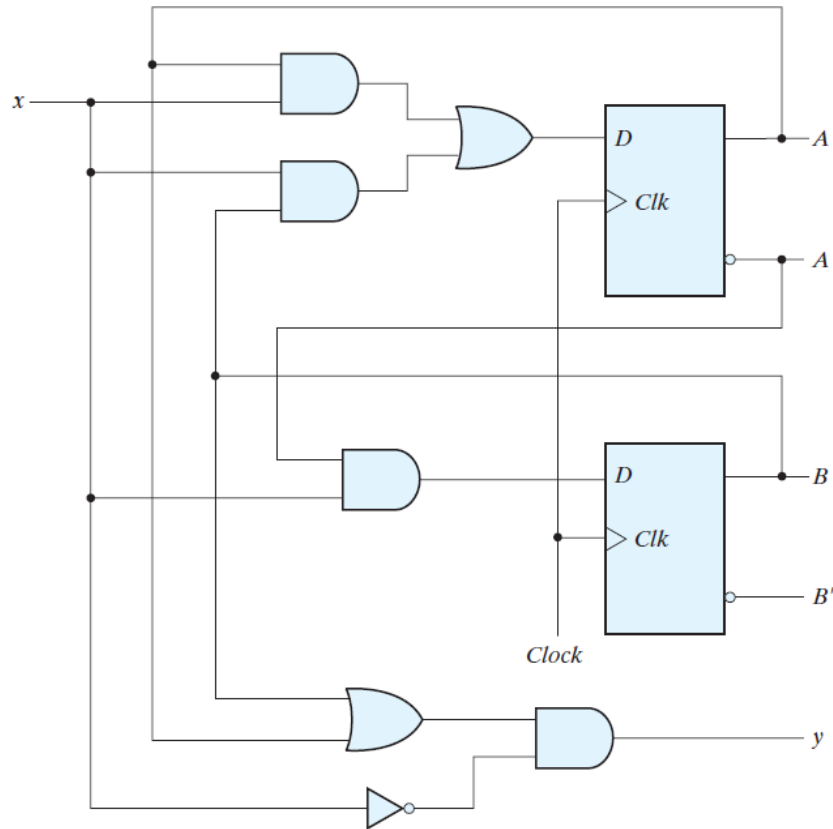


$$D_A = Ax + Bx$$

$$D_B = A'x$$

$$y = (A + B)x'$$

Example w/ T FF

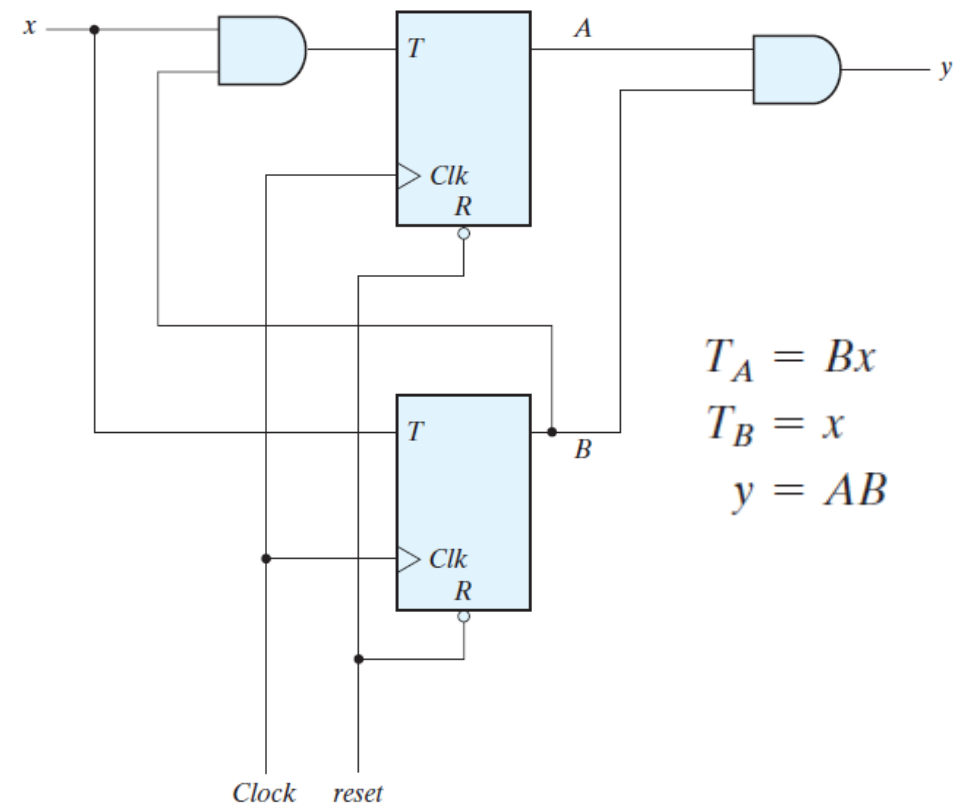

$$T_A = Bx$$

$$T_B = x$$

$$y = AB$$

Design of Sequential Circuits

► Overview of Sequential Circuit Design

- For massive ICs, we rely on automated synthesis tools
 - As a sequential building block, synthesis tools use D flip-flop
 - A sequential circuit **requires a state table** for specification (**or state diagram**)
 - It consists of flip-flops and combinational gates
 - # of FFs = determined by the # of states

► Design Procedure


- A list of recommended steps:

1. From the word description and specifications of the desired operation, derive a state diagram for the circuit.
2. Reduce the number of states if necessary.
3. Assign binary values to the states.
4. Obtain the binary-coded state table.
5. Choose the type of flip-flops to be used.
6. Derive the simplified flip-flop input equations and output equations.
7. Draw the logic diagram.

► State Reduction


- State reduction allows us to design a seq. circuit w/ fewer flip-flops
 - m flip-flops $\rightarrow 2^m$ states
 - But sometimes reduced # of FFs may require more combinational gates to realize its next state and/or output

state	<i>a</i>	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	
input	0	1	0	1	0	
output	0	0	0	0	0	
	<i>e</i>	<i>f</i>	<i>f</i>	<i>g</i>	<i>f</i>	<i>g</i>
	1	1	0	1	0	0
	1	1	0	1	0	0

 

► State Reduction

 - We need the state table for the reduction
 - It is more convenient to look at state table rather than a diagram
 - We look for two present states that **go to the same next state** and **have the same output** for both input combinations



Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>g</i>	<i>f</i>	0	1
<i>g</i>	<i>a</i>	<i>f</i>	0	1

► State Reduction

- We may perform state reduction multiple times

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>f</i>	0	1
<i>e</i>	<i>a</i>	<i>f</i>	0	1
<i>f</i>	<i>e</i>	<i>f</i>	0	1



Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>d</i>	0	1
<i>e</i>	<i>a</i>	<i>d</i>	0	1

Original

state	<i>a</i>	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>f</i>	<i>g</i>	<i>f</i>	<i>g</i>	<i>a</i>
input	0	1	0	1	0	1	1	0	1	0	0	
output	0	0	0	0	0	1	1	0	1	0	0	

Reduced

state	<i>a</i>	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>d</i>	<i>d</i>	<i>e</i>	<i>d</i>	<i>e</i>	<i>a</i>
input	0	1	0	1	0	1	1	0	1	0	0	
output	0	0	0	0	0	1	1	0	1	0	0	

► Design Procedure

- A list of recommended steps:

1. From the word description and specifications of the desired operation, derive a state diagram for the circuit.
2. Reduce the number of states if necessary.
3. Assign binary values to the states.
4. Obtain the binary-coded state table.
5. Choose the type of flip-flops to be used.
6. Derive the simplified flip-flop input equations and output equations.
7. Draw the logic diagram.

► State Assignment

- To design a sequential circuit w/ physical components, it is necessary to assign **unique binary codes** to the states
 - With n bits, we can assign codes to 2^n states

State	Assignment 1, Binary	Assignment 2, Gray Code	Assignment 3, One-Hot
<i>a</i>	000	000	00001
<i>b</i>	001	001	00010
<i>c</i>	010	011	00100
<i>d</i>	011	010	01000
<i>e</i>	100	110	10000



Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
<i>a</i>	<i>a</i>	<i>b</i>	0	0
<i>b</i>	<i>c</i>	<i>d</i>	0	0
<i>c</i>	<i>a</i>	<i>d</i>	0	0
<i>d</i>	<i>e</i>	<i>d</i>	0	1
<i>e</i>	<i>a</i>	<i>d</i>	0	1

Present State	Next State		Output	
	$x = 0$	$x = 1$	$x = 0$	$x = 1$
000	000	001	0	0
001	010	011	0	0
010	000	011	0	0
011	100	011	0	1
100	000	011	0	1


► Design Procedure

- A list of recommended steps:

 1. From the word description and specifications of the desired operation, derive a state diagram for the circuit.
2. Reduce the number of states if necessary.
3. Assign binary values to the states.
4. Obtain the binary-coded state table.
5. Choose the type of flip-flops to be used.
6. Derive the simplified flip-flop input equations and output equations.
7. Draw the logic diagram.

► Synthesis Using D Flip-Flops

- Suppose we wish to design a circuit that detects a sequence of three or more consecutive 1's
 - Input is a serial bit stream
 - We can derive a state table from a given state diagram



State Table for Sequence Detector




Present State		Input <i>x</i>	Next State		Output <i>y</i>
<i>A</i>	<i>B</i>		<i>A</i>	<i>B</i>	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	1	1	1	1

We choose two D flip-flops
(represent four states)

Label outputs as A and B

► Flip-Flop Input Equations w/ D FF

   - It can be obtained directly from the next-state columns of A and B
 - Express in sum-of-minterms form




$$A(t + 1) = D_A(A, B, x) = \Sigma(3, 5, 7) \quad B(t + 1) = D_B(A, B, x) = \Sigma(1, 5, 7)$$

$$y(A, B, x) = \Sigma(6, 7)$$

► Schematic of a Sequence Detector

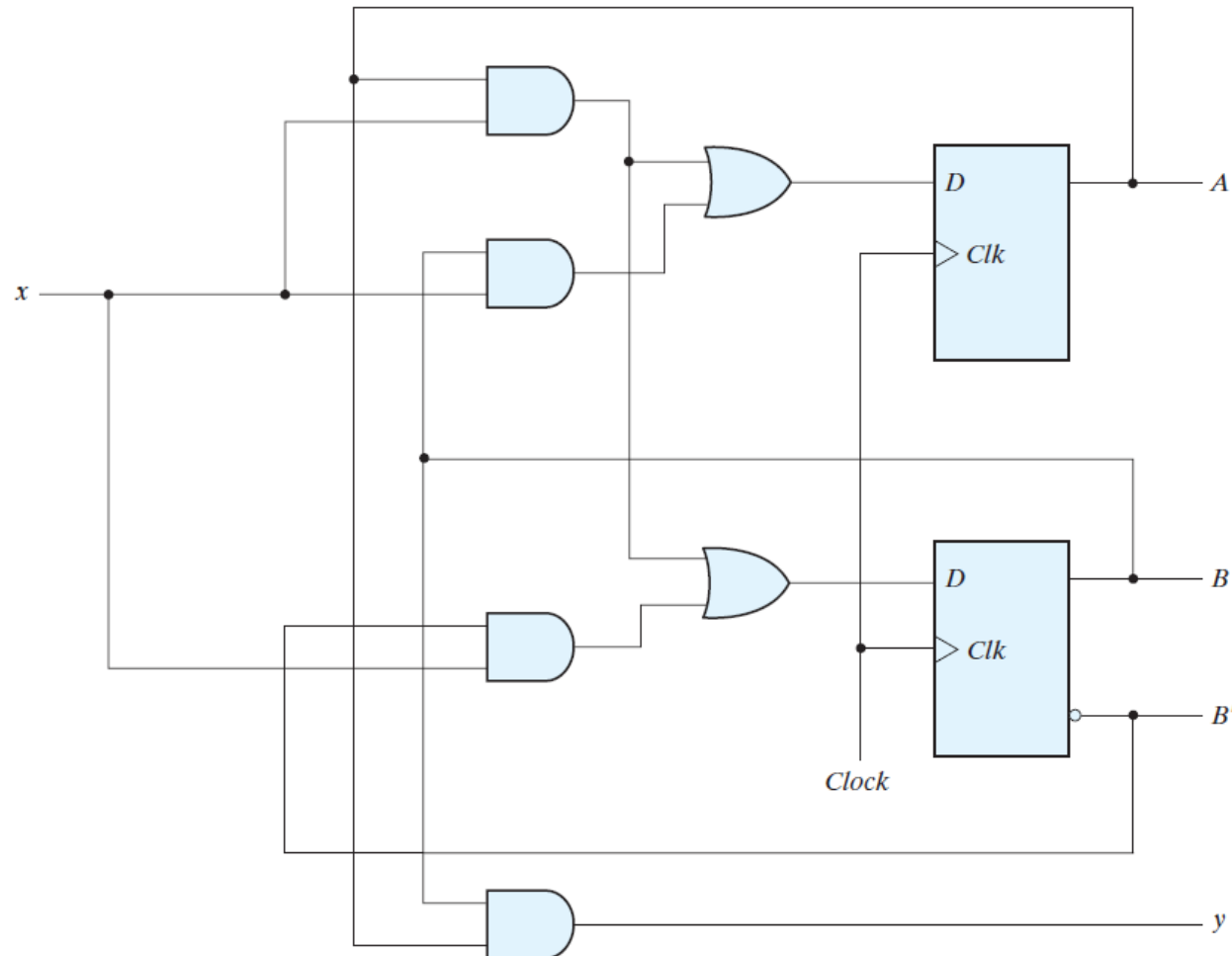- The schematic of the designed sequential circuit is



What type of FSM??

► Synthesis Using JK Flip-Flops

- Manual synthesis procedure for sequential circuits w/ JK flip-flops is the same as with D FFs
 - Except that input equations must be evaluated from the present-state to the next-state transition (excitation table)

FF Excitation Table


$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Present State		Input	Next State		Flip-Flop Inputs			
A	B	x	A	B	J_A	K_A	J_B	K_B
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

► Flip-Flop Input Equations w/ JK FF


- Now, we can derive input equations as a function of present state A, B, and input x

Present State		Input x	Next State		Flip-Flop Inputs			
A	B		A	B	J_A	K_A	J_B	K_B
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

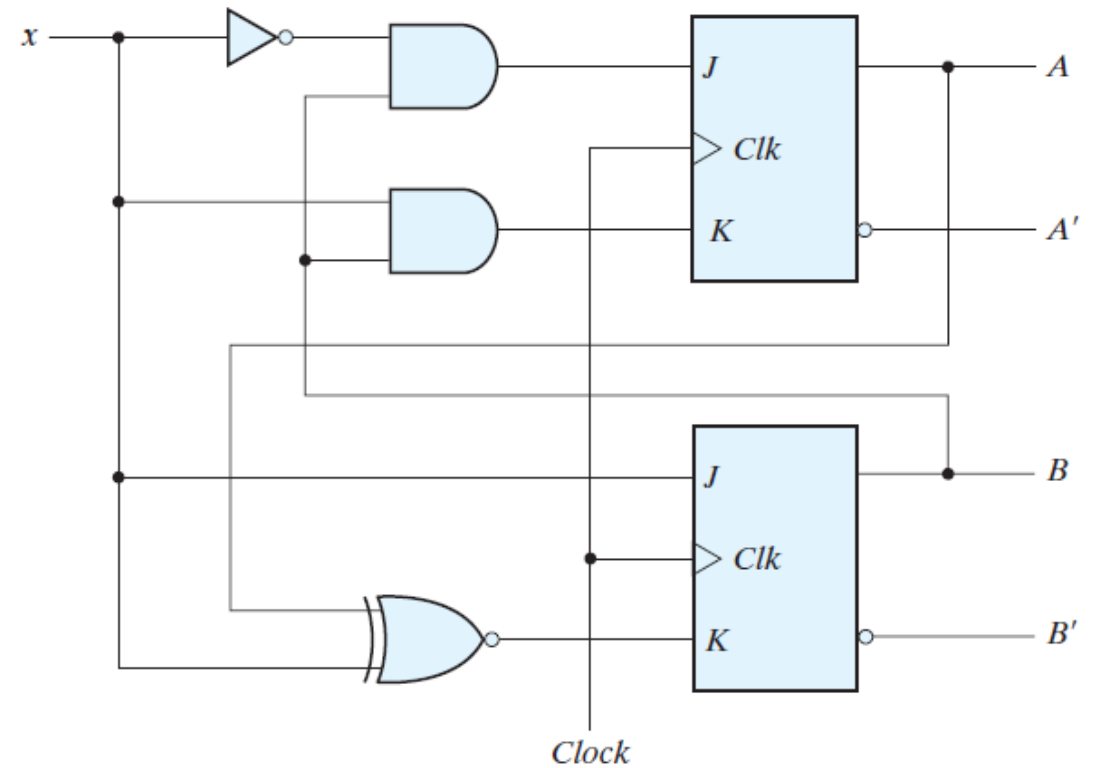


► More example: 111 detector

- Design a 111 detector

 



► More example: 111 detector

 


1. Power on Reset
2. Other conditions: Not defined in any states.
 - Initial state
 - Prevent undefined state
3. Reset to initial or pre-defined state
 - Synchronous reset
 - Asynchronous reset

**Generally
Not
Defined
In the
State diagram**

► More example: 111 detector

  

► Bad design example

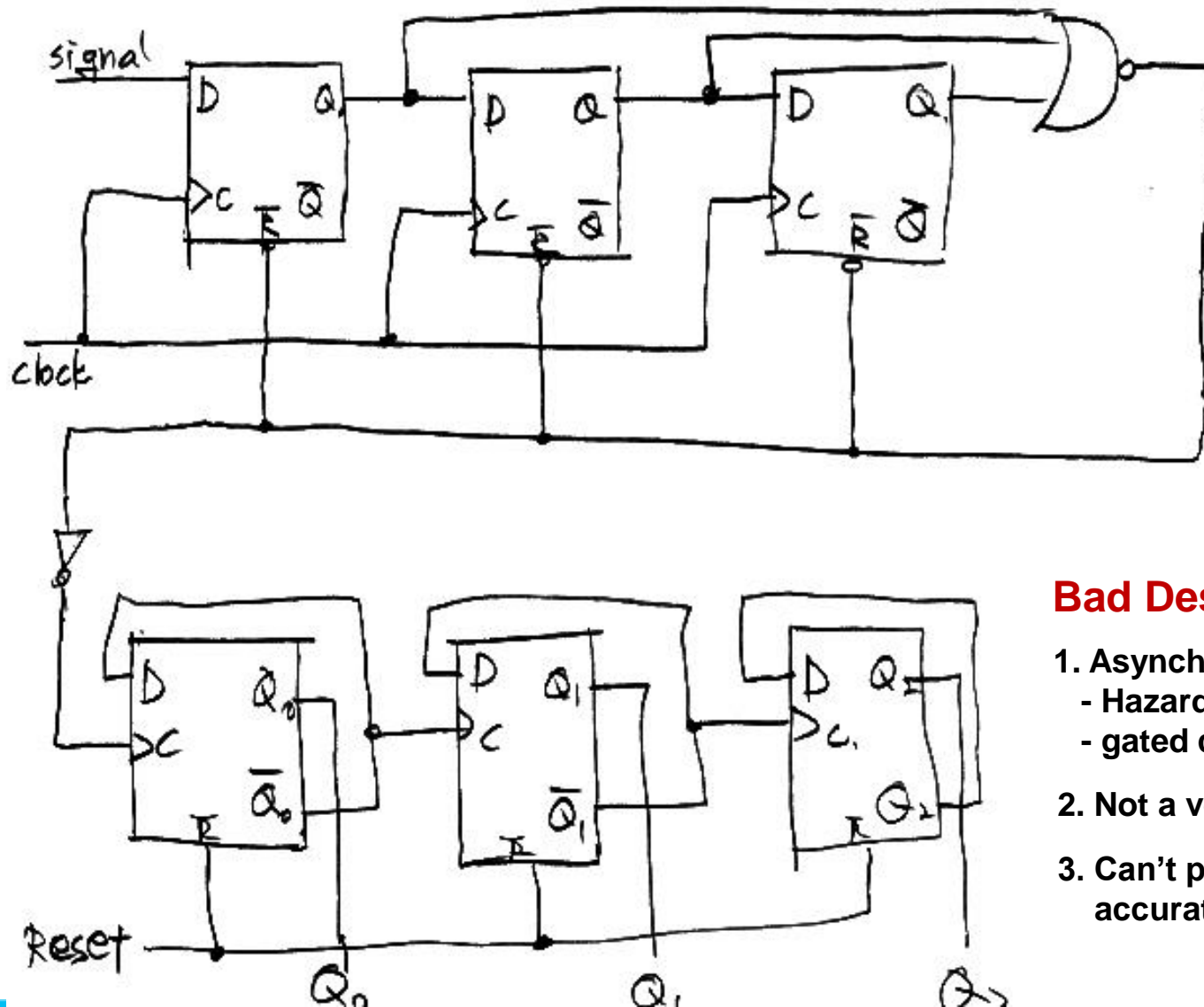


Bad Design Method

 1. Asynchronous design
 - Hazards
 - gated clocks
2. Not a verified design
3. Can't predict the operation accurately

▶ Bad design example

Design verification by checking timing diagram for a test vector



- glitches
- does not work when clock rate is very high
- consecutive 111 patterns are not detected

▶ Design procedure

✓ Draw the state diagram **————→ State table reduction**

✓ Write the state table


✓ Determine the excitation equations



✓ Finish the design

- Output logic
- Excitation logic

► Mealy 111 detector

- State diagram

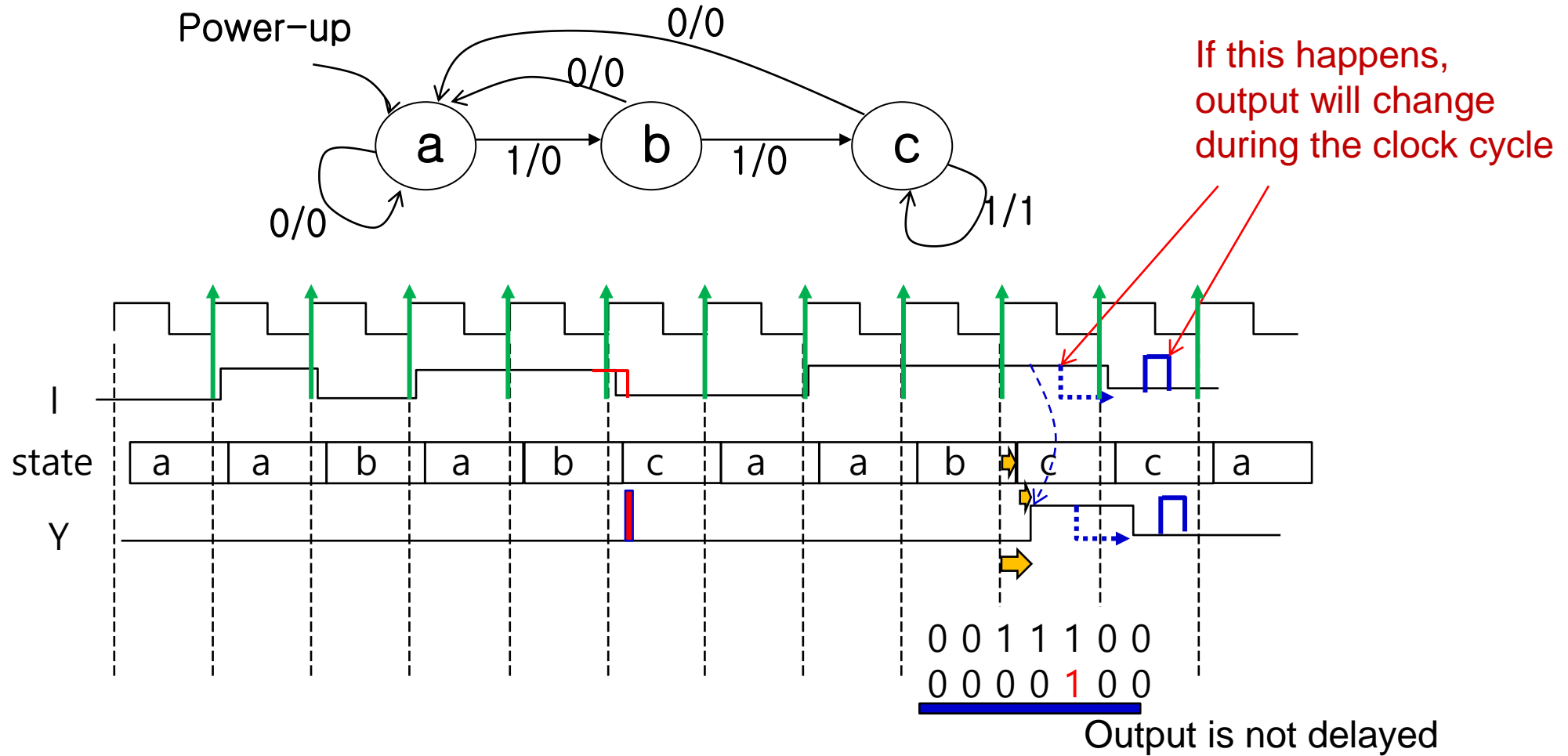

  
$$\begin{array}{ccccccc} 0 & 0 & 1 & 1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ \hline \end{array}$$

Output is stable for a whole clock period even when inputs and other signals change.

Output is delayed by 1 clock cycle

► Moore vs Mealy Machine

- ✓ Outputs depend only on the present state.
- ✓ Easier to design and debug than Mealy machines.
- ✓ But often contain more states than equivalent Mealy machines.
- ✓ No outputs occur during the transition.
- ✓ Cannot respond to an input until the active edge of the clock occurs; this is in contrast to a Mealy circuit.

► Summary

- We learned how to analyze sequential circuits
 - State equations, state table, state diagram
 - Finite state machines: Mealy and Moore machines
- Learned how to design sequential circuits
 - Sequential circuit design procedure
 - Design sequential circuits in Verilog