

Digital Logic Circuit (SE273 – Fall 2020)

Lecture 7: Sequential Circuits

Jaesok Yu, Ph.D. (jaesok.yu@dgist.ac.kr)

Assistant Professor
Department of Robotics Engineering, DGIST


▶ Goal

- Introduce the concept of sequential circuits
 - Sequential circuit definitions
 - Latches, flip-flops
- Different types of latches and flip-flops
 - SR latch, D latch
 - D flip-flop, SR flip-flop, and others

► Combinational vs Sequential


- A combinational circuit:

 - At any time, **outputs depend only on inputs**
 - Changing inputs changes outputs
- No regard for previous inputs
 - **No memory** (history)




► Combinational Adder

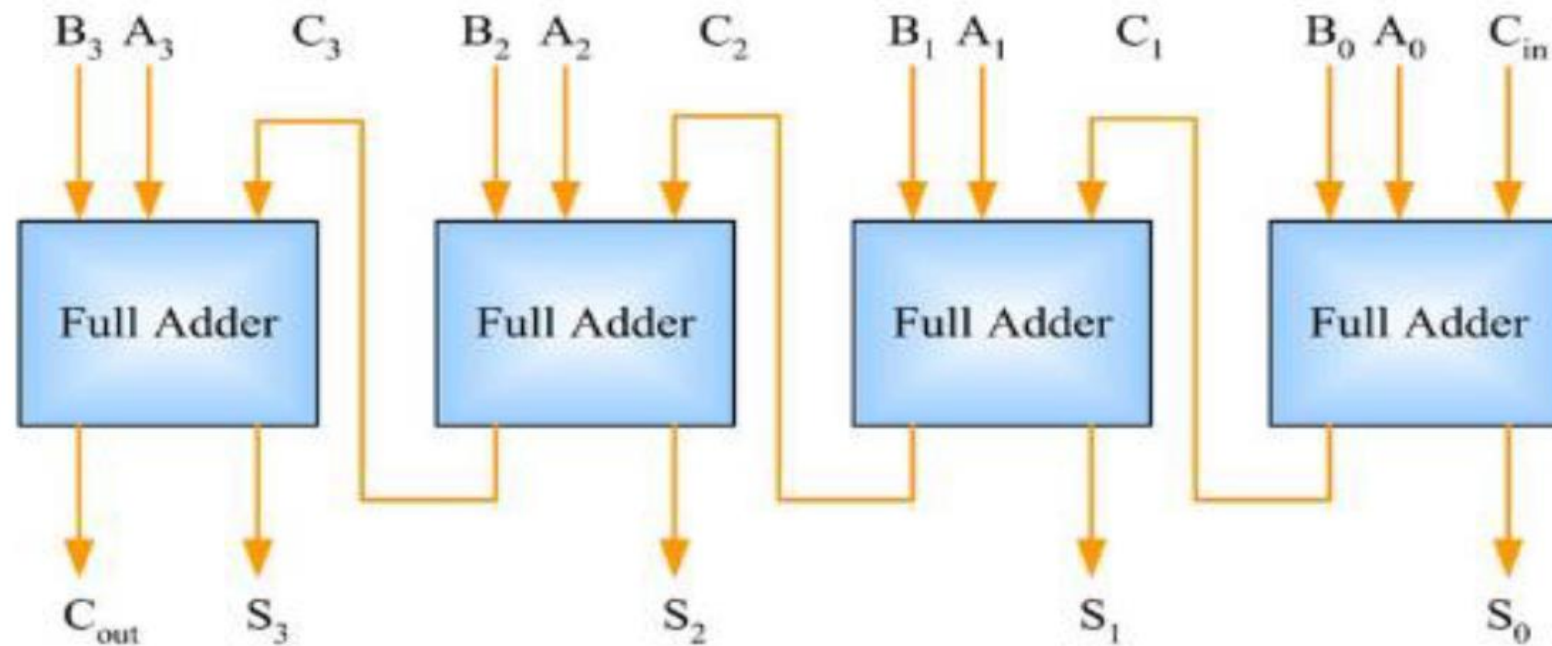- 4-bit adder (ripple carry)
 - Notice how carry-out propagates
 - One adder is active at a time




► Sequential Adder

 - 1-bit memory and two 4-bit memory
 - Only one full-adder!
 - N clocks (four in this case) to get the output
 - **The 1-bit memory defines the circuit state** (0 or 1)



► Sequential Circuits

 - A sequential circuit contains:
 - Storage elements: **latches** or **flip-flops**
 - Combinational logic that implements a multiple-output switching function:
 - **Inputs** are signals from the outside
 - **Outputs** are signals to the outside
 - Other inputs, **State**, are signals from storage elements
 - The remaining outputs, **Next State**, are inputs to storage elements



► Moore vs Mealy machine


Combinatorial Logic

Next state function


Next State = $f(\text{Inputs}, \text{State})$

Output function, two types:

- **Moore**
Outputs = $h(\text{State})$

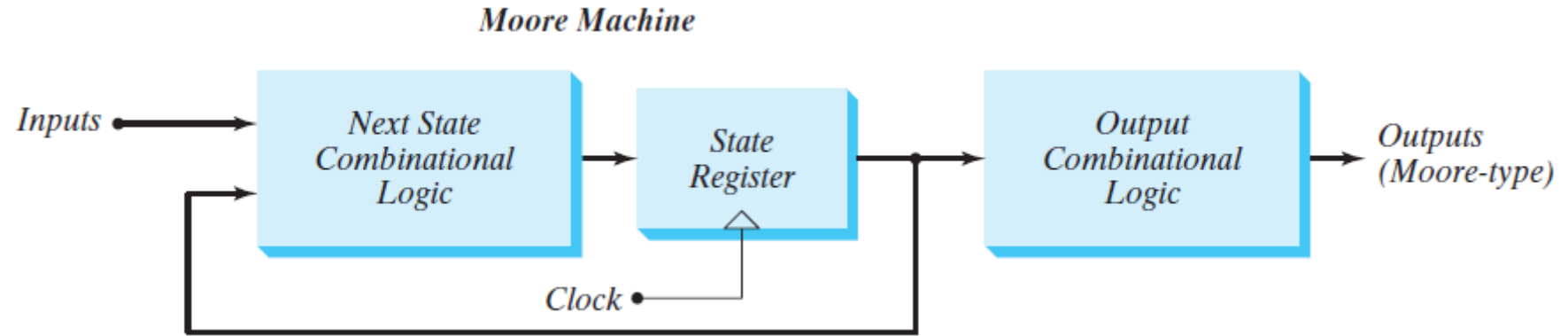

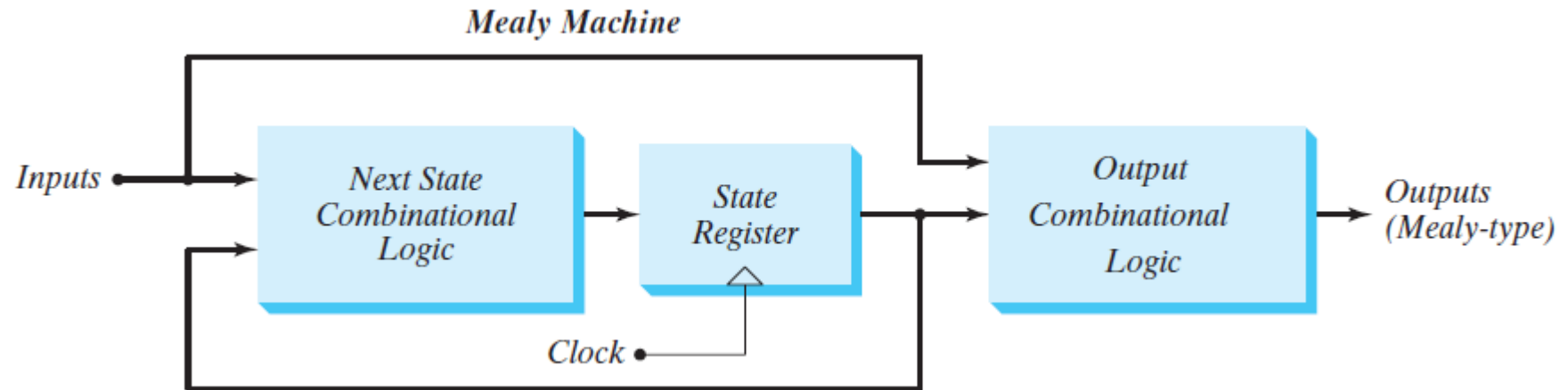- **Mealy**
Outputs = $g(\text{Inputs}, \text{State})$



Output function type depends on specification and affects the design significantly

► Types of Sequential Circuits

- Depends on the times at which:

- Storage elements observe their inputs and change their state


- Synchronous

- Behavior is defined from knowledge of signals **at discrete** instances of time
 - Storage elements observe inputs and can change state only in relation to a timing signal (**clock pulses from a clock**)

► Synchronous vs Asynchronous Design

Typical Processor Circuitry Implementation Comparison
-Design Methodology vs. Clockless/Asynchronous Design Methodology

Synchronous Design

 


Asynchronous Design




▶ Asynchronous vs Synchronous



Asynchronous

 

Synchronous

 

Asynchronous Circuit

  


► Discrete Event Simulation

- In order to understand the time behavior of a sequential circuit, we use **discrete event simulation**
- Rules:
 - Gates modeled by an ideal (instantaneous) function and a **fixed gate delay**
 - Any **change in input values** is evaluated to see if it causes a **change in output value**
 - Changes in output values are scheduled for **the fixed gate delay** after the input change
 - At the time for a scheduled output change, the output value is changed along with **any inputs it derives**

▶ Simulated NAND Gate


 
- Example: a 2-input NAND gate with a 0.5 ns delay
 - Assume A and B have been 1 for a long time
 - At time $t=0$, A changes to 0 & at $t=0.8\text{ns}$, back to 1



t (ns)	A	B	F(I)	F	Comment
$-\infty$	1	1	0	0	$A=B=1$ for a long time
0	$1 \Rightarrow 0$	1	$1 \Leftarrow 0$	0	FI changes to 1
0.5	0	1	1	$1 \Leftarrow 0$	F changes to 1 after a 0.5 ns delay
0.8	$1 \Leftarrow 0$	1	$1 \Rightarrow 0$	1	FI changes to 0
0.13	1	1	0	$1 \Rightarrow 0$	F changes to 0 after a 0.5 ns delay



► Gate Delay Models

  - Suppose gates with delay 'k' ns are represented for $k = 0.2\text{ns}$, $k = 0.4\text{ns}$, $k = 0.5\text{ns}$, respectively



▶ Circuit Delay Models

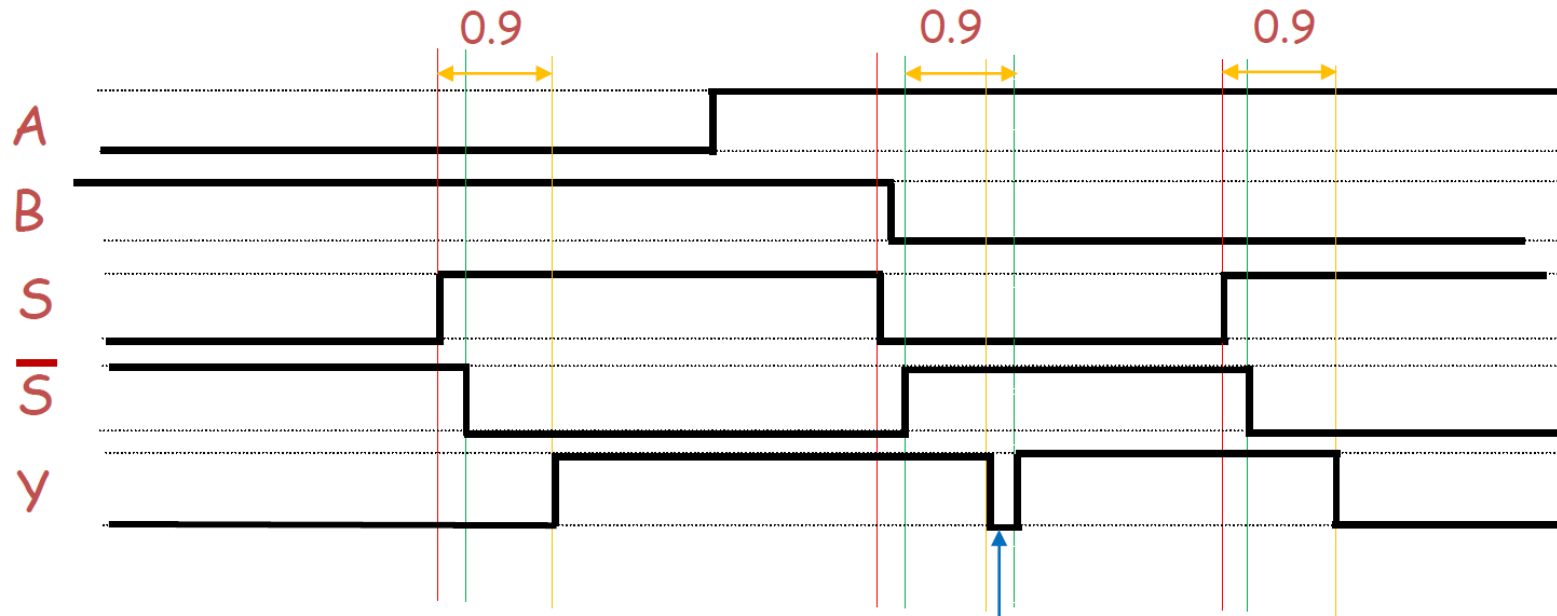 - Consider a simple 2-input multiplexer:
- With function:
 - $y = B$ for $S = 1$
 - $y = A$ for $S = 0$




"computer glitch" is due to delay of inverter

► Storage Elements (Memory)

- A storage element can maintain a binary state (0,1) indefinitely, until it is directed by an input signal to switch state
- Main difference btw storage elements:
 - # of inputs they have
 - How the inputs affect the binary state
- Two main types:
 - Latches (level-sensitive): useful in asynchronous circuits
 - Flip-flops (edge-sensitive): build w/ latches – synchronous circuits


► Synchronous Sequential Circuits

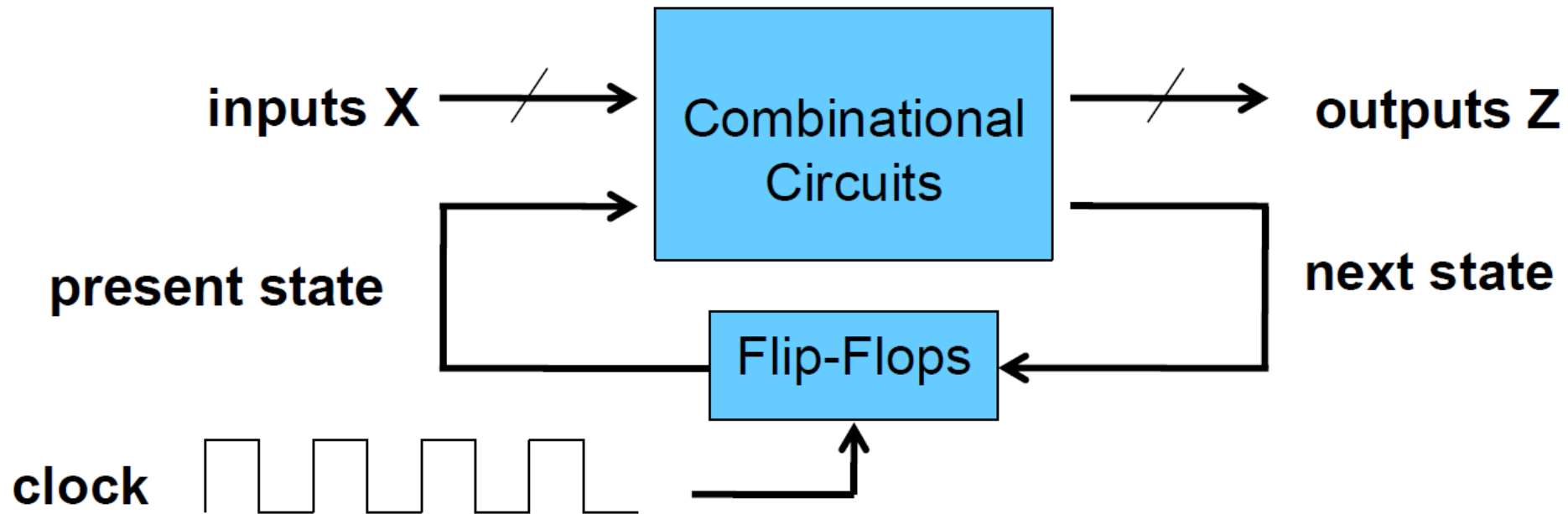- Synchronous circuits employs a synchronizing signal called **clock**
- A clock determines **when** computational activities occur
- Other signals determine **what** changes will occur




► Synchronous Sequential Circuits

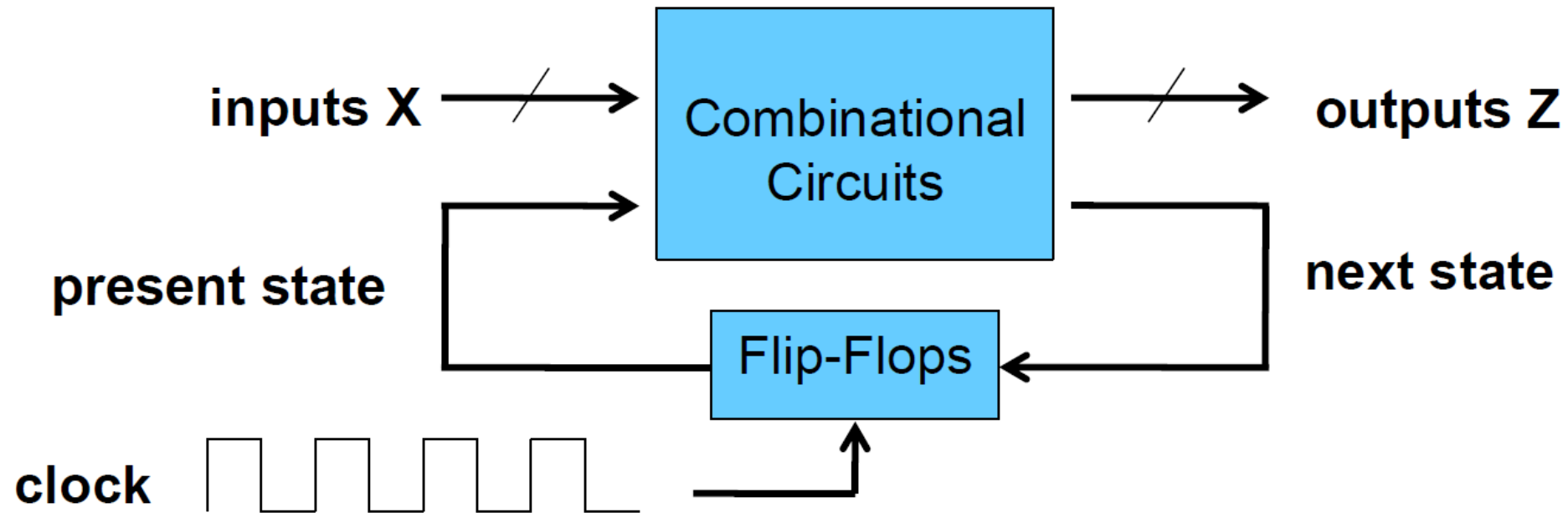
- The storage elements used in clocked sequential circuits are called **flip-flops (FFs)**
 - Each FF can store 1bit of information
 - A circuit may use many FFs: they define the circuit state



► System Clock

 


► System Clock

 


- Clock period (normally measured in micro- or nanoseconds) is the time between successive transitions in the same direction.
- Clock frequency (measured in MHz or GHz) is the reciprocal of clock period
- Clock width is the time interval during which clock is equal to 1
- Duty cycle is the ratio of the clock width and clock period
- Clock signal is **ACTIVE HIGH** if the changes occur at the rising edge or during the clock width. Otherwise, it is active low.

▶ System Clock

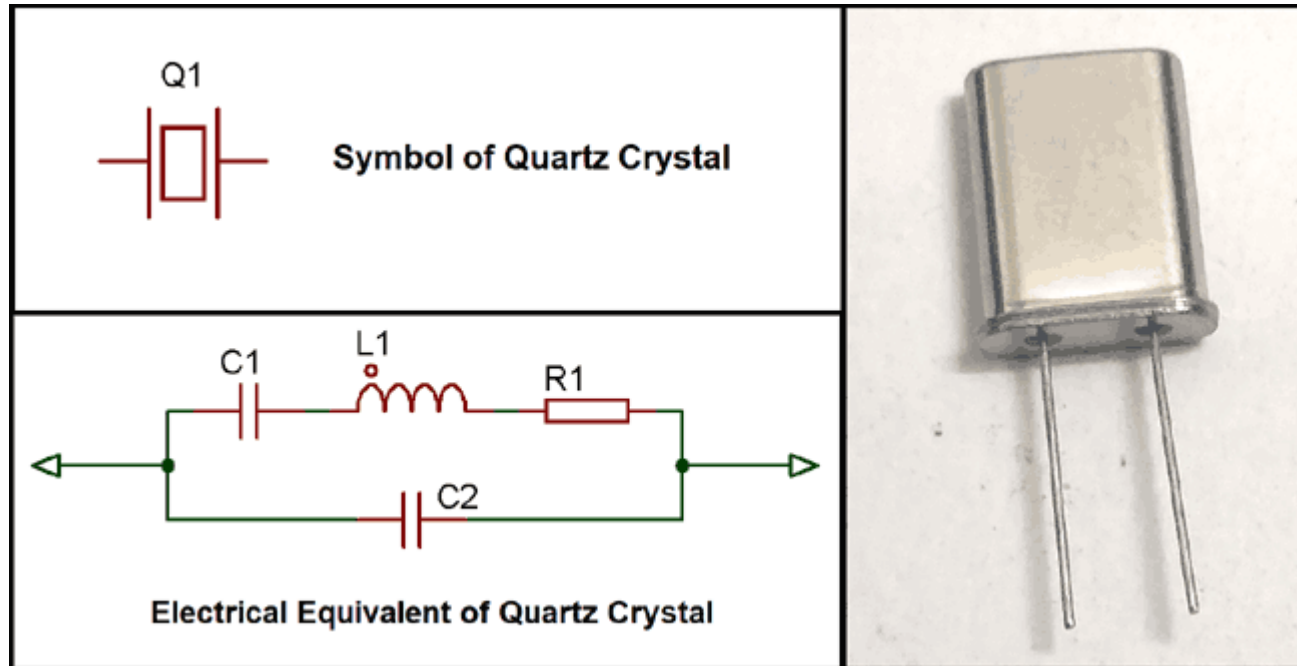

 Quartz frequency = 32,768 Hz ($=2^{15}$)
 > 15bit binary counter will count 1 sec.





Latches

► What are Latches?

- A latch is a binary storage element
 - Can store 0 or 1
- The most basic memory component
- Easy to build
 - Build with primitive gates (NORs, NANDs, INV)







► First Attempt for Bit Storage

  - We need some sort of feedback
 - Does a circuit on the right do what we want?




► Bit Storage Using SR Latch

      - Does the circuit to the right, with cross-coupled NOR gates, do what we want?



► SR Latch

 - **Two states:** 'set' ($Q = 1$) and 'reset' ($Q = 0$)
 - When $S = R = 0$, Q remains the same (**$S = R = 1$ is not allowed!**)
 - **State of the circuit depends** not only on the current inputs, but **also on the recent history of the inputs**






S	R	Q	\bar{Q}	
1	0	1	0	Set state
0	0	1	0	
0	1	0	1	Reset state
0	0	0	1	
1	1	0	0	Undefined



Function table

► Problem with SR Latch

   - If $S = R = 1$ simultaneously, we don't know what value Q will take




  Q may oscillate. Then, because one path will be slightly longer than the other, Q will eventually settle to 1 or 0 - but we don't know which.



► Basic (NAND) S'R' Latch

 - “Cross-coupling” two NAND gates gives the S'-R' latch
- Which has the time sequence behavior of:




Time	\bar{R}	\bar{S}	Q	\bar{Q}	Comment
	1	1	?	?	Stored state unknown: 01/10
	1	0	1	0	"Set" Q to 1
	1	1	1	0	Now Q "remembers" 1
	0	1	0	1	"Reset" Q to 0
	1	1	0	1	Now Q "remembers" 0
	0	0	1	1	Both go high Unstable!

forbidden

► S'R' Latch

 - Similar to SR latch (complemented)
 - Two states: 'set' ($Q = 0$) and 'reset' ($Q = 1$)
 - When $S = R = 1$, Q remains the same
 - **$S = R = 0$ is not allowed!**




Logic diagram

S	R	Q	\bar{Q}	
0	1	1	0	Set state
1	1	1	0	
1	0	0	1	Reset state
1	1	0	1	
0	0	1	1	Undefined


Function table

► More Problems with S'R' Latch

 - The problem occurs even if SR inputs come from a circuit that supposedly never set $S = 1$ and $R = 1$ at the same time
 - But it may happen, due to different delays of different paths




 The longer path from X to R than to S causes $SR=11$ for short time - could be long enough to cause oscillation



► S'R' Latch with Clock

 - An SR latch can be modified to control when it changes an additional input signal 'Clock (C)'
 - When $C = 0$, the S and R inputs have no effect on the latch
 - When $C = 1$, the inputs affect the state of the latch and possibly the output




Logic diagram

C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; Reset state
1	1	0	$Q = 1$; Set state
1	1	1	Undefined

Function table

► Dealing with the Undefined State (S'R' Latch)

 - How can we eliminate the undefined state?




Logic diagram

C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	Q = 0; Reset state
1	1	0	Q = 1; Set state
1	1	1	Undefined

forbidden

Function table

► D Latch

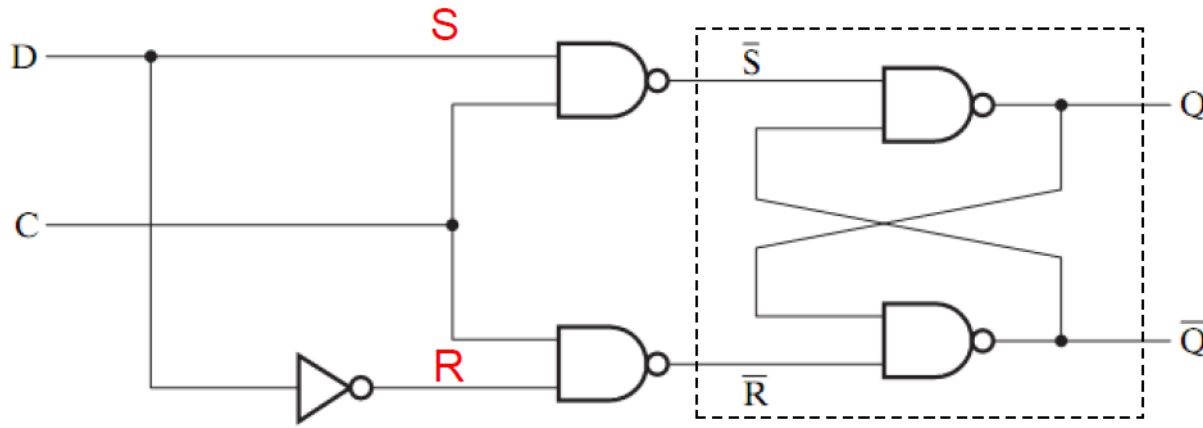


Logic diagram

C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

Function table

- Ensure S and R are never equal to 1 at the same time
 - **Add inverter**
- Only one input (D)
 - D stands for 'data'
- Output follows input when $C = 1$
 - **Transparent**
- When $C = 0$, Q remains the same

► Graphical Symbols for Latches

 


- A latch is designated by a rectangular block with inputs on the left and outputs on the right
- For $S'R'$ latch (w/ NANDs), bubbles are added to the input

Flip-Flops

► Issues with Latches



- What happens if Clock = 1?

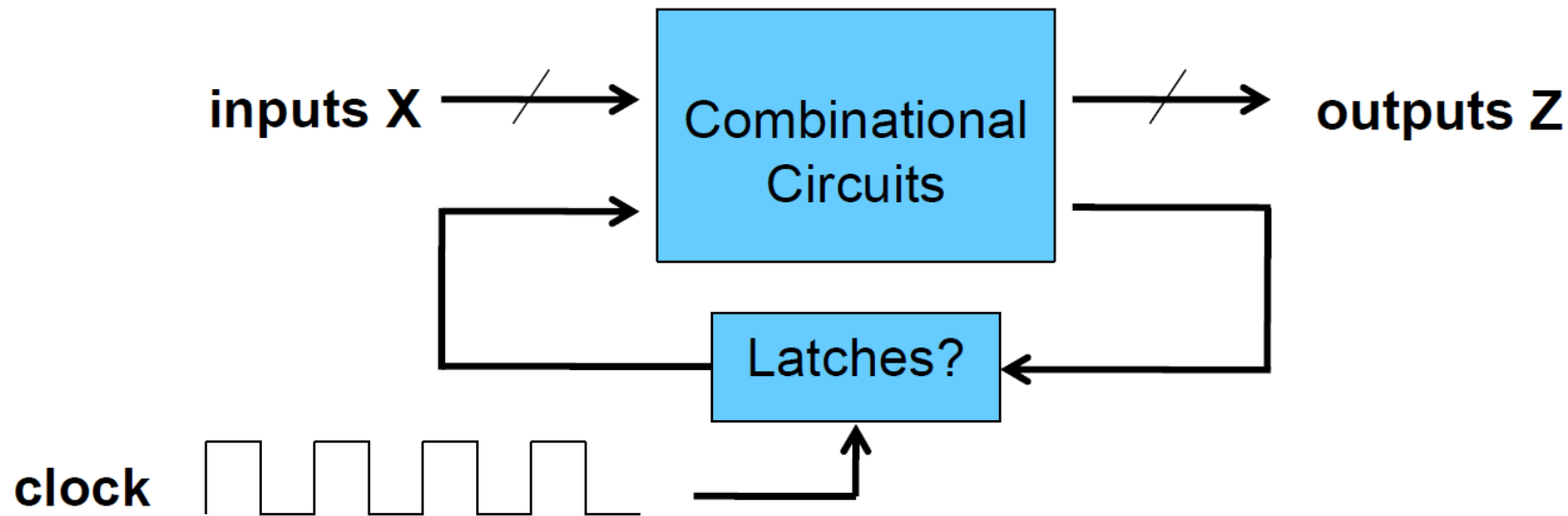- A latch is **transparent**: state keeps changing as long as clock remains active
- Due to this uncertainty, latches cannot be **reliably** used as storage elements



► Timing Problem in Latches

  
- Consider the following circuit
- Suppose that initially $y = 0$



- ✓ As long as $C = 1$, the value of y continues to change!
- ✓ The changes are based on the delay present on the loop
- ✓ This behavior is clearly unacceptable
- ✓ **Desired behavior:** y changes **only once** per clock pulse


► Flip-Flops (FFs)

 - A flip-flop is an 1bit memory similar to latches
- Solves the issue of latch transparency
 - Note that latches are level-sensitive
 - Active when the clock = 1 (whole duration)
- FFs are edge-triggered or edge-sensitive memory
 - Active only at transitions, i.e. either from $0 \rightarrow 1$ or $1 \rightarrow 0$




► Design of a Flip-Flop

- FF can be built using two latches in a **master-slave** configuration
 - A master latch receives external inputs
 - A slave latch receives inputs from the master latch
- Depending on the clock signal, only one latch is active
 - If $\text{clk} = 1$, the master latch is enabled and **inputs are latched**
 - If $\text{clk} = 0$, the master is disabled and the **slave is activated to generate outputs**

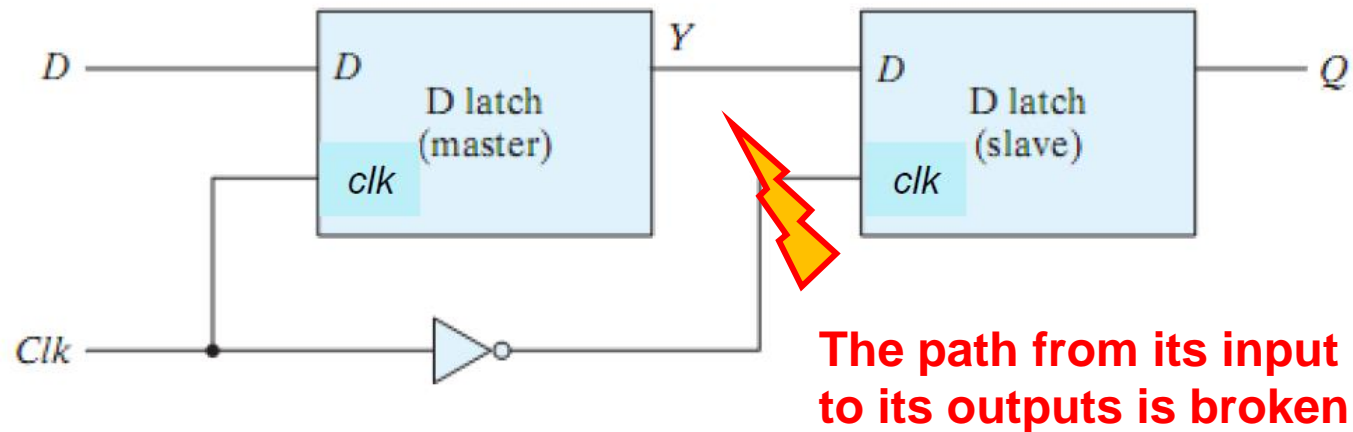


► Property of a Flip-Flop

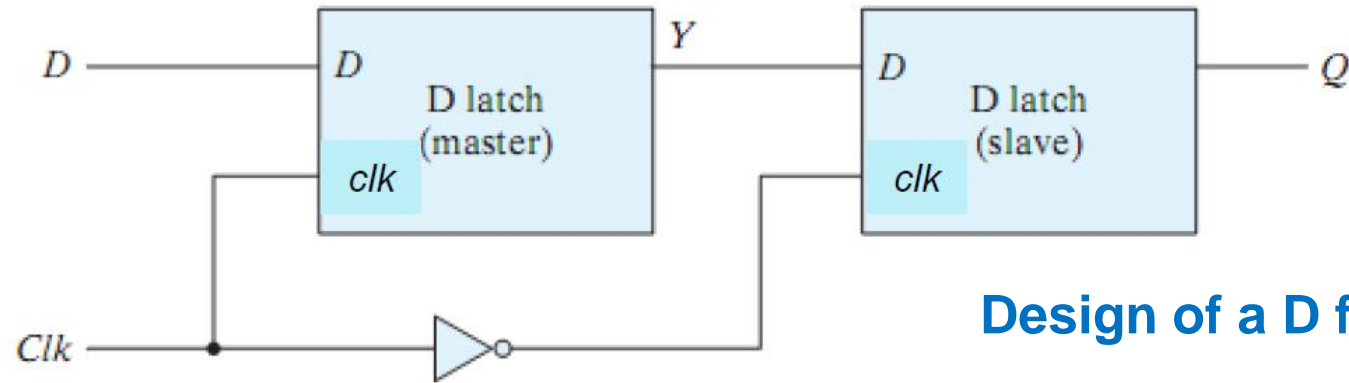

Design of a D flip-flop


• Important timing considerations

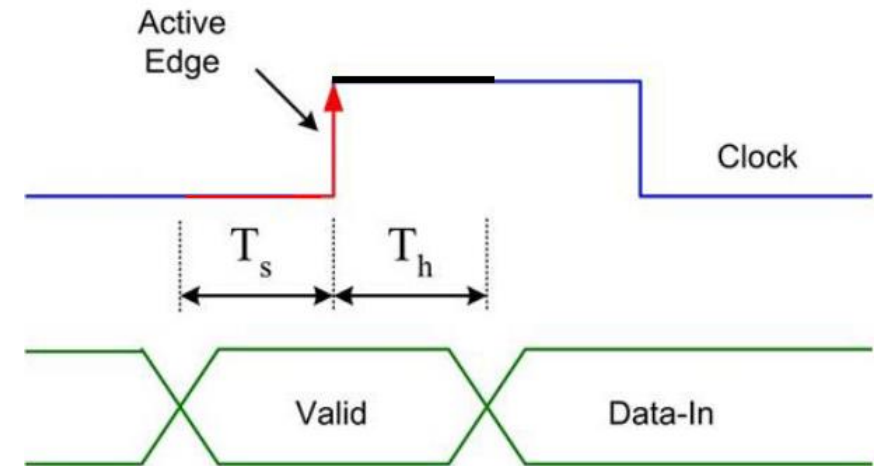- **Setup Time (T_s):** The minimum time during which D input must be maintained before the clock transition occurs.
- **Hold Time (T_h):** The minimum time during which D input must not be changed after the clock transition occurs.





► SR Flip-Flop

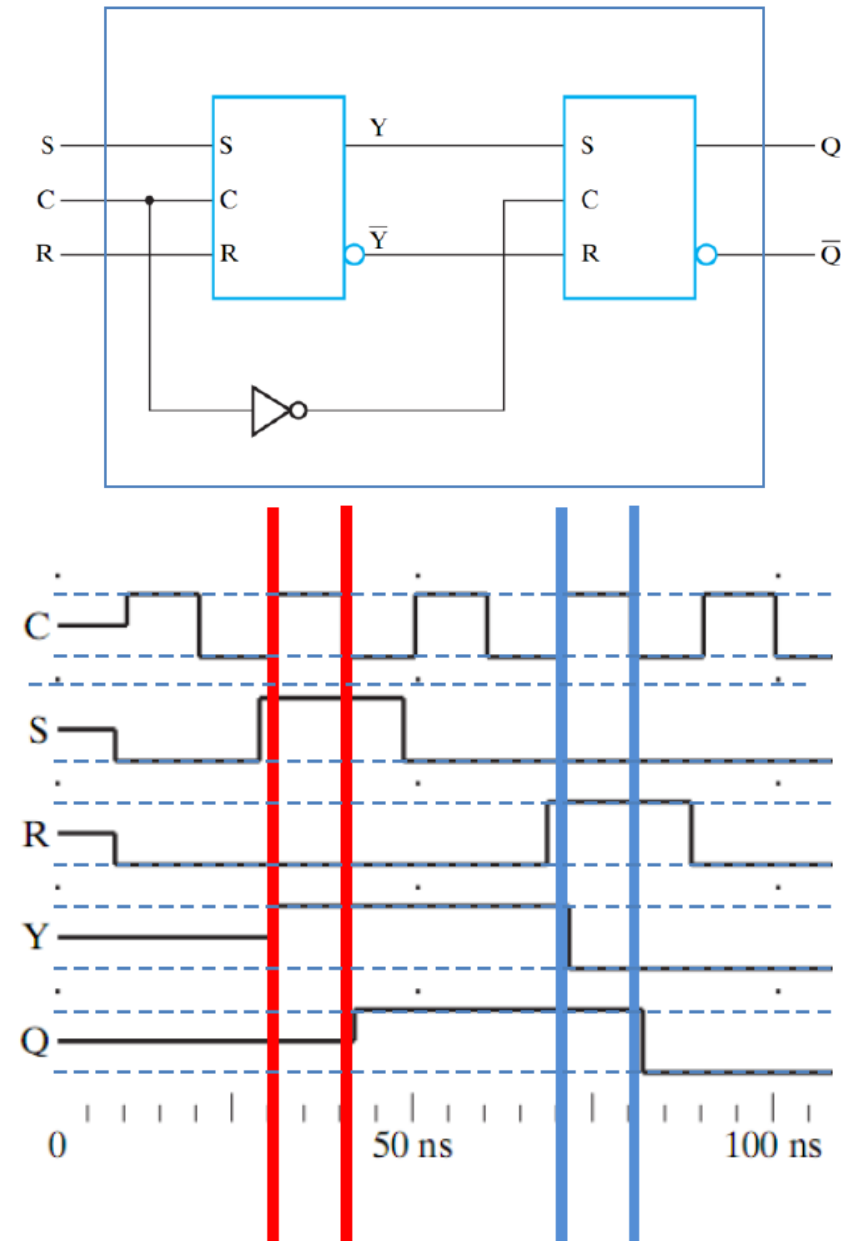- Built using two SR latches (master and slave)
- Data is entered on the rising edge of the clock pulse
 - But, the output does not reflect the change until the falling edge
- Q is sampled at the falling edge




► More on Simulation of SR Flip-Flops

 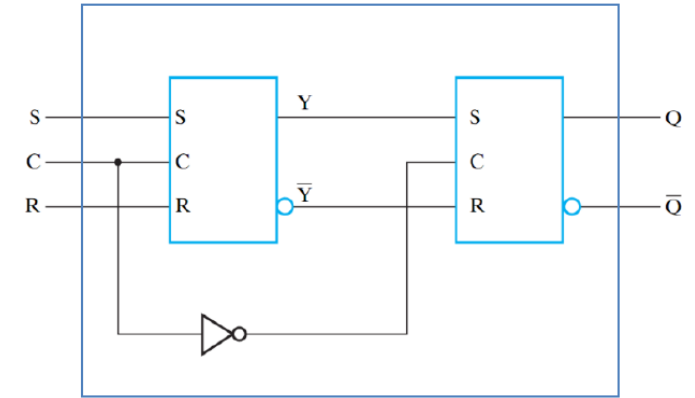


► Edge-Triggered D Flip-Flop

 - The change of D flip-flop output is associated w/ negative edge at the end of the pulse
(**negative-edge triggered FF**)



 - **Positive-edge triggered**
D flip-flop is formed by adding an inverter to 'C' input




C(0→1): copies the state of the master latch

► D-Type Positive Edge-Triggered Flip-Flop

- An efficient construction of an edge-triggered D FF uses three SR latches

- Two latches respond to D and CLK
- The third latch provides Q

 
- ✓ If $CLK = 0$, both output signals of input stage are 1 regardless of D
- ✓ The output latch is unaffected and it stored the previous state



► D-Type Positive Edge-Triggered Flip-Flop

- An efficient construction of an edge-triggered D FF uses three SR latches

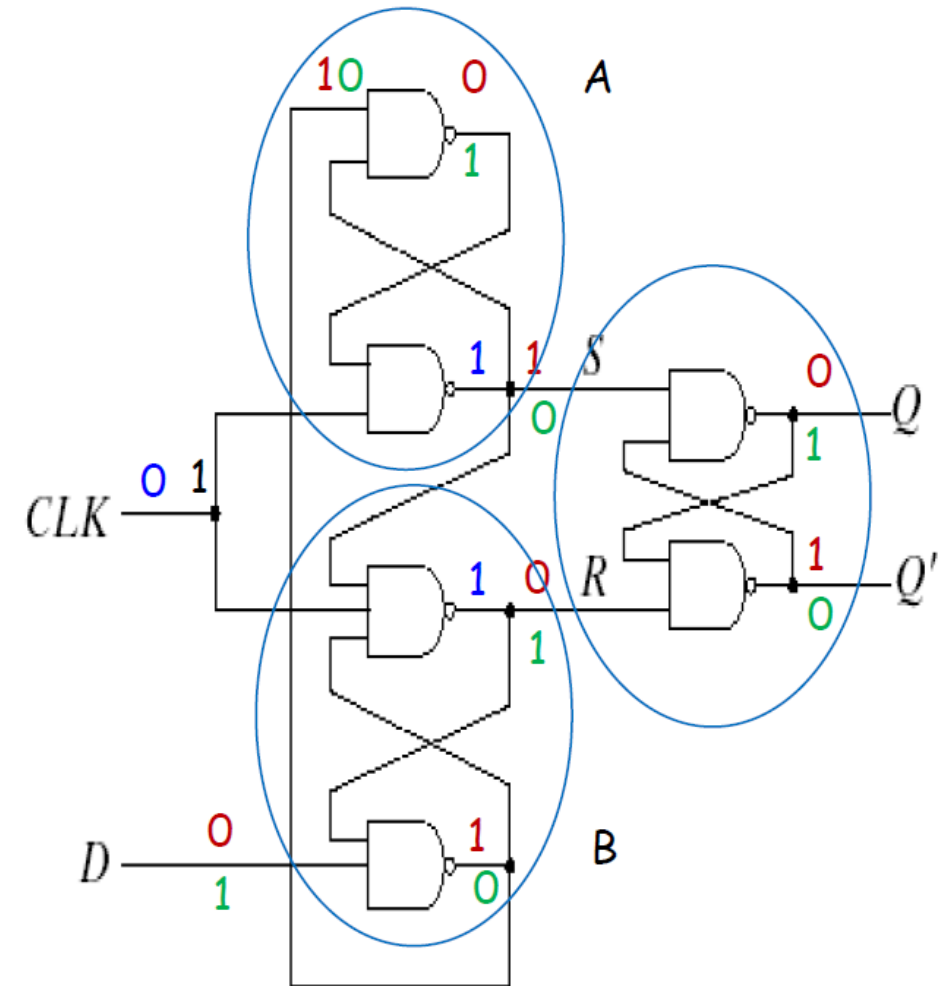- ✓ When CLK goes from 0 to 1, only one of the output voltages goes to 0 & sets/resets the output latch
- ✓ Consider $D = \text{CLK} = 0$ with $\{R, S\} = 2'b11$. What happens with CLK $0 \rightarrow 1$?
- ✓ Consider $\text{CLK} = 0, D = 1$ with $\{R, S\} = 2'b11$. What happens with CLK $0 \rightarrow 1$?



► State Transition for Previous D Flip-Flop

- To analyze the previous FF design, the next state equations are:

$$S_+ = (\overline{C} \cdot \overline{A}) = \overline{C} + \overline{A} = \overline{C} + B \cdot S = \overline{C} + (\overline{D} + \overline{R}) \cdot S$$


$$R_+ = \overline{S} + \overline{C} + \overline{B} = \overline{S} + \overline{C} + R \cdot D$$

- These equations lead to the following flow table where input variables are: C (CLK), D, R, and S


C	D	R	S	R+	S+
0	0	0	0	1	1
0	0	0	1	1	1
0	0	1	0	1	1
0	0	1	1	1	1
0	1	0	0	1	1
0	1	0	1	1	1
0	1	1	0	1	1
0	1	1	1	1	1
1	0	0	0	1	0
1	0	0	1	0	1
1	0	1	0	1	0
1	0	1	1	0	1
1	1	0	0	1	0
1	1	0	1	0	1
1	1	1	0	1	0
1	1	1	1	1	0

► Standard Graphics Symbols

 
- A rectangular block with inputs (left) and outputs (right)
 - Bubble represents the complement
 - Ex) S`R` latch
- The inverters unfortunately cause the clock signal to these FFs to be delayed
 - Careful design of **clock tree** is required



(a) Latches

 


(b) Master-slave flip-flops

 

 (c) Edge-triggered flip-flops


► Other Flip-Flops

- D flip-flop is the most economical and efficient (why?)
 - Still, there are other types of FFs that are less widely used
 - **JK** and T flip-flops
 - ✓ Set to 1, reset to 0, or complement output





► Other Flip-Flops

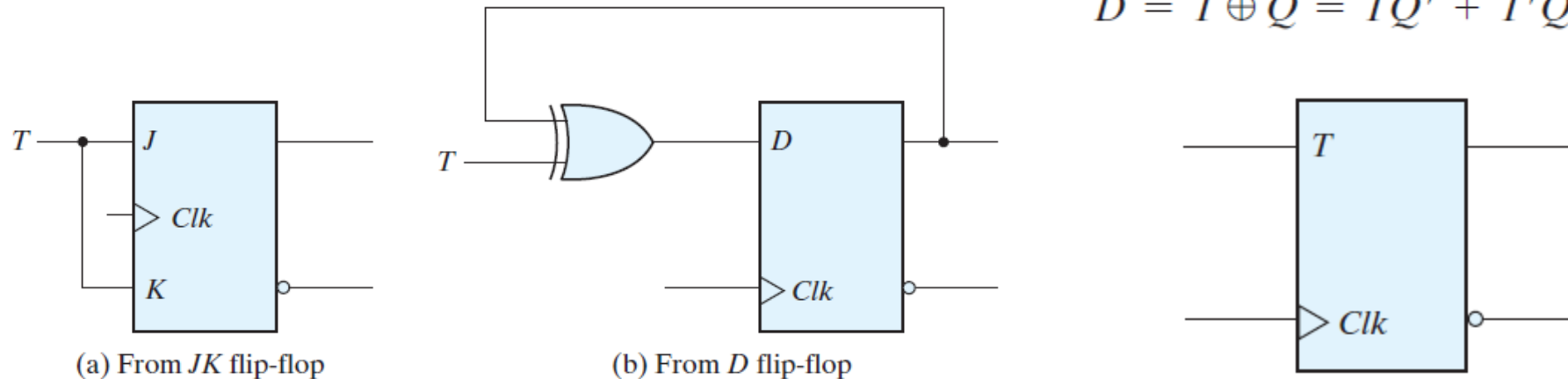- D flip-flop is the most economical and efficient (why?)
 - Still, there are other types of FFs that are less widely used
 - JK and **T flip-flops** (toggle FF)



► Direct Inputs

  - Some FFs have asynchronous inputs to force FF to a particular state
 - Direct set (preset): sets FF to 1
 - Direct reset (clear): sets FF to 0
 - Good to bring all FFs to a known starting state after power-on



R	Clk	D	Q	Q'
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0

Function table